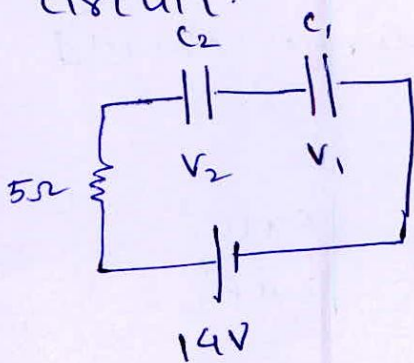


CAPACITOR

①

1] ②

In steady state, no current will flow through the circuit.



$$\therefore V_1 + V_2 = 14$$

$$\therefore \frac{Q}{C_1} + \frac{Q}{C_2} = 14$$


$$\therefore Q \left(\frac{1}{5} + \frac{1}{2} \right) = 14$$

$$\therefore Q = 14 \times \frac{10}{7}$$

$$\therefore Q = 20 \mu\text{C}$$

$$\therefore C_2 = \frac{Q}{V_2} \Rightarrow V_2 = \frac{Q}{C_2} = \frac{20}{2} = 10\text{V}$$

2] ③

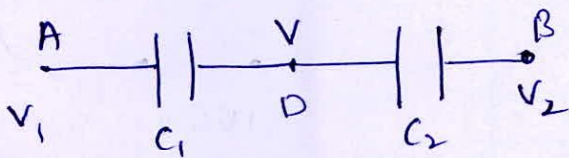

$$V_1 - V = \frac{Q}{C_1} \quad \text{--- (1)}$$

$$V - V_2 = \frac{Q}{C_2} \quad \text{--- (2)}$$

charge on both capacitors will be same as they are in series.

$$\therefore Q = C_2 (V - V_2) \quad \dots \text{ (from (2))}$$

Putting this in (1),

$$V_1 - V = \frac{C_2 (V - V_2)}{C_1}$$

$$\therefore C_1 V_1 - C_1 V = C_2 V - C_2 V_2$$

$$\therefore C_1 V_1 + C_2 V_2 = (C_1 + C_2) V \Rightarrow V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

3] ④

$$Q_1 = C_1 V_1 = 1 \times 6 = 6 \times 10^{-3} \text{ C}$$


$$Q_2 = C_2 V_2 = 2 \times 4 = 8 \times 10^{-3} \text{ C}$$

∴ When connected in series charge on both capacitors will be same, so the charge should not exceed $6 \times 10^{-3} \text{ C}$.


$$\begin{aligned} \therefore N_1 + V_2 &= \frac{Q_1}{C_1} + \frac{Q_2}{C_2} = \frac{6 \times 10^{-3}}{1 \mu\text{F}} + \frac{6 \times 10^{-3}}{2 \mu\text{F}} \\ &= (6 + 3) \text{ KV} \\ &= 9 \text{ KV} \end{aligned}$$

②


4] ④

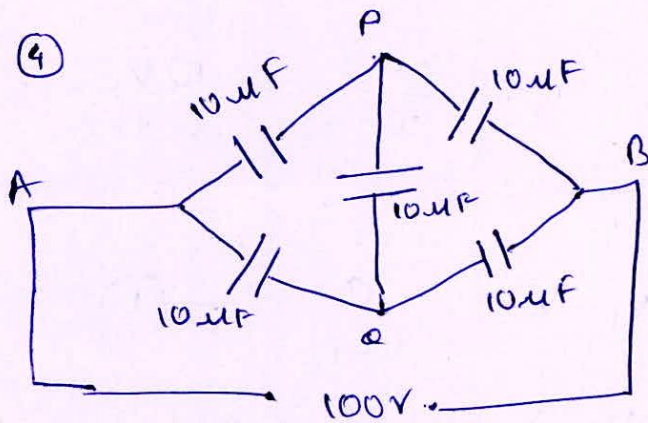


⇒

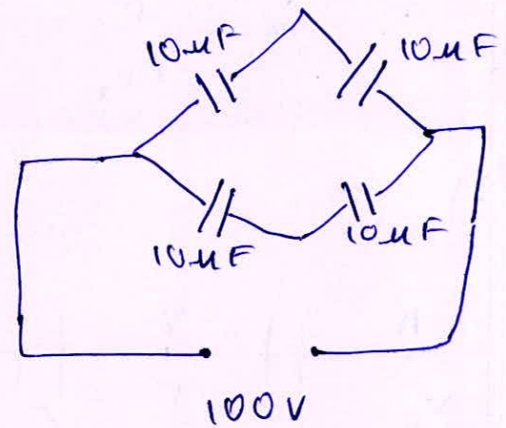

⇓

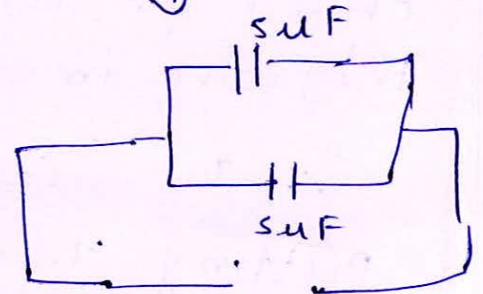

⇐

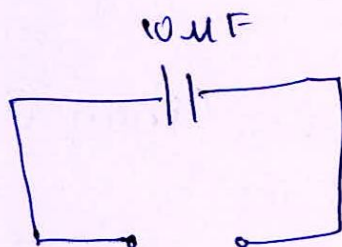

5] (3)


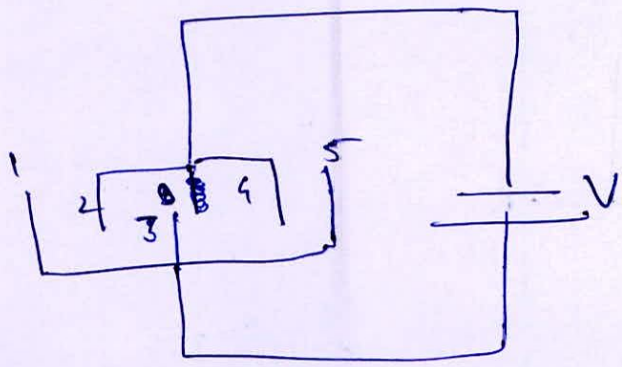


plate 3, 1 and 5 will be at potential V and 2, 4 will be at the potential of 0.


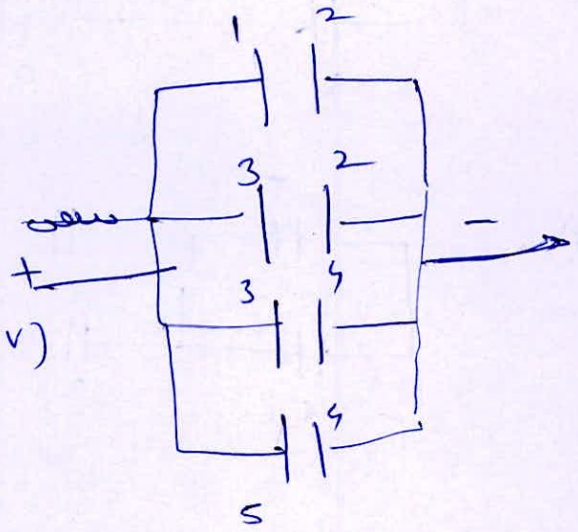


charge on 1 = $+CV$

charge on plate 4 = $-CV + (-CV) = -2CV$

6

6] (2)

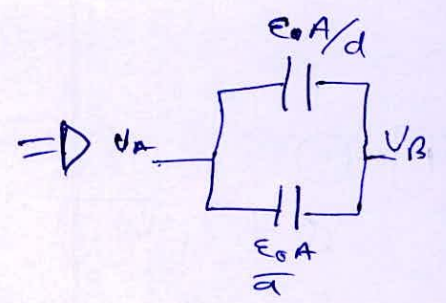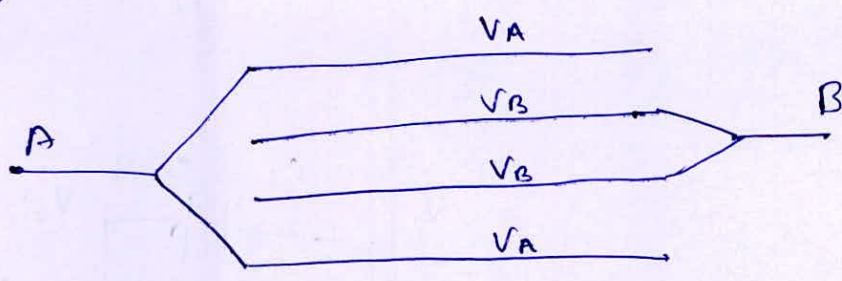

So equivalent capacitance will be $\frac{2\epsilon_0 A}{d}$

7] (3)

$$E_1 = E_2 = \frac{Q}{2C} = \frac{1}{2} CV^2 = E$$


When dielectric is inserted

$$E_1' = \frac{1}{2} CKV^2 = KE_1^2$$

$$E_2' = \frac{Q}{2Kc} = \frac{1}{K} E_2$$




$$\therefore \text{Ratio} = \frac{E_1 + E_2}{E_1' + E_2'}$$
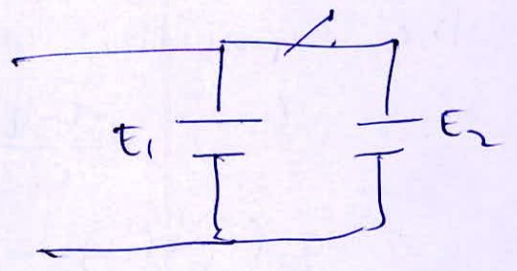
$$\therefore \text{Ratio} = \frac{6}{10} = \frac{3}{5} = \frac{2E}{(3 + \frac{1}{3})E}$$



8) ①


④

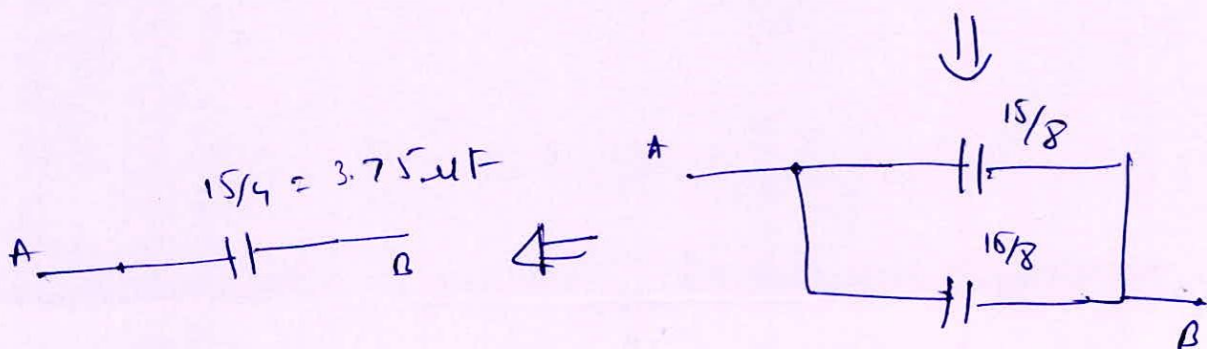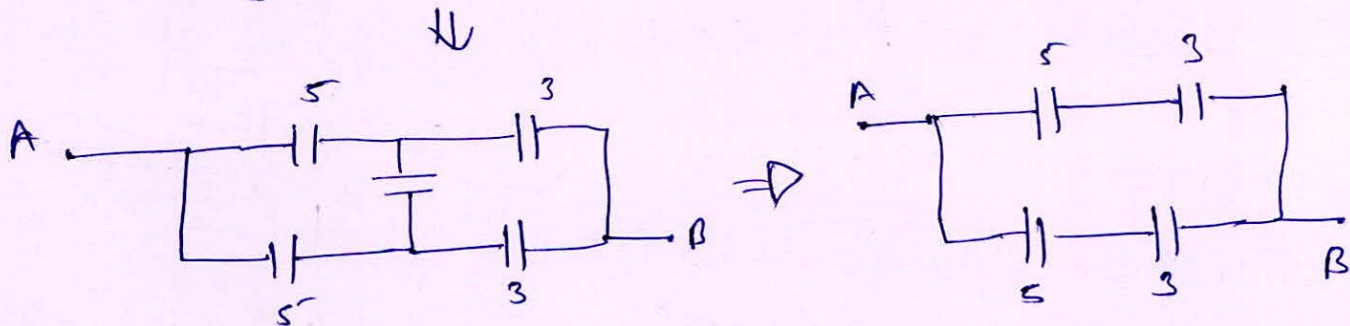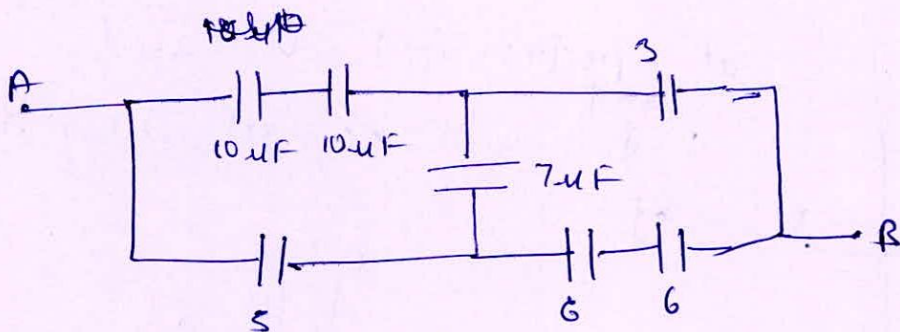

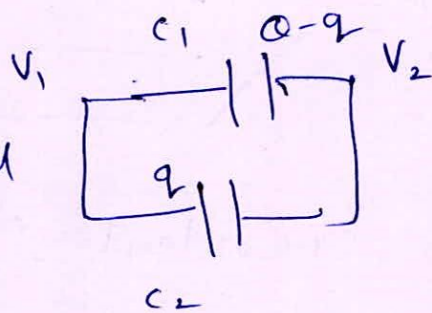10) ①

$$Q = C_1 V$$

When the capacitor is connected to another capacitor, the charge will get redistributed and potential across both the capacitors will be same.



$$\therefore \frac{q}{C_2} = \frac{Q-q}{C_1} \Rightarrow qC_1 = QC_2 - qC_2$$

$$\therefore q(C_1 + C_2) = QC_2 \Rightarrow q = \frac{QC_2}{C_1 + C_2}$$

$$\therefore V_2 - V_1 = \frac{q}{C_2} = \frac{QC_2}{\frac{C_1 + C_2}{C_2}} = \frac{Q}{C_1 + C_2} = \frac{C_1 V}{C_1 + C_2}$$

11] (1)

$$U = \frac{1}{2} C_1 V^2$$

$$U_2 = \frac{1}{2} C_1 (V_2 - V_1)^2 + \frac{1}{2} C_2 (V_2 - V_1)^2$$

$$= \frac{1}{2} (C_1 + C_2) (V_2 - V_1)^2$$

$$= \frac{1}{2} (C_1 + C_2) \frac{C_1^2 V^2}{(C_1 + C_2)^2} = \frac{1}{2} \frac{C_1^2 V^2}{C_1 + C_2} = \frac{1}{2} C_1 V^2 \times \frac{C_1}{C_1 + C_2}$$


$$\therefore U_2 = \frac{U C_1}{C_1 + C_2}$$

(5)

12] (2)

$$C_2 = k_1 \frac{\epsilon_0 A}{d/2} = \frac{2k_1 \epsilon_0 A}{d}$$
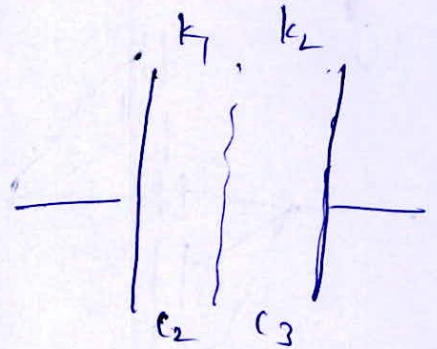
$$C_3 = k_2 \frac{\epsilon_0 A}{d/2} = \frac{2k_2 \epsilon_0 A}{d}$$



$$\therefore C_{eq} = \frac{C_2 C_3}{C_2 + C_3} = \frac{\left(\frac{\epsilon_0 A}{d}\right)^2 4k_1 k_2}{\left(\frac{\epsilon_0 A}{d}\right) (2k_1 + 2k_2)}$$

$$\therefore C_{eq} = \frac{2k_1 k_2}{k_1 + k_2} \frac{\epsilon_0 A}{d}$$

$$C = \frac{\epsilon_0 A}{d}$$

$$\therefore C_{eq} = \left(\frac{2k_1 k_2}{k_1 + k_2} \right) C$$

14] (2)

As the capacitors are in series, the charges on both capacitors are same

$$q = CV \Rightarrow V = \frac{q}{C_1}$$

$\therefore \Delta V \propto \frac{1}{C_1}$ As the change in potential across C_1 is greater, $C_1 < C_2$


16] ④

As the capacitors are in series, the charges on the capacitors will be same. ⑤





17] ①

The charge on +2C point will become zero.
 ∴ The force will be zero.


18] ①

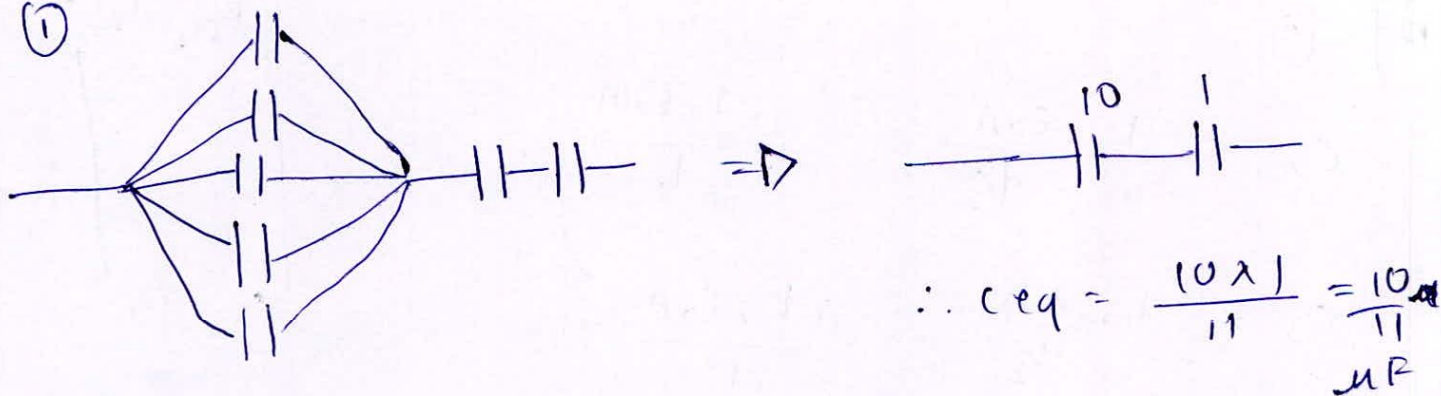


19] ①

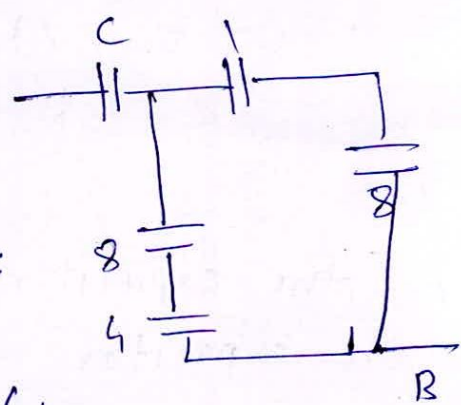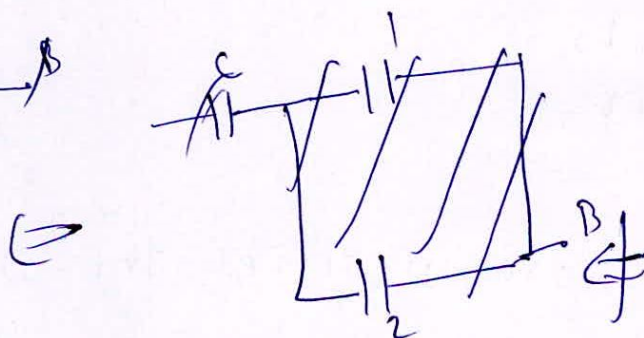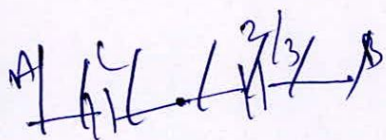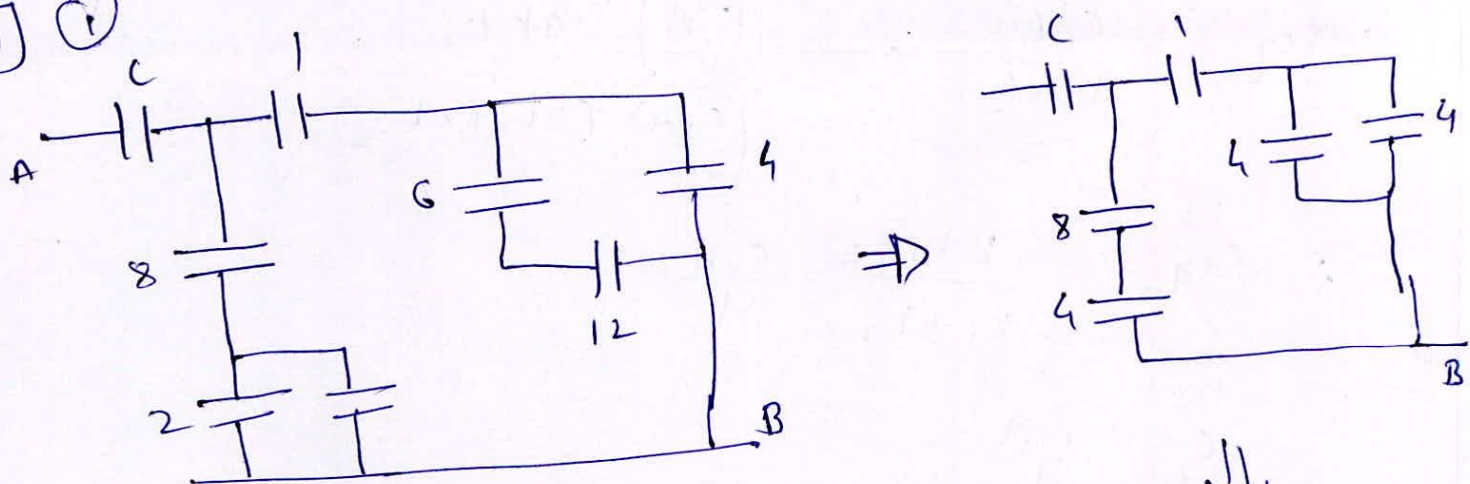

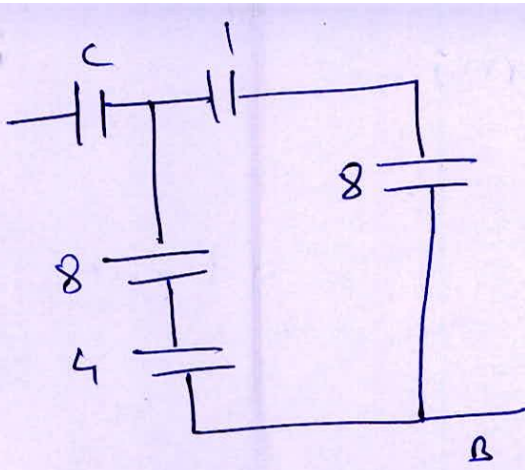
Now, $\frac{C \times \frac{2}{3}}{C + \frac{2}{3}} \neq \frac{2C}{2C + 2} \neq \frac{1}{3C + 2}$



\Rightarrow

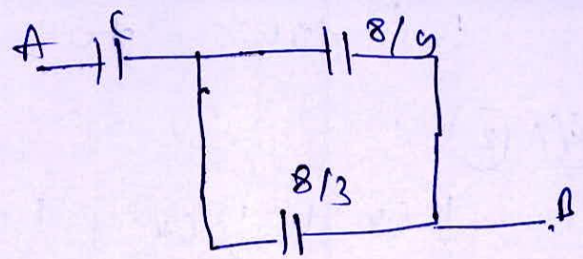

\Downarrow

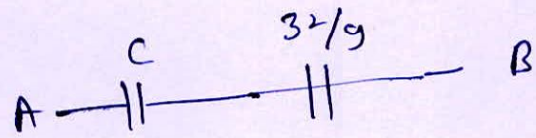

(7)

$$\therefore \frac{C \times \frac{32}{g}}{C + \frac{32}{g}} = 1$$

$$\therefore \frac{32C}{32 + 9C} = 1 \Rightarrow$$

$$32C = 32 + 9C$$

$$\therefore 23C = 32$$

$$\therefore C = \frac{32}{23} \mu\text{F}$$

20] (1)

$$C_1 = \frac{\epsilon_0 A}{d}$$

$$C_2 = k_1 \frac{\epsilon_0 A}{2d} + k_2 \frac{\epsilon_0 A}{2d}$$

$$\therefore C_2 = \frac{k_1 + k_2}{2} \left(\frac{\epsilon_0 A}{d} \right)$$

$$\therefore C_2 = \frac{k_1 + k_2}{2} C_1$$

(\because the capacitors will be in series)

Windows to JEE main

8

1) (4) (2)

$$E = \frac{1}{2} CV^2 + \frac{1}{2} CV^2 + \frac{1}{2} CV^2 + \dots \quad n \text{ times}$$

$$\therefore E = \frac{1}{2} n CV^2$$

2) (1)


$$E = 4\pi\epsilon_0 R$$

$$\therefore E = \frac{R}{K} = \frac{1}{9 \times 10^9} = 1.1 \times 10^{-10}$$

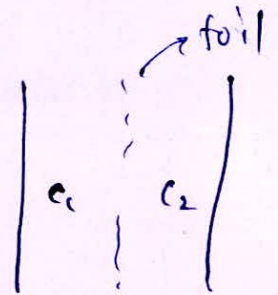3) (1)

When aluminium foil is inserted, the two capacitances will be in series

\therefore The net capacitance will decrease



4) (4)

Work done will be equal to the energy stored

$$\therefore W = \frac{1}{2} CV^2$$

$$= \frac{1 \cdot 0^2}{2C}$$

$$= \frac{64 \times 10^{-36}}{2 \times 10^{-4}} = 32 \times 10^{-32} \text{ J}$$

5) (1)

For n plates, number of capacitors formed will be $n-1$

$$\therefore C_{eq} = (n-1)C$$

10] (3)

$$q = CV$$

$$\frac{dq}{dt} = C \frac{dV}{dt} \Rightarrow 2 = 10^{-6} \times \frac{dV}{dt}$$

$$\therefore \frac{dV}{dt} = 2 \times 10^6 \text{ V/s.}$$

(10)


11] (4)

$$C_0 = \frac{K \epsilon_0 A}{d}$$

$$C = \frac{2K \epsilon_0 A/3}{d} + \frac{K \epsilon_0 2A/3}{d}$$

$$= \frac{2}{3} \frac{K \epsilon_0 A}{d} + \frac{2}{3} \frac{K \epsilon_0 A}{d}$$
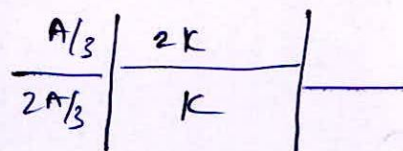
$$= \frac{4}{3} \frac{K \epsilon_0 A}{d}$$



The capacitors will be in parallel

12]

Potential on both can be zero, therefore charge on both capacitors should be equal.


$$\text{So, } C_1 V_1 = C_2 V_2$$

$$\therefore C_1 \times 120 = C_2 \times 200$$

$$\therefore 3C_1 = 5C_2$$

13]

(11)

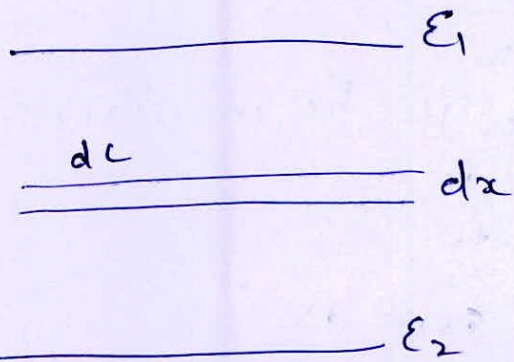

E at any x will be given by

$$E_x = E_1 + \left(\frac{E_2 - E_1}{d} \right) x$$

Capacitance for a small element will be given by

$$dC = \frac{E_x A}{d} = \frac{\left(E_1 + \left(\frac{E_2 - E_1}{d} \right) x \right) A}{dx}$$

All the capacitances will be in series.

$$\therefore \frac{1}{C_{eq}} = \int \frac{1}{dC}$$

$$= \int_0^d \frac{dx}{\left(E_1 + \left(\frac{E_2 - E_1}{d} \right) x \right) A}$$

$$= \frac{d}{(E_2 - E_1) A} \ln \left(E_1 + \left(\frac{E_2 - E_1}{d} \right) x \right) \Big|_0^d$$

$$= \frac{d}{(E_2 - E_1) A} \left[\ln(E_2) - \ln(E_1) \right]$$

$$\frac{1}{C_{eq}} = \frac{d}{(E_2 - E_1) A} \ln \left(\frac{E_2}{E_1} \right)$$

$$\therefore C_{eq} = \frac{(E_2 - E_1) A}{d \ln \left(\frac{E_2}{E_1} \right)}$$

14] (3)

$$dC = \frac{(k_0 + \lambda x) \epsilon_0 A}{dx} ; C_0 = \frac{\epsilon_0 A}{d} \text{ (12)}$$

All these will be in series.

$$\frac{dC}{dx}$$

$$\therefore \frac{1}{C_{eq}} = \int \frac{1}{dC}$$

$$= \int \frac{\epsilon_0 A dx}{\epsilon_0 A (k_0 + \lambda x)}$$

$$= \frac{1}{\epsilon_0 A} \int \frac{dx}{k_0 + \lambda x}$$

$$= \frac{1}{\epsilon_0 A} \frac{1}{\lambda} \ln(k_0 + \lambda x) \Big|_0^d$$

$$= \frac{1}{\lambda \epsilon_0 A} (\ln(k_0 + \lambda d) - \ln k_0)$$

$$= \frac{1}{\lambda \epsilon_0 A} \ln\left(1 + \frac{\lambda d}{k_0}\right)$$

$$\therefore C_{eq} = \frac{\lambda \epsilon_0 A}{\ln\left(1 + \frac{\lambda d}{k_0}\right)}$$

$$\therefore C_{eq} = \frac{\lambda d}{\ln\left(1 + \frac{\lambda d}{k_0}\right)} C_0$$

15]

$$C_{eq} = \frac{k \epsilon_0 A x}{d} + \frac{\epsilon_0 A (L-x)}{d}$$

$$U = \frac{Q^2 d}{2(k \epsilon_0 A x + \epsilon_0 A (L-x))}$$

$$A = \omega L$$

15] (3)

(13)

$$C_{eq} = \frac{\kappa \epsilon_0 \bar{w} x}{d} + \frac{\epsilon_0 \bar{w} (L-x)}{d}$$

$$\therefore U = \frac{Q^2}{2C_{eq}}$$

$$\therefore U = \frac{Q^2 d}{2(\kappa \epsilon_0 \bar{w} x + \epsilon_0 \bar{w} (L-x))}$$

$$F = -\frac{dU}{dx}$$


$$\therefore F = \frac{Q^2 d}{2(\kappa \bar{w} \epsilon_0 x + \epsilon_0 \bar{w} (L-x))^2} \times (\kappa \epsilon_0 \bar{w} - \epsilon_0 \bar{w})$$

\therefore At $x=0$


$$F = \frac{Q^2 d \epsilon_0 \bar{w} (\kappa - 1)}{2(\epsilon_0 \bar{w} L)^2}$$

$$\therefore F = \frac{Q^2 d (\kappa - 1)}{2 \epsilon_0 \bar{w} L^2}$$


16] (4)

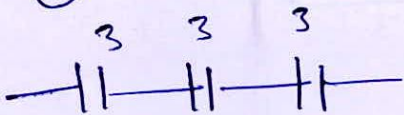

$$C_{eq} = \frac{3}{3} = 1 \mu F$$

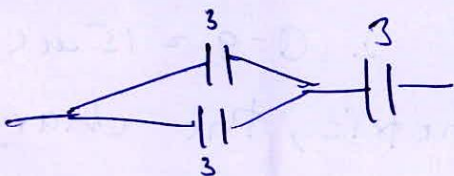
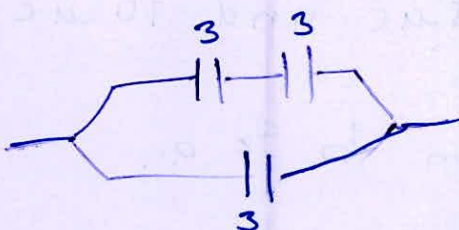
$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{3} \Rightarrow C_{eq} = 2 \mu F$$



$$C_{eq} = \frac{3}{2} + 3 = 4.5 \mu F$$

We cannot get $6 \mu F$ as C_{eq}

17] (4)

$$E \times d = V = \frac{Q}{K \epsilon_0 A}$$

$$\therefore E \times d = \frac{Qd}{K \epsilon_0 A}$$


$$\therefore \frac{Q}{A} = E \times K \times \epsilon_0$$

$$= 3 \times 10^4 \times 2.2 \times 8.85 \times 10^{-12}$$

$$\approx 6 \times 10^{-7} \text{ C/m}^2$$

18] (1)

When the switch is closed,

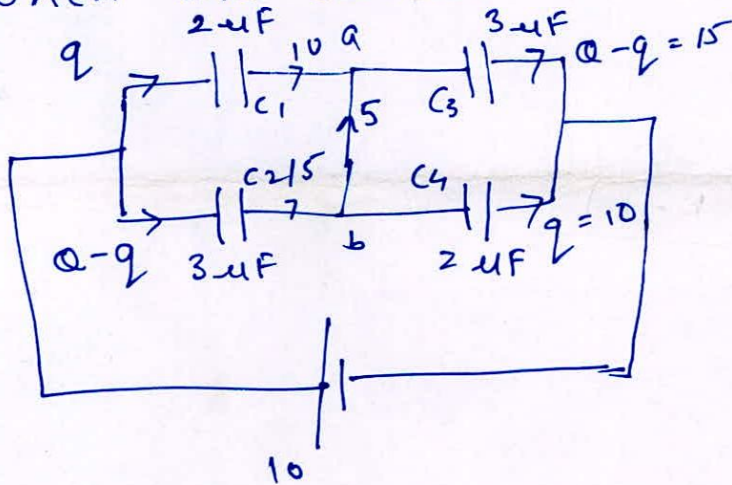

$$\frac{1}{C_{eq}} = \frac{1}{5} + \frac{1}{5}$$

$$\therefore C_{eq} = \frac{5}{2}$$

$$\therefore Q = C_{eq} V$$

$$= \frac{5}{2} \times 10$$

$$Q = 25 \mu\text{C}$$

Now, the $2 \mu\text{F}$ and $3 \mu\text{F}$ are in parallel

$$\therefore \frac{q}{2} = \frac{Q-q}{3} \Rightarrow \frac{q}{2} = \frac{25-q}{3}$$

$$\therefore 3q = 50 - 2q$$

$$\therefore 5q = 50 \Rightarrow q = 10 \mu\text{F} \quad \therefore Q-q = 15 \mu\text{C}$$

Now as the structure is symmetric, the charges through C_3 and C_4 will be $15 \mu\text{C}$ and $10 \mu\text{C}$ respectively

$\therefore 5 \mu\text{C}$ charge will flow from b to a .

(14)