

JEE Main Exercise

1. (D)

$$R = R_0(1 + \alpha\Delta T)$$

$$60 = 20[1 + \alpha(500 - 20)]$$

$$\alpha = \frac{1}{240}/^{\circ}\text{C}$$

$$R = R_0(1 + \alpha\Delta T)$$

$$\Rightarrow 25 = 20\left(1 + \frac{1}{240}(T - 20)\right)$$

$$\Rightarrow T = 80^{\circ}\text{C}$$

2. (C)

At 0°C , $R_1 = 400\Omega$, $R_2 = 800\Omega$

$$R_{eq} = \frac{400 \times 800}{400 + 800} = \frac{800}{3}\Omega$$

At $t^{\circ}\text{C}$,

$$\frac{1}{R'_{eq}} = \frac{1}{R'_1} + \frac{1}{R'_2}$$

$$\frac{1}{\frac{800}{3}(1 + \alpha_{eq}t)} = \frac{1}{400(1 + \alpha t)} + \frac{1}{400(1 + 4\alpha t)}$$

$$\Rightarrow \frac{3}{800}(1 - \alpha_{eq}t) = \frac{1}{400}(1 - \alpha t) + \frac{1}{800}(1 - 4\alpha t)$$


$$\Rightarrow \frac{3\alpha_{eq}t}{800} = \frac{\alpha t}{400} + \frac{4\alpha t}{800}$$

$$\Rightarrow \alpha_{eq} = 2\alpha$$

3. (C)

$$i = \frac{Q}{T} = \frac{Q}{\left(\frac{2\pi}{\omega}\right)} = \frac{Q\omega}{2\pi}$$

4. (D)




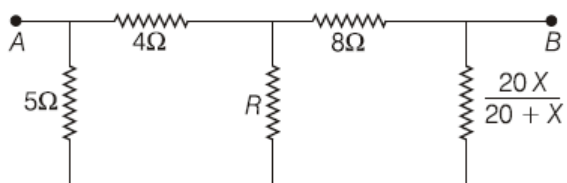


For equivalent resistance to be independent of R , it should be a balanced Wheatstone bridge.

$$\Rightarrow 4 \left(\frac{20X}{20+X} \right) = 8 \times 5$$


$$\Rightarrow x = 20 \Omega$$

5. (A)

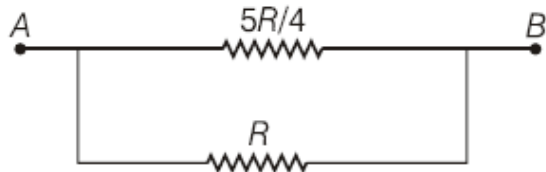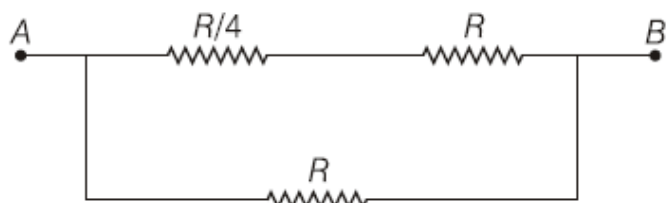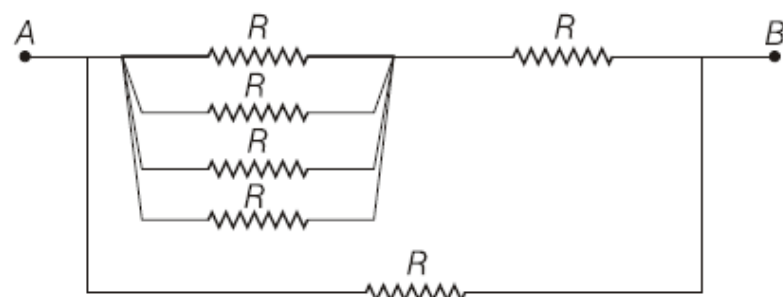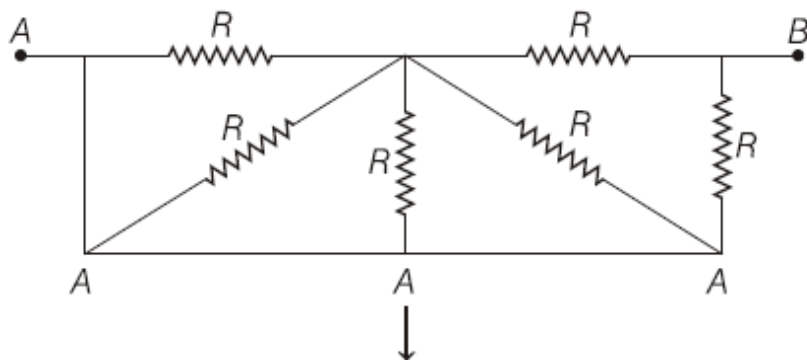

$$\frac{1}{R_{eq}} = \frac{1}{5R} + \frac{1}{R}$$

$$\Rightarrow R_{eq} = \frac{5R}{9}$$

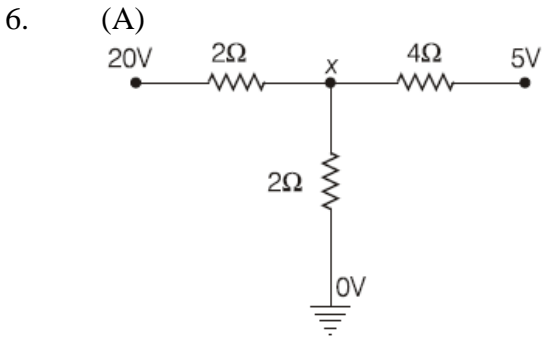

Lets take potential of junction to be x .


Applying KCL at the junction,

$$\frac{20-x}{2} + \frac{5-x}{4} + \frac{0-x}{2} = 0$$

$$\Rightarrow 40 - 2x + 5 - x - 2x = 0$$

$$x = 9 \text{ V}$$
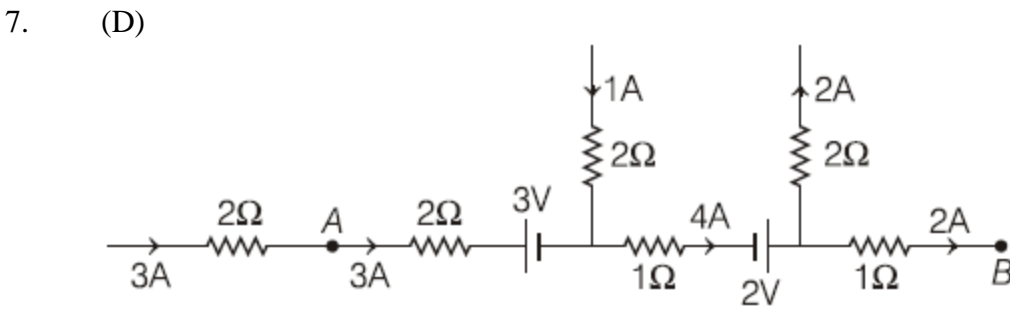
$$\begin{aligned} \text{Current through the switch} &= \frac{x-0}{2} \\ &= \frac{9-0}{2} = 4.5 \text{ A} \end{aligned}$$



$$V_A - 3(2) - 3 - 4(1) + 2 - 2(1) = V_B$$

$$\Rightarrow V_A - V_B = 13 \text{ V}$$

8. (A)
Lets take potential of the junction to be x .


Using KCL at the junction,

$$\frac{10-x}{1} + \frac{10-x}{1} + \frac{10-x}{1} = 9$$


$$\Rightarrow x = 7 \text{ V}$$

$$\frac{x-V_D}{\frac{4}{3}} = 9 \Rightarrow 7 - V_D = 12$$

$$\Rightarrow V_D = -5 \text{ V}$$

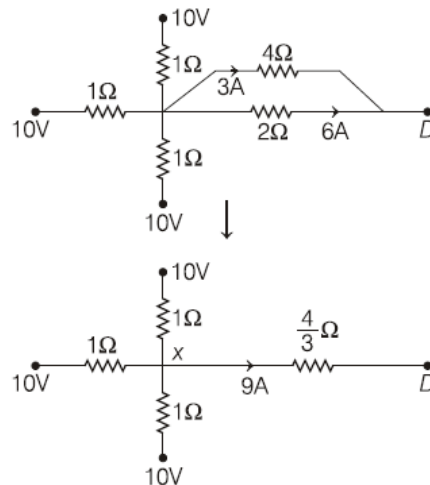


9. (B)

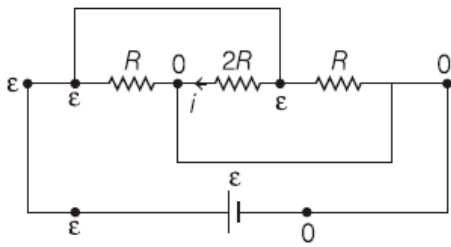


Current in a resistor flows from high potential to low potential. So, current in $2R$ resistance will be from right to left.

10. (B)

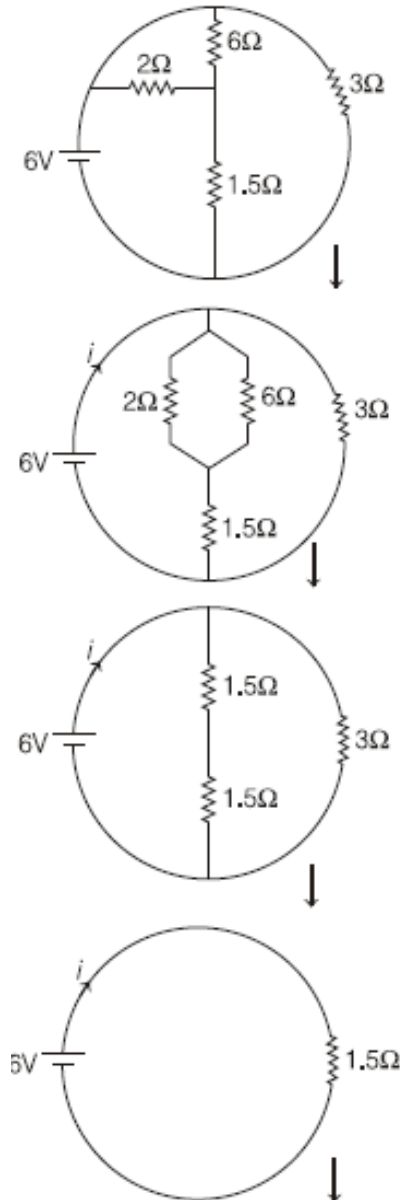

$$i = \frac{6}{1.5} = 4 \text{ A}$$

11. (B)

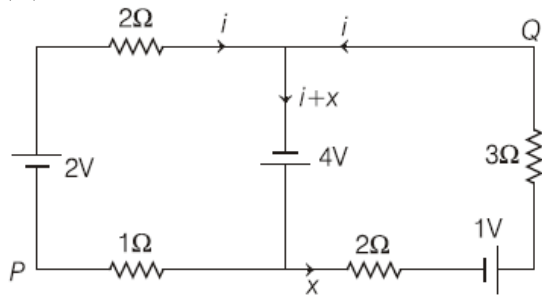

Using KVL,

$$+2 - 2i + 4 - i(1) = 0$$

$$\Rightarrow i = 2 \text{ A}$$


$$+4 - 2x + 1 - 3x = 0$$

$$\Rightarrow x = 1 \text{ A}$$

$$V_P + 2 - i(2) = V_Q$$

$$\Rightarrow V_P - V_Q = 2i - 2 = 2(2) - 2 = 2 \text{ V}$$

12. (B)

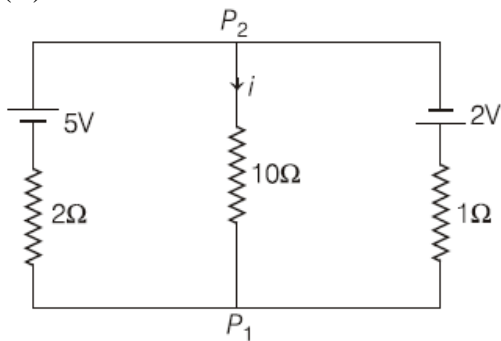


$$\epsilon_{eq} = \frac{\frac{\epsilon_1 + \epsilon_2}{\frac{1}{r_1} + \frac{1}{r_2}}}{\frac{1}{2} + \frac{1}{1}} = \frac{\frac{5 - 2}{\frac{1}{2} + \frac{1}{1}}}{\frac{1}{2} + \frac{1}{1}} = \frac{1}{3} \text{ V}$$

$$r_{eq} = \frac{r_1 r_2}{r_1 + r_2} = \frac{2}{3} \Omega$$

$$i = \frac{\epsilon_{eq}}{R + r_{eq}} = \frac{\frac{1}{3}}{10 + \frac{2}{3}} = \frac{1}{32} \text{ A} = 0.03 \text{ A}$$

13. (D)

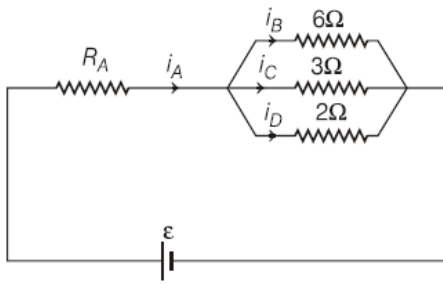


$$i_B : i_C : i_D = \frac{1}{R_B} : \frac{1}{R_C} : \frac{1}{R_D}$$

$$= \frac{1}{6} : \frac{1}{3} : \frac{1}{2} = 1 : 2 : 3$$

$$i_A = i_B + i_C + i_D$$

$$\Rightarrow i_A : i_B : i_C : i_D = 6 : 1 : 2 : 3$$


14. (B)

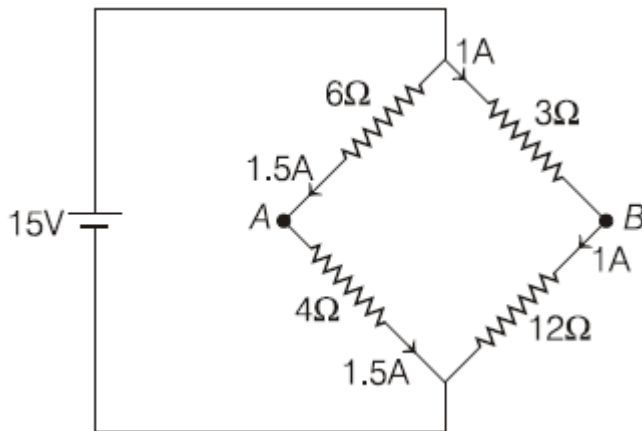

$$V_A - 1.5(4) + 1(12) = V_B$$

$$V_A - V_B = -6 \text{ V}$$


15. (C)

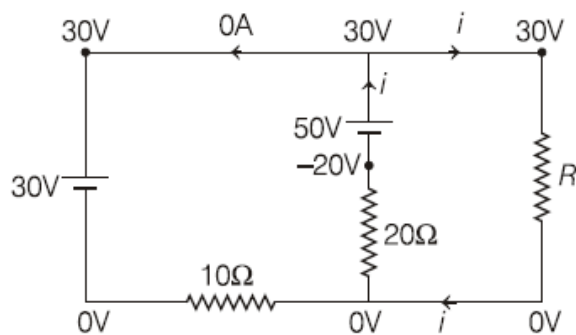

$$i = \frac{0 - (-20)}{20} = \frac{30 - 0}{R}$$

$$\Rightarrow R = 30\Omega$$

16. (D)

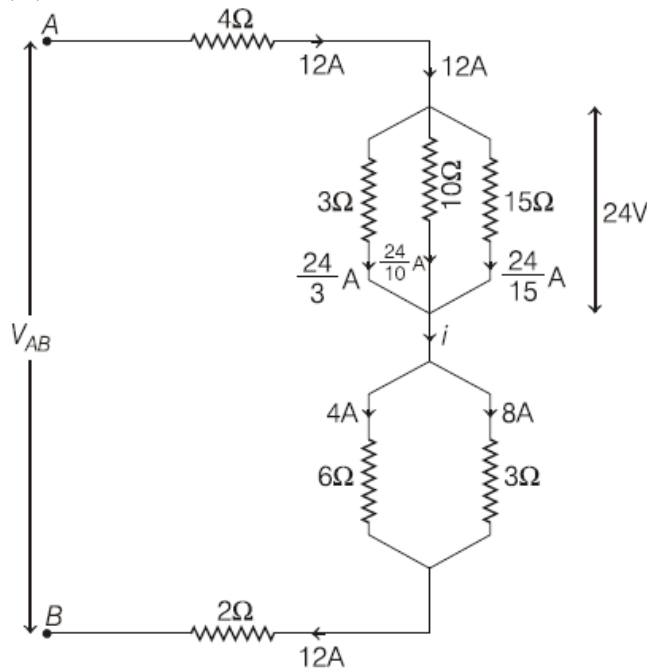


$$i = \frac{24}{15} + \frac{24}{10} + \frac{24}{3} = 12 \text{ A}$$

$$V_{AB} = 12(4) + 24 + 8(3) + 12(2) = 120 \text{ V}$$

$$\text{Current through } 6\Omega \text{ resistor} = \frac{3}{3+6}(12) = 4 \text{ A}$$

17. (C)

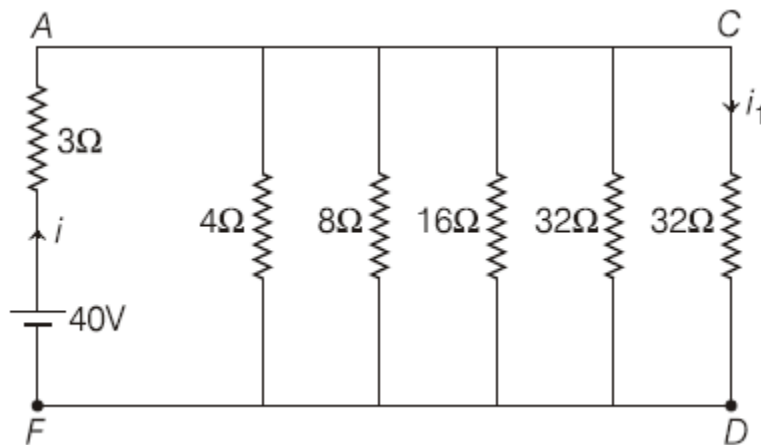

$$R_{eq} = 3 + \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{32} \right)^{-1} = 3 + 2 = 5 \Omega$$


$$i = \text{Current through battery} = \frac{40}{5} = 8 \text{ A}$$

$$i_1 = \left(\frac{\frac{1}{32}}{\frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{32}} \right) (8)$$

$$i_1 = \frac{1}{2}$$

$$\frac{i_1}{i} = \frac{1/2}{8} = \frac{1}{16}$$

18. (A)

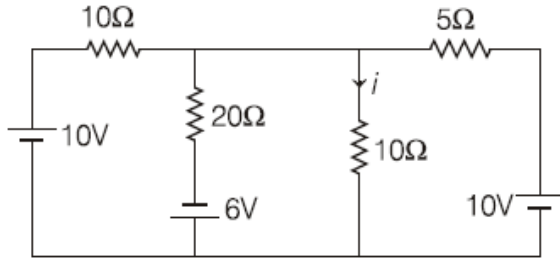

$$\begin{aligned} \varepsilon_{\text{eq}} &= \frac{\frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2} + \frac{\varepsilon_3}{r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}} \\ &= \frac{\frac{10}{10} - \frac{6}{20} + \frac{10}{5}}{\frac{1}{10} + \frac{1}{20} + \frac{1}{5}} = \frac{54}{7} \text{ V} \end{aligned}$$


$$\begin{aligned} i &= \frac{\varepsilon_{\text{eq}}}{R + r_{\text{eq}}} = \frac{\frac{54}{7}}{10 + \frac{20}{7}} \\ &= \frac{54}{90} = \frac{3}{5} = 0.6 \text{ A} \end{aligned}$$

19. (D)

Resistance of an ideal voltmeter is infinite.

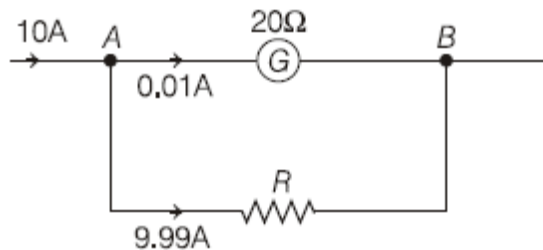20. (B)


Full scale deflection current $= i_g = \frac{0.2}{20} = 0.01 \text{ A}$



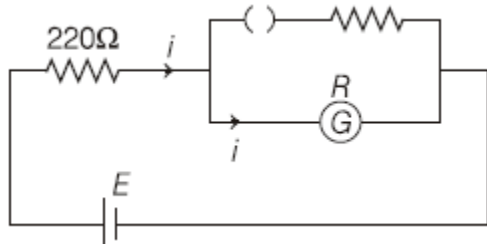21. (D)

For galvanometer, $i \propto \theta$


If deflection becomes $\left(\frac{1}{5}\right)$ th, then current through galvanometer will also become $\left(\frac{1}{5}\right)$ th.



When K_1 is closed and K_2 is open, let current through the galvanometer be i .

Let R be resistance of the galvanometer.

$$\Rightarrow i = \frac{E}{220 + R}$$

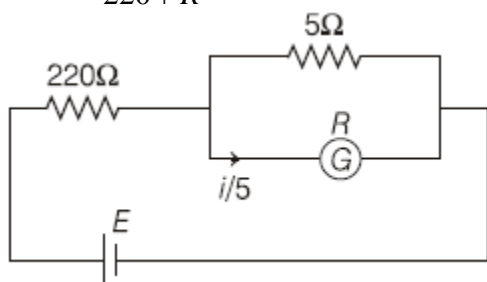

When K_2 is also closed, current through the galvanometer becomes $\frac{i}{5}$.

$$\frac{i}{5} = \left(\frac{E}{220 + \frac{5R}{5+R}} \right) \left(\frac{5}{5+R} \right)$$

$$\Rightarrow \frac{1}{5} \left(\frac{E}{220 + R} \right) = \left(\frac{E}{220 + \frac{5R}{5+R}} \right) \left(\frac{5}{5+R} \right)$$

$$\Rightarrow R = 22 \Omega$$

22. (D)

$$V = i_g (R_G + R)$$


$$\Rightarrow 20 = i_g (R_G + 1680) \quad \dots(i)$$

$$\Rightarrow 30 = i_g (R_G + 2930) \quad \dots(ii)$$

Solving Eqs. (i) and (ii), we get

$$R_G = 820 \Omega \text{ and } i_g = 8 \text{ mA}$$

23. (B)

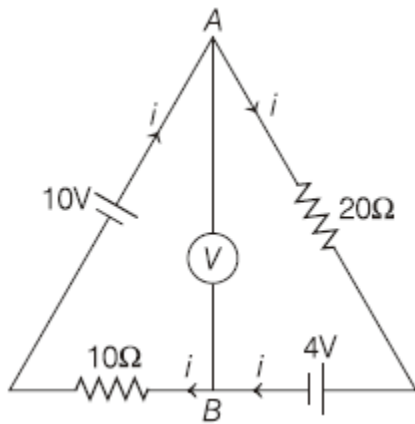

Ideal voltmeter has infinite resistance, so current through voltmeter is nearly zero.

Applying KVL in the loop,


$$+10 - 20i - 4 - 10i = 0$$

$$\Rightarrow i = 0.2 \text{ A}$$

$$V_A - 20(0.2) - 1 = V_B$$

$$V_A - V_B = 8 \text{ V}$$

24. (A)

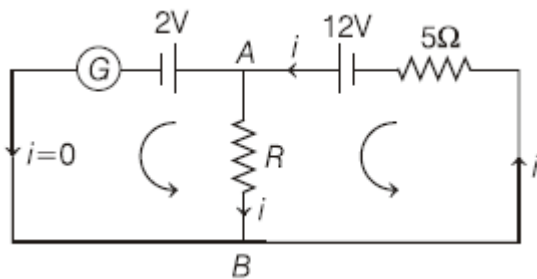

Applying KVL,


$$+12 - iR - 5i = 0$$

$$i = \frac{12}{R+5}$$

$$V_A - 2 = V_B \Rightarrow V_A - V_B = 2$$

$$\Rightarrow \left(\frac{12}{R+5} \right) R = 2 \Rightarrow R = 1 \Omega$$

25. (A)

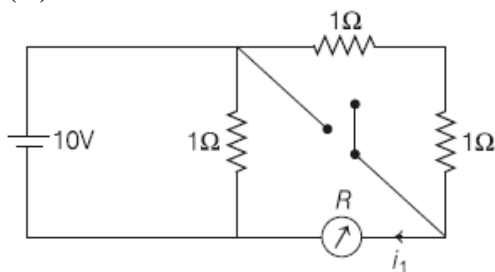


Let the resistance of the ammeter be R .

When the switch is open,

$$\text{Reading of ammeter} = i_1 = \frac{10}{R+2}$$

When the switch is closed.

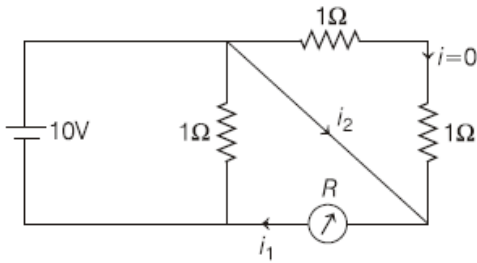


$$i_2 = \frac{10}{R}$$

$$i_2 = 2i_1$$

$$\Rightarrow \frac{10}{R} = 2 \left(\frac{10}{R+2} \right)$$

$$\Rightarrow R = 2\Omega$$

26. (C)

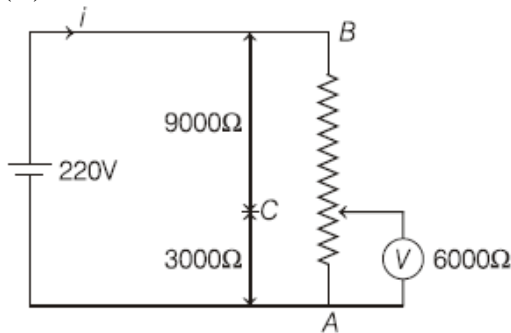

$$R_{CA} = \frac{1}{4}(12000) = 3000\Omega$$

$$R_{BC} = \frac{3}{4}(12000) = 9000\Omega$$

$$i = \frac{220}{900 + \frac{6000 \times 3000}{6000 + 3000}} = 0.02\text{ A}$$

$$\text{Reading voltmeter} = (0.02) \left(\frac{6000 \times 3000}{6000 + 3000} \right) = 40\text{ V}$$

27. (A)

From the graph,

When $G \rightarrow \infty$, $V = 20\text{ V}$

Potential difference across resistor when $G \rightarrow \infty$

$$= \left(\frac{24}{R+1} \right) R = 20$$

$$\Rightarrow 6R = 5R + 5$$

$$\Rightarrow R = 5\Omega$$

28. (B)

For balanced Wheatstone bridge,

$$6(625) = QS$$

$$\Rightarrow \frac{P}{Q} = \frac{S}{625} \quad \dots(i)$$

After interchanging P and Q , condition for the balanced Wheatstone bridge,

$$Q(625+51) = PS$$

$$\Rightarrow \frac{P}{Q} = \frac{676}{S} \quad \dots(ii)$$

From Eqs. (i) and (ii), we get

$$\frac{S}{625} = \frac{676}{S}$$

$$\Rightarrow S = \sqrt{625 \times 676} = 25 \times 26 = 650 \Omega$$

29. (5)

$$R = \frac{\rho l}{A}$$

$$R' = \frac{\rho(1 + \alpha_1 \Delta T) / (1 + \alpha_2 \Delta T)}{A(1 + 2\alpha_1 \Delta T)}$$


$$R' = \frac{\rho l}{A} (1 + \alpha_1 \Delta T)(1 - \alpha_2 \Delta T)$$



$$R' = R(1 + (\alpha_1 - \alpha_2) \Delta T)$$

Temperature coefficient of resistance = $\alpha_1 - \alpha_2$

$$= 6 \times 10^{-3} - 1 \times 10^{-3} = 5 \times 10^{-3}$$

30. (5)


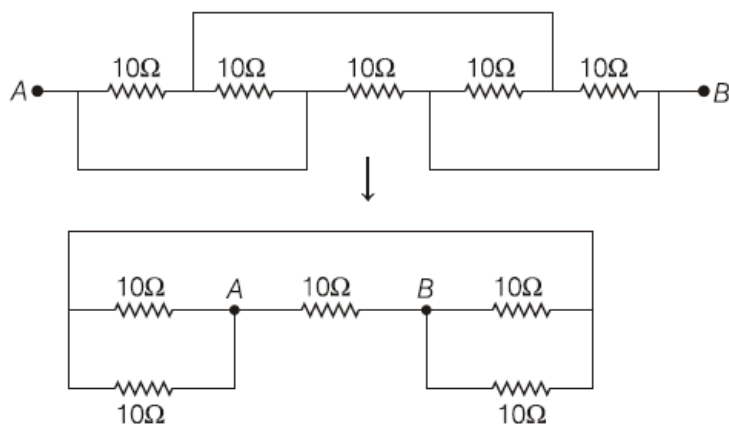


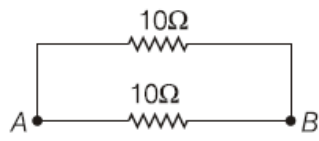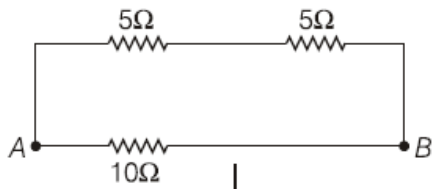


$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{10} \Rightarrow R_{eq} = 5 \Omega$$

31.

(4)

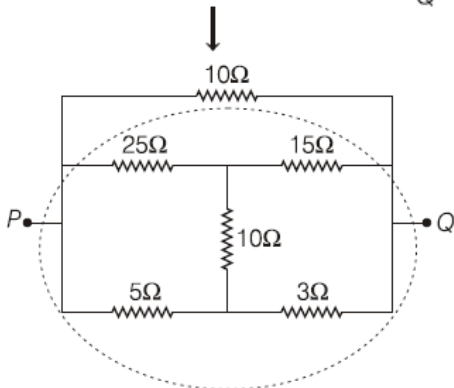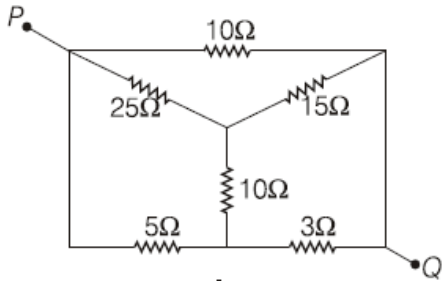


Balanced Wheatstone bridge

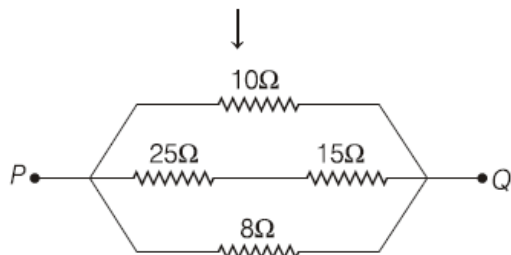

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{40} + \frac{1}{8}$$

$$\Rightarrow R_{eq} = 4 \Omega$$

32. (9)

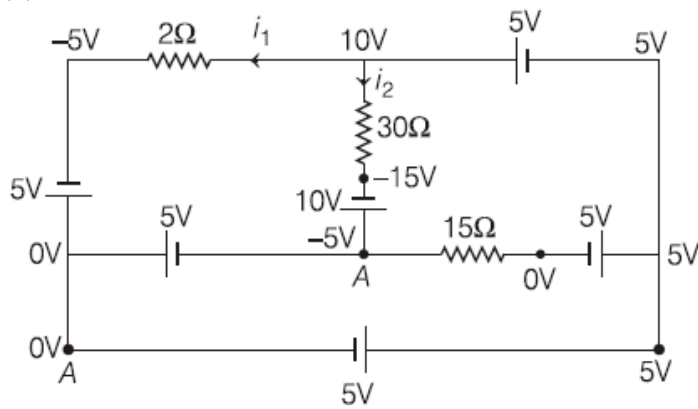


Lets take $V_A = 0 \text{ V}$

$$i_1 = \frac{10 - (-5)}{2} = 7.5 \text{ A}$$

$$i_2 = \frac{10 - (-15)}{30} = \frac{5}{6} \text{ A}$$

$$\frac{i_1}{i_2} = \frac{\frac{15}{2}}{\frac{5}{6}} = 9$$

33. (5)

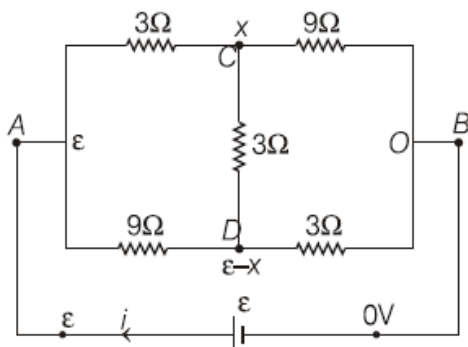

Due to cross-symmetry, current through both 3Ω resistances will be same. So, potential difference across both 3Ω resistances will be also same.

Applying KCL at junction C,

$$\frac{\varepsilon - x}{3} + \frac{0 - x}{9} + \frac{(\varepsilon - x) - x}{3} = 0$$


$$\Rightarrow 3\varepsilon - 3x - x + 3\varepsilon - 6x = 0$$

$$\Rightarrow x = \frac{3\varepsilon}{5}$$


$$i = \frac{\varepsilon - x}{3} + \frac{\varepsilon - (\varepsilon - x)}{9} = \frac{2\varepsilon}{15} + \frac{\varepsilon}{15} = \frac{\varepsilon}{5}$$

$$R_{\text{eq}} = \frac{\varepsilon}{i} = 5 \Omega$$

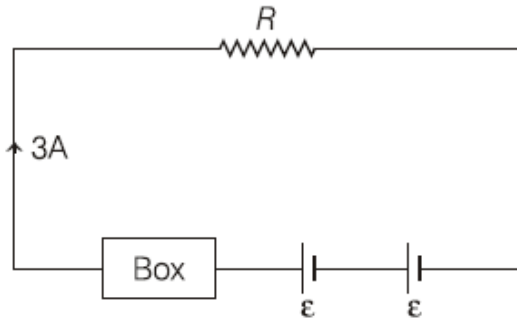34. (1)
 Lets take number of cells wrongly connected in the box to be n .
 Equivalent emf of the box $= (12 - n)\epsilon - n\epsilon = (12 - 2n)\epsilon$



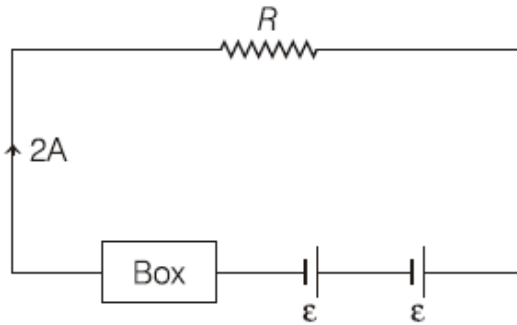
$$3 = \frac{(12 - 2n)\epsilon + 2\epsilon}{R} \quad \dots(i)$$



$$2 = \frac{(12 - 2n)\epsilon - 2\epsilon}{R} \quad \dots(ii)$$

Solving Eqs. (i) and (ii), we get
 $n = 1$

35. (6)

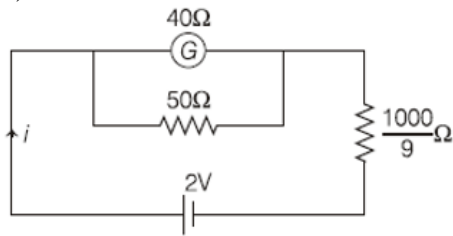


$$\begin{aligned} \text{Current through galvanometer} &= \left(\frac{50}{50 + 40} \right) \times (15 \text{ mA}) \\ &= \frac{25}{3} \text{ mA} \end{aligned}$$

$$\text{Current sensitivity} = \frac{50}{\frac{25}{3}} = 6 \text{ div/mA}$$

$$\begin{aligned} i &= \frac{2}{\frac{1000}{9} + \left(\frac{40 \times 50}{40 + 50} \right)} \\ &= 158 \times 10^{-3} \text{ A} \\ &= 15 \text{ mA} \end{aligned}$$

36. (2)

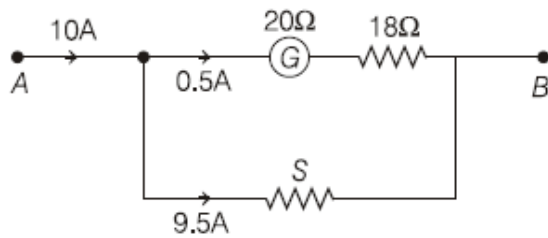


For half scale deflection, current through the galvanometer = 0.5 A

$$V_A - V_B = 0.5(20 + 18) = 9.5(S)$$

$$\Rightarrow S = 2\Omega$$

37. (30)

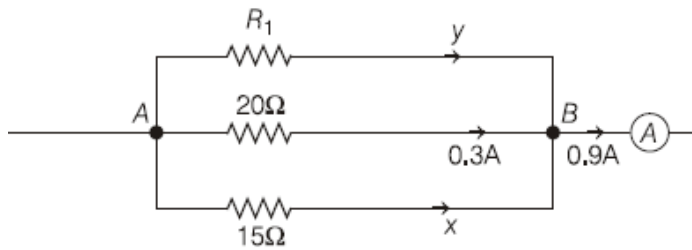


$$V_A - V_B = 20(0.3) = x(15) \Rightarrow x = 0.4 \text{ A}$$

$$x + y + 0.3 = 0.9 \Rightarrow y = 0.2 \text{ A}$$

$$V_A - V_B = 20 = (0.2)R_1$$

$$\Rightarrow R_1 = 30\Omega$$

38. (7)

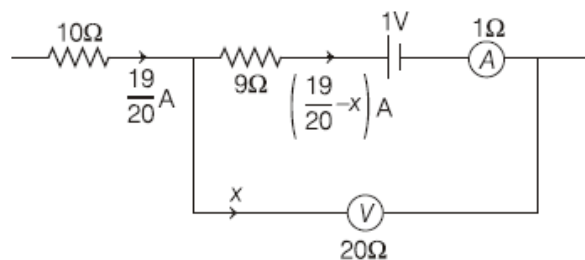


Using KVL in the loop,

$$-9\left(\frac{19}{20} - x\right) - 1 - 1\left(\frac{19}{20} - x\right) + 20x = 0$$

$$\Rightarrow x = 0.35 \text{ A}$$

$$\text{Reading of voltmeter} = x(20) = 0.35 \times 20 = 7 \text{ V}$$


39. (6600)

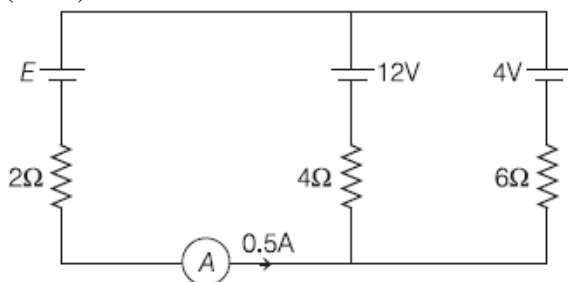

$$\epsilon_{\text{eq}} = \frac{\frac{12}{4} + \frac{4}{6}}{\frac{1}{4} + \frac{1}{6}} = \frac{44}{5} \text{ V}$$

$$\frac{1}{r_{\text{eq}}} = \frac{1}{4} + \frac{1}{6}$$
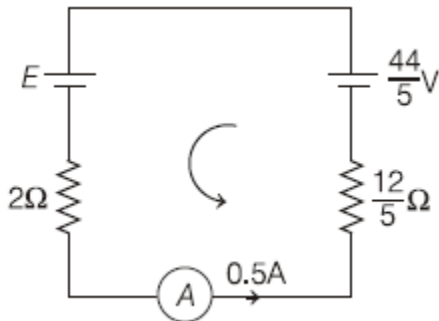
$$\Rightarrow r_{\text{eq}} = \frac{12}{5} \Omega$$




Applying KVL in the loop,

$$+\frac{44}{5} - E - 2(0.5) - \frac{12}{5}(0.5) = 0$$

$$\Rightarrow E = 6.6 \text{ V} = 6600 \text{ mV}$$

40. (80)

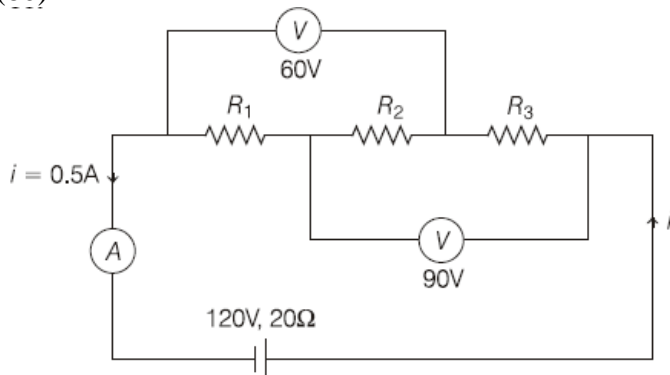

$$i(R_1 + R_2) = 60$$

$$\Rightarrow 0.5(R_1 + R_2) = 60$$

$$\Rightarrow R_1 + R_2 = 120 \Omega \quad \dots(\text{i})$$

$$i(R_2 + R_3) = 90$$

$$\Rightarrow 0.5(R_2 + R_3) = 90$$

$$\Rightarrow R_2 + R_3 = 180 \Omega \quad \dots(\text{ii})$$

$$i = \frac{120}{R_1 + R_2 + R_3 + 20} = 0.5$$

$$\Rightarrow R_1 + R_2 + R_3 = 220 \quad \dots(\text{iii})$$

Solving Eqs. (i), (ii) and (iii), we get

$$R_2 = 80 \Omega$$

41. (3)
Let balance length be l and unknown resistance be R .

For null point,

$$2(100 - l) = R(l) \quad \dots(i)$$

When 2Ω and R are interchanged, balance point shifts by 20 cm.

So, for null point,


$$R(100 - (l + 20)) = 2(l + 20)$$

$$\Rightarrow R(80 - l) = 2(l + 20) \quad \dots(ii)$$

Solving Eqs. (i) and (ii), we get

$$l = 40 \text{ cm and } R = 3\Omega$$

42. (3)

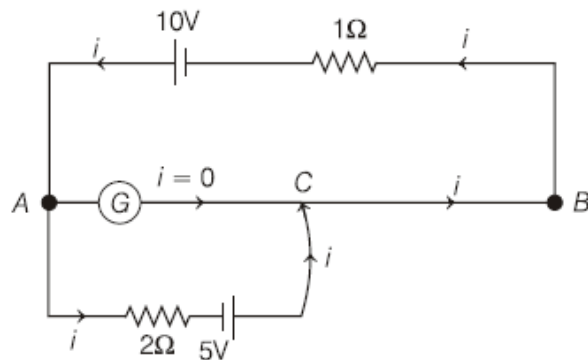

Applying KVL,

$$-i + 10 - 2i + 5 - iR_{BC} = 0$$

$$\Rightarrow i = \frac{15}{3 + R_{BC}}$$

$$V_A - V_C = 5 - 2i = 0$$

$$\Rightarrow i = 2.5 \text{ A}$$

$$2.5 = \frac{15}{3 + R_{BC}}$$

$$\Rightarrow R_{BC} = 3\Omega$$

43. (0.2)

$$\text{Current in the primary circuit} = \frac{3}{10 + 20} = 0.1 \text{ A}$$

$$\begin{aligned} \text{Potential drop across the potentiometer wire} \\ = 0.1 \times 20 = 2 \text{ V} \end{aligned}$$

$$x = \text{potential gradient} = \frac{2}{10} = 0.2 \text{ V/m} = 0.2 \text{ mV/mm}$$

For balance point,

$$V = xI$$

$$\Delta V = x\Delta l = \left(0.2 \frac{\text{mV}}{\text{mm}}\right)(1 \text{ mm}) = 0.2 \text{ mV}$$

1. (A)
In electric circuit ammeter is connected in series with resistance and voltmeter parallel with the net resistance.
In ohm's law, we check $V = IR$ by varying net resistance of the circuit.

2. (B)

(b) Resistance between P and Q

$$r_{PQ} = r \parallel \left(\frac{r}{3} + \frac{r}{2} \right) = \frac{r \times \frac{5}{6}r}{r + \frac{5}{6}r} = \frac{5}{11}r$$

Resistance between Q and R

$$r_{QR} = \frac{r}{2} \parallel \left(r + \frac{r}{3} \right) = \frac{\frac{r}{2} \times \frac{4}{3}r}{\frac{r}{2} + \frac{4}{3}r} = \frac{4}{11}r$$

Resistance between P and R

$$r_{PR} = \frac{r}{3} \parallel \left(\frac{r}{2} + r \right) = \frac{\frac{r}{3} \times \frac{3}{2}r}{\frac{r}{3} + \frac{3}{2}r} = \frac{3}{11}r$$

Hence, it is clear that r_{PQ} is maximum.

3. (C)


(c) As 200 V battery is charging

$$\text{So, } 220 = 200 + i \cdot 1$$

$$i = 20 \text{ A}$$

$$\text{So, } 20 \times R = 220 \text{ V}$$

$$\Rightarrow R = 11 \Omega$$

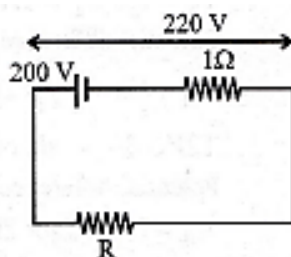


4. (C)

$$(c) \frac{100}{R+r} = \frac{90}{R} \Rightarrow \frac{R+r}{R} = \frac{10}{9} \Rightarrow 1 + \frac{0.5}{R} = \frac{10}{9}$$

$$\Rightarrow \frac{0.5}{R} = \frac{1}{9} \therefore R = 4.5 \Omega$$

5. (D)

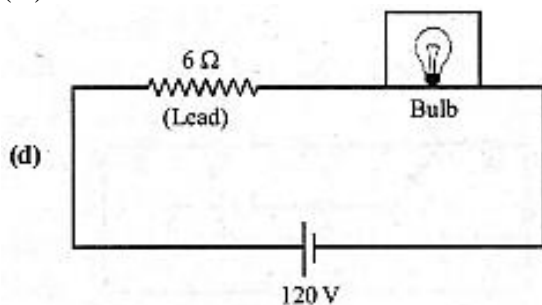

Power of bulb = 60 W (given)

$$\text{Resistance of bulb} = \frac{120 \times 120}{60} = 240 \Omega \quad \left[\because P = \frac{V^2}{R} \right]$$

Power of heater = 240 W (given)

$$\text{Resistance of heater} = \frac{120 \times 120}{240} = 60 \Omega$$

Voltage across bulb before heater is switched on,

$$V_1 = \frac{240}{246} \times 120 = 117.73 \text{ volt}$$

Voltage across bulb after heater is switched on,

$$V_2 = \frac{48}{54} \times 120 = 106.66 \text{ volt}$$

Hence decrease in voltage

$$V_1 - V_2 = 117.073 - 106.66 = 10.04 \text{ Volt (approximately)}$$

6. (C)

(c) Total power consumed by electrical appliances in the building, $P_{\text{total}} = 2500 \text{ W}$

Watt = Volt \times ampere

$$\Rightarrow 2500 = V \times I \Rightarrow 2500 = 220 I$$

$$\Rightarrow I = \frac{2500}{220} = 11.36 \approx 12 \text{ A}$$

(Minimum capacity of main fuse)

7. (C)

(c) Current in each bulb = $\frac{\text{Power}}{\text{Voltage}} = \frac{100}{220} = 0.45 \text{ A}$

Current through ammeter = $0.45 \times 3 = 1.35 \text{ A}$

8. (B)

$$(b) \quad V = IR = (neAv_d)\rho \frac{\ell}{A} \quad \therefore \rho = \frac{VA}{n_eAV_d\ell} = \frac{V}{n_eV_d\ell}$$

Here V = potential difference

ℓ = length of wire

n = no. of electrons per unit volume of conductor.

e = no. of electrons

Placing the value of above parameters we get resistivity

$$\rho = \frac{5}{8 \times 10^{28} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-4} \times 0.1} = 1.6 \times 10^{-5} \Omega m$$

9. (C)


$$(c) \quad i = neAV_d \text{ and } V_d \propto \sqrt{E} \text{ (Given)}$$

$$\text{or, } i \propto \sqrt{E} \text{ or, } i^2 \propto E \text{ or, } i^2 \propto V$$

Hence graph (c) correctly depicts the V - I graph for a wire made of such type of material.

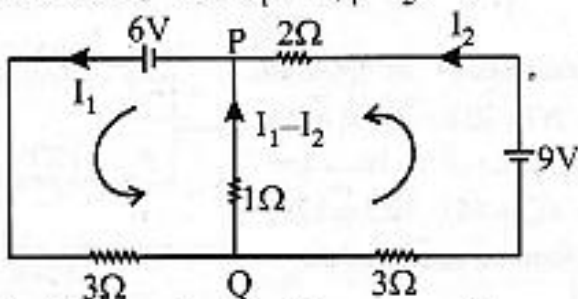10. (A)

$$(a) \text{ From KVL, } -6 + 3I_1 + 1(I_1 - I_2) = 0$$



$$6 = 3I_1 + I_1 - I_2; \quad 4I_1 - I_2 = 6 \quad \dots(i)$$

$$-9 + 2I_2 - (I_1 - I_2) + 3I_2 = 0$$

$$-I_1 + 6I_2 = 9 \quad \dots(ii)$$

On solving (i) and (ii)

$$I_1 = 0.13A$$

Direction Q to P, since $I_1 > I_2$.

11. (C)

$$(c) \quad i = \frac{V}{R + \frac{Rr}{R+r}} \times \left(\frac{R}{R+r} \right) = \frac{V}{R+2r}$$

$$\text{So, } P = i^2 R = \frac{V^2 R}{(R+2r)^2}$$

for H_{\max} , P is maximum

$$\frac{dp}{dr} = 0 \Rightarrow \frac{(R+2r)^2 - 2(R+2r) \cdot 2r}{(R+2r)^4} = 0$$

$$\Rightarrow (R+2r)(R+2r-4r) = 0$$

$$\Rightarrow r = -\frac{R}{2} \text{ or } r = \frac{R}{2} \Rightarrow r = \frac{R}{2} \text{ so, } f = \frac{1}{2}$$

12. (A)

Given $R_1 = 100\Omega$, $r' = r/2$, $R_2 = ?$

Resistivity of wire, $R = \frac{\rho l}{A} \because \text{Area} \times \text{lenght} = \text{volume}$

$$\text{Hence, } R = \frac{\rho V}{A^2}$$

Since, $\rho \rightarrow \text{constant}$, $V \rightarrow \text{constant}$

$$R \propto \frac{1}{A^2} \text{ OR } R \propto \frac{1}{r^4} \because A = \pi r^2$$

$$\frac{R_2}{R_1} = 16 \Rightarrow R_2 = 16 \times 100 = 1600\Omega, \text{ Resistance of new wire.}$$

13. (A)

(a) In steady state, flow of current through capacitor will be zero.


Current through the circuit,

$$i = \frac{E}{r+r_2}$$

Potential difference through capacitor

$$V_c = \frac{Q}{C} = E - ir = E - \left(\frac{E}{r+r_2} \right) r$$

$$\therefore Q = CE \frac{r_2}{r+r_2}$$

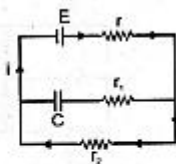

14. (B)

The potential difference in each loop is zero.

\therefore No current will flow or current in each resistance is zero

15. (D)


(d) There is no change in null point, if the cell and the galvanometer are exchanged in a balanced wheatstone bridge.

On balancing condition $\frac{R_1}{R_3} = \frac{R_2}{R_4}$

After exchange


On balancing condition

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

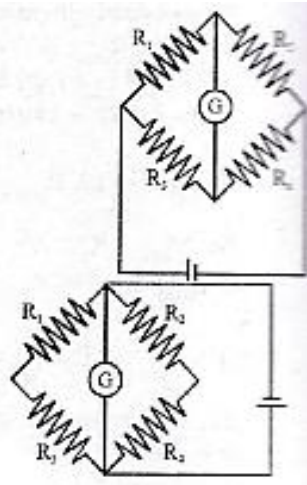

16. (A)

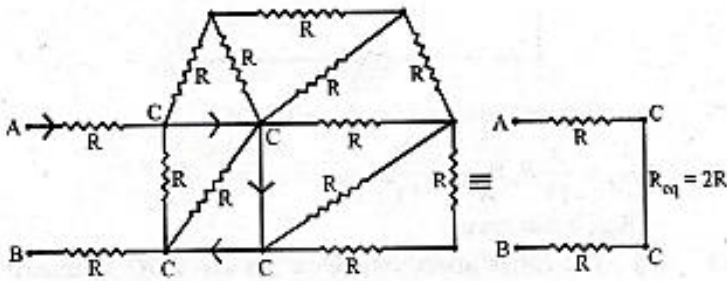(a) Current will follow the path ACCCCB so we will get our final circuit as shown below



17. (B)

(b) Using Kirchhoff's law at P we get


$$\frac{V-12}{1} + \frac{V-13}{2} + \frac{V-0}{10} = 0$$

[Let potential at P, Q, U = 0
and at R = V]

$$\Rightarrow \frac{V}{1} + \frac{V}{2} + \frac{V}{10} = \frac{12}{1} + \frac{13}{2} + \frac{0}{10}$$

$$\Rightarrow \frac{10+5+1}{10}V = \frac{24+13}{2} \Rightarrow V \left(\frac{16}{10} \right) = \frac{37}{2}$$
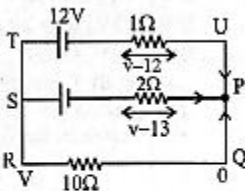
$$\Rightarrow V = \frac{37 \times 10}{16 \times 2} = \frac{370}{32} = 11.56 \text{ volt}$$



18. (A)

(a) Rate of heat i.e., Power developed in the wire

$$P = \frac{V^2}{R}$$

Resistance of the wire of length, L $R_1 = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2}$

\therefore Power, $P_1 = \frac{V^2}{R_1}$

Resistance of the wire when length is halved i.e., $L/2$

$$R_2 = \frac{\rho \frac{L}{2}}{\pi (2r)^2} = \frac{\rho L}{\pi 8r^2} = \frac{R_1}{8}$$

\therefore Power, $P_2 = \frac{V^2}{\frac{R_1}{8}} = \frac{8V^2}{R_1}$ or, $P_2 = 8P_1$

i.e., power increased 8 times of previous or original wire.

19. (B)

Using formula, internet resistance,

$$r = \left(\frac{l_1 - l_2}{l_2} \right) s = \left(\frac{52 - 40}{40} \right) \times 5 = 1.5 \Omega$$

20. (C)

(c) $R_1 + R_2 = 1000$

$\Rightarrow R_2 = 1000 - R_1$

On balancing condition

$R_1(100 - l) = (1000 - R_1)l$... (i)

On Interchanging resistance balance point shifts left by 10 cm.

On balancing condition

$(1000 - R_1)(110 - l) = R_1(l - 10)$

or, $R_1(l - 10) = (1000 - R_1)(110 - l)$... (ii)

Dividing eqn (i) by (ii)

$$\frac{100 - l}{l - 10} = \frac{l}{110 - l}$$

$\Rightarrow (100 - l)(110 - l) = l(l - 10)$

$\Rightarrow 11000 - 100l - 110l + l^2 = l^2 - 10l$



$\Rightarrow 11000 = 200l$ or, $l = 55$

Putting the value of 'l' in eqn (i)

$R_1(100 - 55) = (1000 - R_1)55 \Rightarrow R_1(45) = (1000 - R_1)55$

$\Rightarrow R_1(9) = (1000 - R_1)11 \Rightarrow 20R_1 = 11000$

$\therefore R_1 = 550 \text{K}\Omega$

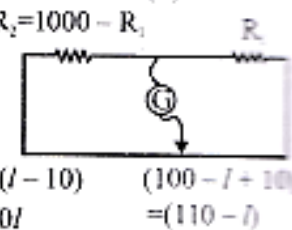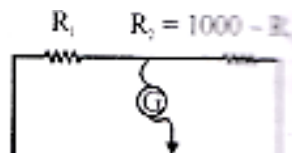

21. (D)

(d) Charge mobility

$$(\mu) = \frac{V_d}{E} \quad [\text{Where } V_d = \text{drift velocity}]$$

$$\text{and resistivity } (\rho) = \frac{E}{j} = \frac{EA}{I} \Rightarrow E = \frac{I(\rho)}{A}$$

$$\Rightarrow \mu = \frac{V_d}{E} = \frac{V_d A}{I \rho} = \frac{1.1 \times 10^{-3} \times \pi \times (5 \times 10^{-3})^2}{5 \times 1.7 \times 10^{-8}}$$

$$\Rightarrow \mu = 1.0 \frac{\text{m}^2}{\text{Vs}}$$

22. (B)

(b) Equation of straight line from graph

$$y = -mx + c$$

$$\Rightarrow \ln R = -m \left(\frac{1}{T^2} \right) + c$$

here, m & c are constants


$$R = e^{-m \left(\frac{1}{T^2} \right) + c} = e^{-m \left(\frac{1}{T^2} \right)} \times e^c \Rightarrow R(T) = R_0 e^{\frac{-T_d^2}{T^2}}$$

23. (A)

$$(a) \quad dR = \frac{(\rho)(dx)}{4\pi x^2}$$

$$R = \int dR$$
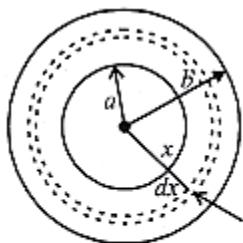
$$\int dR = \rho \int_a^b \frac{dx}{4\pi x^2}$$



$$\Rightarrow R = \frac{\rho}{4\pi} \left[\frac{-1}{x} \right]_a^b \Rightarrow R = \left(\frac{\rho}{4\pi} \right) \cdot \left(\frac{1}{a} - \frac{1}{b} \right)$$

24. (C)

25. (A)

Clearly, from graph

$$\text{Current, } I = \frac{dq}{dt} = 0 \text{ at } t = 4\text{s} \quad [\text{Since } q \text{ is constant}]$$

26. (A)

Using, $I = neAv_d$

$$\therefore \text{Drift speed } v_d = \frac{1}{neA}$$


$$= \frac{1.5}{9 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-6}} = 0.02 \text{ mms}^{-1}$$

27. (C) (c) When length becomes double its resistance becomes

$$(R \propto l^2)$$


$$R = 4 \times 3 = 12 \Omega$$
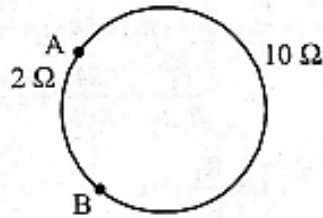
$$R_{\text{eq}} = \frac{2 \times 10}{12} = \frac{5}{3} \Omega$$



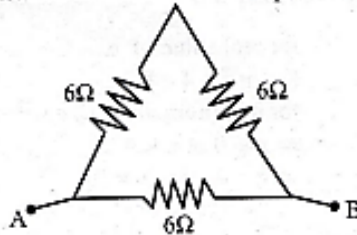28. (A) (a) Resistance, $R \propto l$ so resistance of each side of the equilateral triangle = 6Ω

Resistance R_{eq} between any two vertices



$$\frac{1}{R_{\text{eq}}} = \frac{1}{12} + \frac{1}{6} \Rightarrow R_{\text{eq}} = 4 \Omega$$

29. (D)


$$(d) \quad i = \left(\frac{\varepsilon}{R+r} \right)$$

Power delivered to R.

$$P = i^2 R = \left(\frac{\varepsilon}{R+r} \right)^2 R$$


$$P \text{ to be maximum, } \frac{dP}{dR} = 0$$
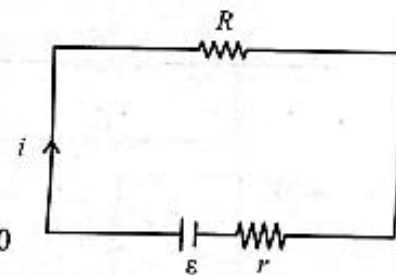
$$\text{or } \frac{d}{dR} \left[\left(\frac{\varepsilon}{R+r} \right)^2 R \right] = 0 \quad \text{or } R = r$$



30. (B)

(b)

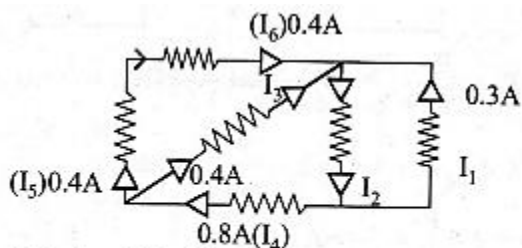

From KCL, $I_3 = 0.8 - 0.4 = 0.4 \text{ A}$

$$I_2 = 0.4 + 0.4 + 0.3 = 1.1 \text{ A}$$

$$\text{and } I_6 = 0.4 \text{ A}$$

31. (A)

(a) As $R = \frac{V^2}{P}$, so $R_1 = \frac{220^2}{25}$ and $R_2 = \frac{220^2}{100}$

Current flow $i = \frac{220}{R_1 + R_2}$

$$P_1 = i^2 R_1 = \frac{220^2}{\left(\frac{220^2}{25} + \frac{220^2}{100}\right)} \times \frac{220^2}{25} = 16 \text{ W}$$

Similarly, $P_2 = i^2 R_2 = 4 \text{ W}$

32. (B)

(b) When two resistances are connected in series,
 $R_{eq} = 2R$

Power consumed, $P = \frac{\epsilon^2}{R_{eq}} = \frac{\epsilon^2}{2R}$

In parallel condition, $R_{eq} = R/2$.

New power, $P' = \frac{\epsilon^2}{(R/2)}$

or $P' = 4P = 240 \text{ W} (\because P = 60 \text{ W})$

33. (A)

(a) Colour code for carbon resistor

Bl, Br, R, O, Y, G, Blue, V, Gr, W
0 1 2 3 4 5 6 7 8 9

Resistance, $R = AB \times C \pm D$

\therefore Resistance, $R = 50 \times 10^2 \Omega$

Now using formula, Power, $P = i^2 R$

$$\therefore i = \sqrt{\frac{P}{R}} = \sqrt{\frac{2}{50 \times 10^2}} = 20 \text{ mA}$$

34. (A)

(a) Power, $P = i^2 R$

$4.4 = 4 \times 10^{-6} \times R \Rightarrow R = 1.1 \times 10^6 \Omega$

When supply of 11 v is connected

$$\text{Power, } P' = \frac{v^2}{R} = \frac{11^2}{1.1} \times \frac{11^2}{1.1} \times 10^{-6} = 11 \times 10^{-5} \text{ W}$$

35. (C)

(c) We have given

$$\frac{dR}{d\ell} \propto \frac{1}{\sqrt{\ell}} \Rightarrow \frac{dR}{d\ell} = k \times \frac{1}{\sqrt{\ell}} \quad (\text{where } k \text{ is constant})$$

$$dR = k \frac{d\ell}{\sqrt{\ell}}$$

Let R_1 and R_2 be the resistance of AP and PB respectively.
Using wheatstone bridge principle

$$\therefore \frac{R'}{R'} = \frac{R_1}{R_2} \text{ or } R_1 = R_2$$

$$\text{Now, } \int dR = k \int \frac{d\ell}{\sqrt{\ell}} \quad \therefore R_1 = k \int_0^{\ell} \ell^{-1/2} d\ell = k \cdot 2 \cdot \sqrt{\ell}$$

$$R_2 = k \int_1^{\ell} \ell^{-1/2} d\ell = k \cdot (2 - 2\sqrt{\ell})$$

Putting $R_1 = R_2$

$$k \cdot 2\sqrt{\ell} = k(2 - 2\sqrt{\ell}) \quad \therefore 2\sqrt{\ell} = 1 \Rightarrow \sqrt{\ell} = \frac{1}{2}$$

$$\text{i.e., } \ell = \frac{1}{4} \text{ m} \Rightarrow 0.25 \text{ m}$$

36. (C)

(c) Current flowing through the circuit (I) is given by

$$I = \left(\frac{4}{R+5} \right) \text{ A}$$


$$\text{Resistance of length 10 cm of wire} = 5 \times \frac{10}{100} = 0.5 \Omega$$

According to question,

$$5 \times 10^{-3} = \left(\frac{4}{R+5} \right) \cdot (0.5)$$

$$\therefore \frac{4}{R+5} = 10^{-2} \text{ or } R+5 = 400 \Omega$$

$$\therefore R = 395 \Omega$$

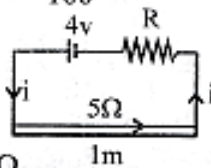

37. (C)

(c) Let x be the length AJ at which galvanometer shows null deflection current,

$$i = \frac{\epsilon}{12r+r} = \frac{3}{13r} \Rightarrow i \left(\frac{x}{L} 12r \right) = \frac{\epsilon}{2}$$

$$\Rightarrow \frac{\epsilon}{13r} \left[\frac{x}{L} 12r \right] = \frac{\epsilon}{2} \Rightarrow \frac{\epsilon}{13r} \left[\frac{x}{L} 12r \right] = \frac{\epsilon}{2} \Rightarrow x = \frac{13L}{24}$$


38. (B)

$$\rho_M = 98 \times 10^{-8}; \rho_A = 2.65 \times 10^{-8}$$

$$\rho_C = 1.724 \times 10^{-8}; \rho_T = 5.65 \times 10^{-8}$$

$$\therefore \rho_M > \rho_T > \rho_A > \rho_C$$

39. (D)

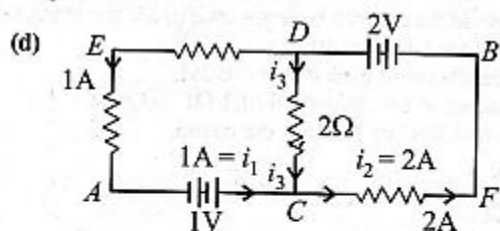

Let us assume the potential at $A = V_A = 0$
Using Kirchoff's junction rule at C , we get

$$i_1 + i_3 = i_2$$

$$1A + i_3 = 2A \Rightarrow i_3 = 2A$$

Now using Kirchoff's loop law along $ACDB$

$$V_A + 1 + i_3(2) - 2 = V_B$$

$$\Rightarrow V_A + 1 + i_3(1) - 2 = V_B \Rightarrow V_B - V_A = 3 - 2 = 1 \text{ volt}$$

40. (D)

(d) Given : Power, $P = 1 \text{ kW} = 1000 \text{ W} = P_{\text{output}}$

$$R = 2\Omega, V = 220 \text{ V}$$

$$\text{Current, } I = \frac{P}{V} = \frac{1000}{220}$$

$$P_{\text{loss}} = I^2 R = \left(\frac{1000}{220}\right)^2 \times 2$$

$$P_{\text{in}} = P_{\text{output}} + P_{\text{loss}}$$

$$\therefore \text{Efficiency} = \frac{1000}{1000 + P_{\text{loss}}} \times 100 = 96\%$$


41. (B)

(b) Maximum power in external resistance is generated when it is equal to internal resistance of battery i.e., P_R maximum when $r = R$

The maximum Joule heating in R will take place for, the resistance of small element

$$dR = \frac{\rho dr}{2\pi r l} \Rightarrow R = \frac{\rho}{2\pi l} \int_a^b \frac{dr}{r}$$
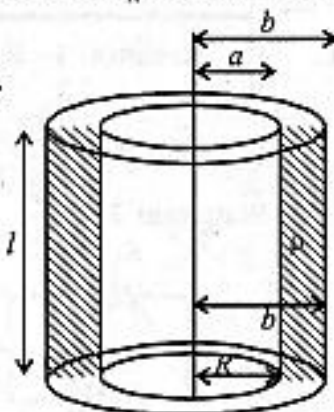
$$\Rightarrow R = \frac{\rho}{2\pi l} \ln \frac{b}{a}$$



42. (D)

(d) The voltmeter of resistance $10\text{k}\Omega$ is parallel to the resistance of 400Ω . So, their equivalent resistance is

$$\frac{1}{R'} = \frac{1}{10\text{ k}\Omega} + \frac{1}{400\Omega} = \frac{1}{10000} + \frac{1}{400}$$

$$\Rightarrow \frac{1}{R'} = \frac{1+25}{10000} = \frac{26}{10000} \Rightarrow R' = \frac{10000}{26}\Omega$$

Using Ohm's law, current in the circuit

$$I = \frac{\text{Voltage}}{\text{Net Resistance}} = \frac{6}{\frac{10000}{26} + 800}$$

Potential difference measured by voltmeter

$$V = IR' = \frac{6}{\frac{10000}{26} + 800} \times \frac{10000}{26} \Rightarrow V = \frac{150}{77} = 1.95 \text{ volt}$$

43. (D)

(d) Let R be the resistance of the whole wire

Potential gradient for the potentiometer wire

$$'AB' = -\frac{dV}{d\ell} = \frac{I \times R}{\ell}$$

$$= \left[\frac{60 \times R}{\ell_{AB}} \right] \text{mv/m}$$


$$V_{AP} = \left(\frac{dV}{d\ell_{AB}} \right) \ell_{AP}$$

$$= \frac{60 \times R}{1200} \times 1000 \text{mV}$$

$$\Rightarrow V_{AP} = 50 R \text{ mV}$$

Also, $V_{AP} = 5 \text{ V}$ (for balance point at P)
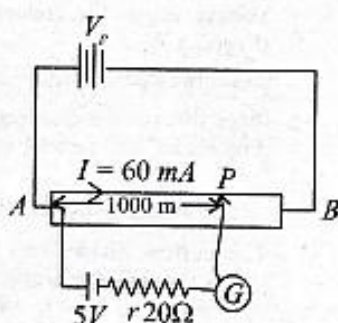
$$\therefore R = \frac{V_{AP}}{50 \times 10^{-3}} = \frac{5}{50 \times 10^{-3}} = 100\Omega$$



44. (D)

(d) From colour code for electric resistance,

Violet Green Red Gold

7 5 2 5%

$$\therefore R = 75 \times 10^2 \pm 5\% \text{ of } 7500 \Rightarrow R = (7500 \pm 375)\Omega$$

45. (A)
 (a) Current is constant in the conductor. $I = \text{constant}$

Resistance of element of conductor, $dR = \frac{\rho dx}{\pi r^2}$


$dV = idR = \frac{i\rho dx}{\pi r^2}$

$E = \frac{dV}{dx} = \frac{i\rho}{\pi r^2}$

Drift velocity,

$V_d = \frac{eE\tau}{m}$ As $V_d \propto E$ and $E \propto \frac{1}{r^2}$

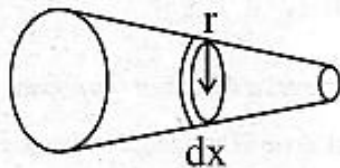So, if r decreases, E will increase and hence V_d .



46. (C)
 (c) From formula, drift velocity, $V_d = neV_d\bar{A}$

$\Rightarrow n = \frac{1}{AeV_d} = \frac{10}{5 \times 10^{-6} \times 1.6 \times 10^{-19} \times 2 \times 10^{-3}}$
 $= 625 \times 10^{25}$

47. (B)
 (b) Given, $i = \alpha_0 t + \beta t^2$

Put $\alpha_0 = 20$ and $\beta = 8$, we get $i = 20t + 8t^2$

Current, $i = \frac{dq}{dt} \Rightarrow \int dq = \int idt \Rightarrow q = \int_0^{15} (20t + 8t^2) dt$

$\Rightarrow q = \left(\frac{20t^2}{2} + \frac{8t^3}{3} \right)_0^{15} = 20 \times \left(\frac{15^2 - 0^2}{2} \right) + \frac{8}{3} (15^3 - 0^3)$

$\Rightarrow q = 10 \times (15)^2 + \frac{8(15)^3}{3} \Rightarrow q = 2250 + 9000 = 11250 \text{ C}$

48. (B)
 (b) Resistance, $R = \frac{\rho \ell}{A} = \frac{\rho \ell^2}{(\text{Vol.})}$ or $R \propto \ell^2$

or, $\frac{R_1}{R_2} = \frac{\ell_1^2}{\ell_2^2}$

As length increases 25%, if $\ell_1 = \ell$ then

$\ell_2 = \ell + \ell \times \frac{25}{100} = 1.25\ell$

$\therefore \frac{R}{R_2} = \frac{\ell^2}{(1.25\ell)^2}$ or, $R_2 = 1.5625R$

\therefore % increase in resistance $R = 56\%$

49. (B)

$$(b) R_{net} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{net} = \left(\frac{\rho_1 \rho_2}{\rho_1 + \rho_2} \right) \frac{l}{A} \Rightarrow l = \frac{(\rho_i + \rho_A) A R_{net}}{\rho_i \rho_A}$$

Putting the required value we get $l = 97 \text{ m}$

50. (A)

$$(a) i_r = \frac{25}{5 + R}$$

in parallel, $E_{eq} = E = 5V$

$$r_{eq} = \frac{r}{5} = \frac{1}{5} \Omega$$

$$i_2 = \frac{5}{R + \frac{1}{5}}$$

putting $i_1 = i_2$,

we get, $4R = 4 \Rightarrow R = 1 \Omega$.

51. (A)

(a) Given, Power of electric bulb, $P = 500W$

$$R = V_1 \Rightarrow 500 = V_1$$

$$\Rightarrow I = 5 \text{ Amp}$$

As current remains same in series, using ohm's law


$$V = I \times R_{eq}$$

$$\Rightarrow 200 = 5 \times R \Rightarrow R_{eq} = 40$$

$$\therefore R + 20 = 40 \Rightarrow R = 20 \Omega$$

52. (B)

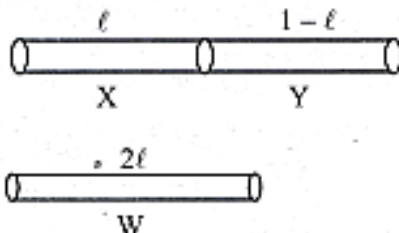(b) Consider of the length of X part is ℓ then the length of Y part will be $1 - \ell$.



$$\frac{R_X}{R_Y} = \frac{\ell_X}{\ell_Y} \left(\because R = \frac{\rho \ell}{A} \right)$$

When wire is stretched to double of its length, then resistance becomes 4 times.

$$R_W = 4R_X = 2R_Y$$

$$\frac{R_X}{R_Y} = \frac{1}{2} \quad \text{So} \quad \frac{\ell_X}{\ell_Y} = \frac{1}{2}$$

53. (A)

(a) Resistance, $R_1 = \rho \frac{L_1}{A_1}$

$$R_2 = \rho \left(\frac{3L_1}{A_1/3} \right) = 9\rho \frac{L_1}{A_1} \quad \therefore \frac{R_2}{R_1} = \frac{9\rho \frac{L_1}{A_1}}{\rho \frac{L_1}{A_1}} = 9$$

54. (A)

(a) We know that

$$R = R_0(1 + \alpha\Delta T)$$

So, $2 = R_0(1 + \alpha \times 10)$... (i)

$3 = R_0(1 + \alpha \times 30)$... (ii)

Dividing (i) by (ii), we get

$$\frac{3}{2} = \frac{1 + 30\alpha}{1 + 10\alpha} \Rightarrow 3 + 30\alpha = 2 + 60\alpha \Rightarrow 1 = 30\alpha$$

$$\Rightarrow \alpha = \frac{1}{30} = 0.033 \text{ } ^\circ\text{C}^{-1}$$

55. (C)

$$R = \frac{\rho l}{A}$$

$$\frac{\Delta R}{R} = \frac{\Delta l}{l} - \frac{\Delta A}{A}$$

[Note: This is not relative error case, so -ve sign comes

with $\frac{\Delta A}{A}$]

Now, $V = \text{constant}$

$$Al = \text{constant}$$

$$\Rightarrow \frac{\Delta A}{A} + \frac{\Delta l}{l} = 0 \Rightarrow -\frac{\Delta A}{A} = \frac{\Delta l}{l}$$

So, $\frac{\Delta R}{R} = \frac{\Delta l}{l} + \frac{\Delta l}{l} \left[\because \frac{\Delta l}{l} = -\frac{\Delta A}{A} \right]$

$$= \frac{2\Delta l}{l} = 2 \times 0.4 = 0.8\%$$

56. (B)

(b) $A \left(\begin{array}{c} \sigma_1 \\ l \end{array} \right) \left(\begin{array}{c} \sigma_2 \\ l \end{array} \right) \equiv \left(\begin{array}{c} \sigma_{eq} \\ 2l \end{array} \right) A$

Let length of wire be ' l ' and area of wire as ' A '

For equivalent wire length = $2l$; area will be A

Equivalent thermal resistance in series will be given as

$$R_{eq} = R_1 + R_2$$

$$\Rightarrow \frac{2\ell}{\sigma_{eq} A} = \frac{\ell}{\sigma_1 A} + \frac{\ell}{\sigma_2 A} \quad \left[\because R = \frac{\ell}{\sigma A} \right]$$

$$\Rightarrow \frac{2\ell}{\sigma_{eq}} = \frac{\ell}{\sigma_1} + \frac{\ell}{\sigma_2} \Rightarrow \sigma_{eq} = \frac{2\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$$


57. (B)

(b) As $R = \frac{\rho l}{A} \Rightarrow R_i = 14\Omega = \frac{\rho l_0}{\pi r_0^2}$

$$R_f = \frac{\rho l_0}{\pi \left(\frac{r_0}{3}\right)^2} = 9 \frac{\rho l_0}{\pi r_0^2} = 9R_i = 9 \times 14 = 126\Omega$$

$$R_{eq} = \frac{R_f}{7} = \frac{126}{7} = 18\Omega$$

58. (A)

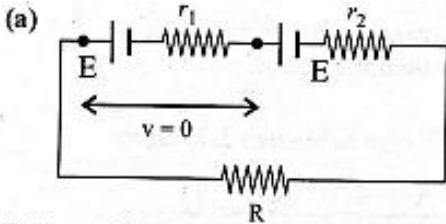

We have, $E - ir_1 = 0$ $[\because V_{r_1} = 0]$
 $\Rightarrow E - ir_1$

Now, $i = \frac{2E}{r_1 + r_2 + R}$

$$\Rightarrow \frac{E}{r_1} = \frac{2E}{r_1 + r_2 + R} \quad \left[\because i = \frac{E}{r_1} \right]$$

$$\Rightarrow r_1 + r_2 + R = 2r_1$$

$$\Rightarrow R = r_1 - r_2$$

59. (A)

(a) In series

$$i_s = \frac{2E}{2r + 2}$$



In parallel

$$i_p = \frac{E}{\frac{r}{2} + 2} = \frac{2E}{r + 4}$$

as, $i_s = i_p$

$$\Rightarrow \frac{2E}{2r + 2} = \frac{2E}{r + 4}$$

$$\Rightarrow r = 2\Omega$$

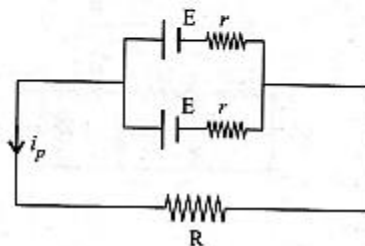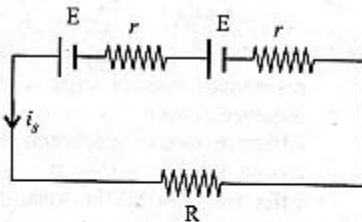

60. (A)

We, have,

$$i = \frac{E_{net}}{R_{net}} = \frac{2E}{R + x_1 + x_3}$$


As, P.d across second cell = 0

$$\Rightarrow E - ir_2 = 0 \quad [\because V = E - iR]$$

$$\Rightarrow E - \frac{2Er_2}{R + r_1 + r_2} = 0$$

$$\Rightarrow R + r_1 + r_2 - 2r_2 = 0$$

$$\Rightarrow R = r_2 - r_1$$

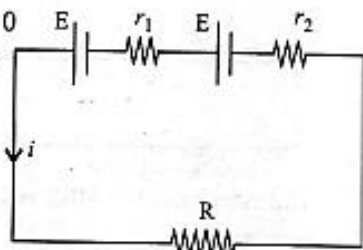

61. (C)



(c) Statement 1 - $R = 80 \Omega$

$$R_1 = R_2 = R_3 = R_4 = 20 \Omega$$

$$\text{In parallel } R_{eq} = \frac{20}{4} = 5 \Omega$$

Statement 2 -

$$R_1 = 3R$$

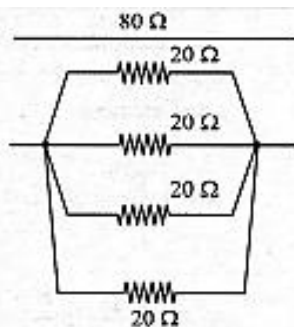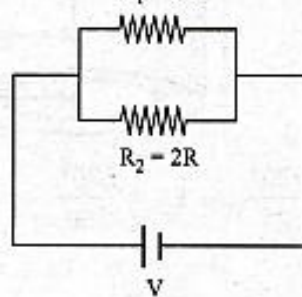

$$P_{th} = \frac{v^2}{R} \Rightarrow P \propto \frac{1}{R}$$

$$\text{So, } \frac{P_1}{P_2} = \left(\frac{R_2}{R_1} \right) = \frac{2}{3} \quad (\text{where } P \text{ is power})$$

62. (B)

(b) Given


$$\frac{1}{2} \frac{\Delta U}{\Delta t} = P_{Bulb} \times N, \text{ where } N = \text{no. of bulb}$$

$$\Rightarrow \frac{9 \times 10^4 \times 10 \times 40}{2 \times 3600} = 100 \times N \quad \left[\because \frac{\Delta U}{\Delta t} = \frac{mgh \text{ J}}{3600 \text{ S}} \right]$$

$$\Rightarrow N = \frac{36 \times 10^6}{72 \times 10^4} \Rightarrow N = \frac{1}{2} \times 100 \Rightarrow N = 50$$

63. (A)

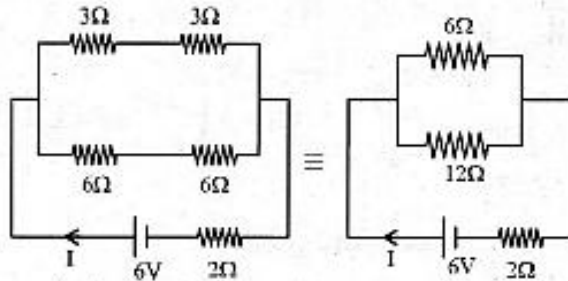(a) Balanced wheat stone bridge in circuit so there is no current in 5Ω resistor so it can be removed from the circuit.



The equivalent resistance will be

$$R_{eq} = \frac{6 \times 12}{6 + 12} + 2 = 6 \Omega$$

Now, apply K.V.L, we have

$$I = \frac{V}{R_{eq}} = \frac{6}{6} = 1A$$

64. (2)

(2) Current through AB , $i_1 = \frac{40}{40 + 60} = 0.4$


Current through AD , $i_2 = \frac{40}{90 + 110} = \frac{1}{5}$

Using KVL in BAD loop

$$V_B + i_1(40) - i_2(90) = V_D$$


$$\Rightarrow V_B - V_D = \frac{1}{5}(90) - \frac{4}{10}(40)$$

$$\Rightarrow V_B - V_D = 18 - 16 = 2V$$

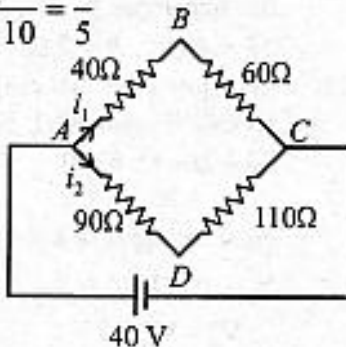

65. (30.00)

(30.00)

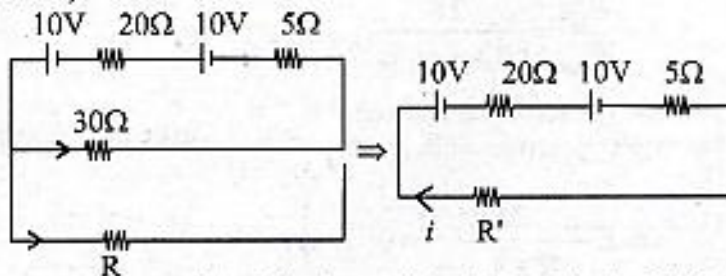

The resistance of 30Ω is in parallel with R . Their effective resistance

$$\frac{1}{R'} = \frac{1}{30} + \frac{1}{R} \Rightarrow R' = \frac{30R}{30+R}$$

Now, $10 - i \times 20 = 0$
 $i = 0.5 \text{ A}$

as, $i = \frac{E}{R_{\text{eq}}} \Rightarrow 0.5 = \frac{10+10}{R'+25}$

$$\Rightarrow 0.5 = \frac{20}{\frac{30R}{R+30} + 25} \Rightarrow R = 30\Omega$$

66. (12)

(12) We know that

$E \propto \ell$ where ℓ is the balancing length

$$\therefore E = k(560) \quad \dots(i)$$

When the balancing length changes by 60 cm

$$\frac{E}{r+10} = k(500) \quad \dots(ii)$$

Dividing (i) by (ii) we get


$$\Rightarrow \frac{r+10}{10} = \frac{56}{50} \Rightarrow 50r + 500 = 560$$

$$\Rightarrow r = \frac{6}{5}\Omega = \frac{N}{10}\Omega \Rightarrow N = 12$$

67. (1)

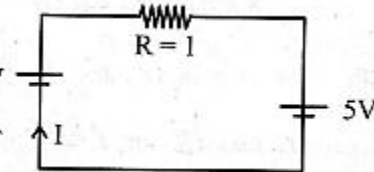(1) From graph (figure 1)
 voltage at $t = 3.2\text{s} = 6\text{V}$

$$\text{Current, } I = \frac{V}{R} = \frac{6-5}{1} = 1\text{A}$$



68. (4)

(4) $I_1 = I_2 = I_{\text{eq}}$
 $A_1 = A_2 = A$ and $A_{\text{eq}} = 2A$

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \frac{\rho(l)}{2A} = \frac{\left(\frac{\rho_1 l}{A}\right)\left(\frac{\rho_2 l}{A}\right)}{\frac{\rho_1 l}{A} + \frac{\rho_2 l}{A}}$$

$$\Rightarrow \frac{\rho}{2} = \frac{\rho_1 \rho_2}{\rho_1 + \rho_2} \Rightarrow \frac{\rho}{2} = \frac{\rho_1 \rho_2}{(\rho_1 + \rho_2)} = \frac{6 \times 3}{(6+3)} = 2$$

$$\therefore \rho = 4$$

69. (5)

(5) Given : Conductivity of wire, $\sigma = 5 \times 10^7 \text{ S/m}$

Radius of wire, $r = 0.5 \text{ mm} = 5 \times 10^{-4} \text{ m}$

Electric field, $E = 10 \times 10^{-3} \text{ V/m}$

$$J = \sigma E = 10 \times 10^{-3} \times 5 \times 10^7 \Rightarrow J = 5 \times 10^5$$

$$\text{Since, } J = \frac{i}{A} \Rightarrow \frac{i}{A} = 5 \times 10^5$$

$$\Rightarrow i = 5 \times 10^5 \times \pi r^2 = 5 \times 10^5 \times \pi \times (5 \times 10^{-4})^2 \\ = 125\pi \times 10^{-3} \text{ A}$$

$$\therefore i = 125\pi \text{ mA} \quad \therefore i = 5^3 \pi \text{ mA} \quad \therefore x = 5$$

70. (300)

(300) Given,

Charge, $q = 20 \text{ C}$, potential difference, $\Delta V = 15 \text{ V}$

Work done, $W = q\Delta V = 20 \times 15 = 300 \text{ J}$

71. (4)

(4) Equivalent resistance in series, $s = R_1 + R_2$

Equivalent resistance in parallel $P = \frac{R_1 R_2}{R_1 + R_2}$

$$\text{Given } (R_1 + R_2) = n \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\Rightarrow R_1^2 + R_2^2 + 2R_1 R_2 = n R_1 R_2$$

$$\Rightarrow \frac{R_1^2}{R_1 R_2} + \frac{R_2^2}{R_1 R_2} + 2 = n \Rightarrow \frac{R_1}{R_2} + \frac{R_2}{R_1} + 2 = n$$

$$\text{Let } \frac{R_1}{R_2} = \alpha$$

$$\text{Then, } \alpha + \frac{1}{\alpha} + 2 = n \Rightarrow \alpha^2 + \alpha(2 - n) + 1 = 0$$

for real value of ' α '

$$(2 - n)^2 - 4 \geq 0$$

$$\text{for minimum value } (2 - n)^2 - 4 = 0$$

$$\Rightarrow n = 0 \text{ or } n = 4$$

$$\Rightarrow n = 4 \quad [\because n \neq 0]$$

72. (20)

(20) in series current i_1 will be $i_1 = \frac{20}{10+10n} = \frac{2}{1+n}$

Current in parallel will be $i_2 = \frac{20}{\frac{10}{n}+10} = \frac{2}{1+n}$

$$\frac{i_2}{i_1} = 20 \Rightarrow \frac{\left(\frac{2n}{1+n}\right)}{\left(\frac{2}{1+n}\right)} = 20 \Rightarrow n = 20$$

73. (15)

(15) Here, $I = \frac{E}{R+r}$ \therefore Terminal voltage $v = IR = \frac{ER}{R+r}$

When potential difference, $V = 1.25\text{V}$ and $R_L = 5\Omega$, then

$$1.25 = \frac{E(5)}{5+r} \quad \dots(i)$$

when potential difference $V = 1\text{V}$ and $R_L = 2\Omega$ then

$$I = \frac{E(2)}{2+r} \quad \dots(ii)$$

From eq. (i) and (ii)

we get $E = \frac{3}{2} = \frac{15}{10}$ \therefore value of $x = 15$

74. (4)

(4) First case $P_1 = \frac{V^2}{R} = \frac{(240)^2}{36}$

Second case $P_2 = \frac{V^2}{R/2} \times 2 = \frac{4v^2}{R} = \frac{4 \times (240)^2}{36}$

$$\therefore \frac{P_1}{P_2} = \frac{1}{4} \quad x = 4.00$$

75. (3840)

(3840) Rate of energy dissipated

$$= \frac{192J}{15} = i^2 R \Rightarrow 192 = 42 \times R, R = 12\Omega$$

$$\text{Energy} = i^2 R t = (8)^2 \times 12 \times 5 = 3840 J$$

76. (2500)

(2500) From, $H = i^2 R \Delta T$

$$10 \times 10^{-3} = (2 \times 10^{-3})^2 \times R \times 1 \quad \therefore R = 2500 \Omega$$

77. (48)


(48) In balanced condition,

$$\frac{x}{12} = \frac{72-x}{6}$$

$$\Rightarrow x = 2(72 - x)$$

$$\text{or, } 3x = 144$$
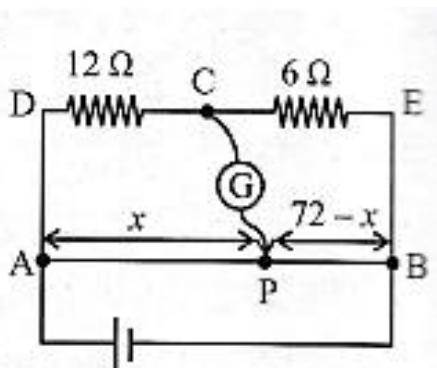
$$\therefore x = \frac{144}{3} = 48 \text{ cm}$$



78. (144)

(144) We have

$$R = \text{slope of } I-V \text{ curve} = \tan 45^\circ = 1$$

$$\text{As, } R = \frac{\rho l}{A} \Rightarrow \rho = \frac{RA}{l} = \frac{1 \times \pi \times (1.2 \times 10^{-2})^2}{31.4 \times 10^{-2}}$$

$$= 144 \times 10^{-3} \Omega \text{ cm}$$

79. (48)

(48) $I = J A$

$$= 4 \times 10^6 \left[\pi R^2 - \pi \left(\frac{R}{2} \right)^2 \right] = 4\pi \times 10^6 \left[\frac{3R^2}{4} \right]$$

$$= \pi \times 10^6 \times 3 \times 16 \times 10^{-6} = 48 \pi \text{ A}$$

80. (300)

(300) If length is increased by n times then, resistance increased by n^2 times


$$\text{So, } R_f = 4R_i$$

$$\Delta R = R_f - R_i = 3R_i$$

$$\% \Delta R = \frac{3R_i}{R_i} \times 100 = 300\%$$

81. (2)

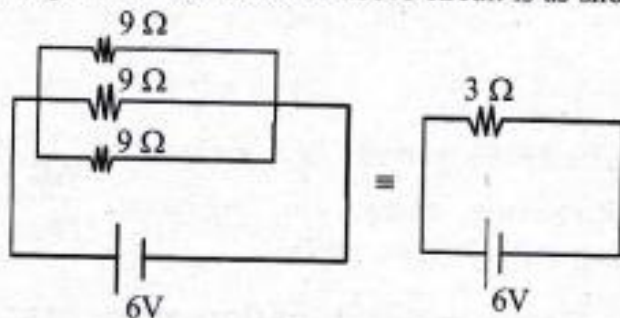(2) Equivalent circuit of the above circuit is as shown below



$$I = \frac{6}{3} = 2A$$


82. (10)

We have $i = \frac{15}{1+2} = 5A$

And, $V_A = V_B = -15 + iR = -15 + 5 \times 1 = -10V$

So, $V_B - V_A = 10V$.

83. (8)

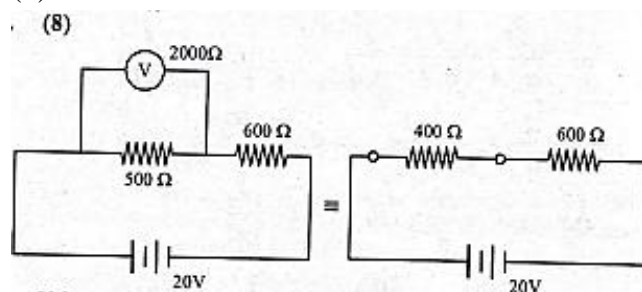

Voltage measured by voltmeter
= voltage across 400Ω

$$= \frac{400}{400 + 600} \times 20 = 8V$$

84. (4)

$$(4) E_{eq} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}} = \frac{\frac{2}{1} + \frac{4}{1} + \frac{4}{1}}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}} = \frac{12}{3} V$$

$$r_{eq} = \frac{1}{3} k\Omega$$

So, $V_o = E_{eq} - i r_{eq} = \frac{12}{3} - 0 \times \frac{1}{3} = 4V$

85. (14)

For Bulb 1

$$R_1 = \frac{V^2}{P} = \frac{220^2}{100} = 484$$

For Bulb 2

$$R_2 = \frac{V^2}{P} = \frac{220^2}{60} = 484 \left(\frac{10}{6} \right)$$

$$I = \frac{220}{484 + 484 \times \frac{10}{6}} \quad \left[\because I = \frac{E}{R_1 + R_2} \right]$$
$$P_1 = I^2 R_1 = 14.06 \text{ W}$$

86. (15)

(15) Thermal energy, $H = \frac{V^2}{R} t$

$$\text{So, } H = \frac{V^2}{R_1} \times 20 \quad \dots(i)$$

$$H = \frac{V^2}{R_2} \times 60 \quad \dots(ii)$$

Dividing (ii) by (i), we get

$$1 = \frac{R_2}{R_1} \times \frac{1}{3} \Rightarrow R_2 = 3R_1$$

$$\text{Now, as } H = \frac{V^2}{R_{eq}} \times t \Rightarrow \frac{V^2}{R_1} \times 20 = \frac{V^2 \times t}{R_{eq}} \quad [\text{from (i)}]$$

$$\Rightarrow \frac{20}{R_1} = \frac{t}{3R_1} \quad \left[\because R_{eq} = \frac{R_1 \cdot 3R_1}{R_1 + 3R_1} \right]$$

$$\Rightarrow t = 15 \text{ minutes}$$

87. (975)

(975) As, $P = Vi$

$$\Rightarrow 5 = 25i \Rightarrow i = 0.2A$$

$$\text{Now, } i = \frac{V_R}{R} \Rightarrow 0.2 = \frac{220 - 25}{R}$$

$$R = \frac{195}{0.2} = 975 \Omega$$


88. (780)

(780) Given null point for cell is, $AC = 60$ cm and $AB = 300$ cm

$$E = \frac{AC}{AB}(V_A - V_B)$$

$$\therefore 20 \times 10^{-3} = \frac{60}{300} \times \frac{4 \times 20}{R + 20}$$

$$\therefore R = 780 \Omega$$

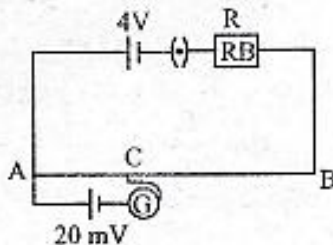


89. (20)

(20) Let resistance of potentiometer wire is R .

The current in the circuit,

$$i = \frac{4}{R + 780}$$

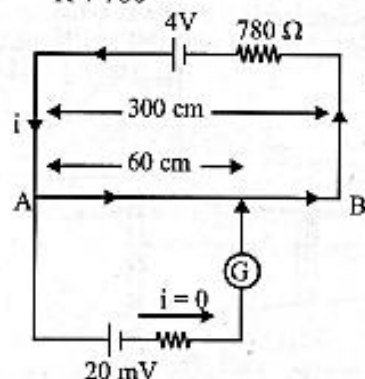

Potential difference across AB , $V_{AB} = iR$

$$= \frac{4}{R + 780}$$

Potential difference across AC , $V_{AC} = iR$

$$= \frac{4R \times 60}{(R + 780) \times 300} = \frac{4R}{5(R + 780)}$$

This should be equal to 20 mV.

$$\frac{4R}{5(R + 780)} = 20 \times 10^{-3} \Rightarrow 4R = 5 \times 20 \times 10^{-3} (R + 780)$$

$$\Rightarrow 40R = R + 780 \Rightarrow 39R = 780$$

$$R = \frac{780}{39} = 20 \Omega$$

90. (54)

(54) As, $E = K\ell$

$$1.2 = (\text{Potential Gradient}) \times 36$$

$$1.8 = (\text{Potential Gradient}) \times x$$


On dividing, we get

$$\frac{2}{3} = \frac{36}{x} \Rightarrow x = 18 \times 3 = 54 \text{ cm}$$

91. (8)

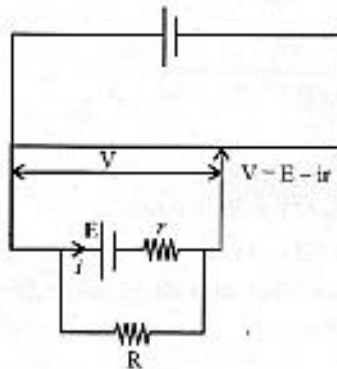(8) We have

$$\frac{V_1}{V_2} = \frac{K \times 3}{K \times 2} = \frac{3}{2}$$



$$\text{Also, } \frac{V_1}{V_2} = \frac{E - i_1 r_1}{E - i_2 r_2} = \frac{E - \frac{E}{8+r} \times r}{E - \frac{E}{4+r} \times r}$$

$$\frac{V_1}{V_2} = \frac{8(4+r)}{4(8+r)}$$


From (i) & (ii), we get

$$\frac{3}{2} = \frac{8(4+r)}{4(8+r)} \Rightarrow \frac{3}{4} = \frac{4+r}{8+r}$$

$$\Rightarrow 24 + 3r = 16 + 4r \Rightarrow 8 = r \Rightarrow r = 8\Omega$$

92. (25)

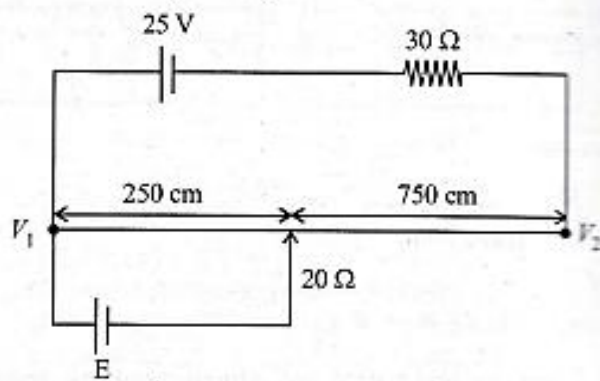(25) Current $i = \frac{25V}{(30 + 20)\Omega}$



$$\Rightarrow i = 0.5A$$

$$\text{So, } v_1 - v_2 = 20i = 20 \times 0.5 = 10 \text{ v}$$

$$E = \text{Potential gradient} \times 250 = \frac{10}{1000} \times 250$$

$$= 2.5 \text{ V} = \frac{25}{10} \text{ V}$$

Solutions to "In-Chapter Exercises"

Learn by doing

Questions based on 'concepts learned so far'

Solⁿ: 1 Number of free charge particles per unit volume

$$n = \frac{\text{total free charge particles}}{\text{total volume}}$$

∴ Total free electrons = total number of atoms

[∵ number of free electron per atom is one]

$$\text{Total free electrons} = \frac{N_A}{M_w} \times M$$

$$\text{so } n = \frac{\frac{N_A}{M_w} \times M}{V} = \frac{N_A}{M_w} \times d = \frac{6.023 \times 10^{23} \times 10^4}{100 \times 10^{-3}}$$

$$n = 6.023 \times 10^{28} \text{ m}^{-3}$$

Solⁿ: 2

~~time = displacement / drift velocity = $\frac{s}{v_d}$~~

~~∴ $v_d = 1 \text{ mm/sec} = 10^{-3} \text{ m/sec}$~~

~~$s = 1 \text{ m}$~~

~~time = $\frac{1}{10^{-3}} = 10^3 \text{ sec}$~~

~~distance travelled = speed × time~~

~~∴ speed = 10^6 m/sec~~

~~so required distance = $10^6 \times 10^3 \text{ m} = 10^9 \text{ m}$~~

Solⁿ: 2

~~We know $R = \frac{\rho l}{A} = \frac{\text{Resistivity} \times \text{length}}{\text{Area of cross section}}$~~

$$R_{AB} = \frac{\rho c}{ab}, \quad R_{CD} = \frac{\rho b}{ac}, \quad R_{EF} = \frac{\rho a}{bc}$$

Solⁿ: 3

As we know that $R = \frac{\rho l}{A}$

In case $R' = \frac{\rho l'}{A'}$

$l' = 2l$

$A'l' = A l$ (Volume of wire remains constant)

$A' = A/2 \Rightarrow R' = \frac{\rho \times 2l}{A/2} = 4R$

$$\therefore R' = 4R$$

Solⁿ 4:

$$R = \frac{\rho l}{A}$$

and

$$\frac{R_1}{R_2} = \frac{l_1^2}{l_2^2}$$

since volume is const.

~~$\frac{AR}{R}$~~

hence $\frac{R_2 - R_1}{R_1} \times 100 = \left[\frac{(1 + \frac{x}{100})^2 - 1}{1} \right] \times 100$

[for x% increment in length]

If x is small

$$\frac{R_2 - R_1}{R_1} \times 100 \approx 2x\%$$

[here x = 1%]

hence $\boxed{\text{Ans: } = 2\%}$

Solⁿ 5:

change in resistance is small

$$\therefore R = R_0 (1 + \alpha \Delta T)$$

$$\Rightarrow 1.2 = 1 \times (1 + 10^{-2} \Delta T)$$

$$\Rightarrow 0.2 = 10^{-2} \Delta T$$

$$\Rightarrow \Delta T = 20^\circ\text{C} \Rightarrow T_2 - T_1 = 20^\circ\text{C} \Rightarrow \boxed{T_2 = 40^\circ\text{C}}$$

Solⁿ 6:

~~$V_C - V_D$~~

$$V_C - V_D = iR$$

$$\Rightarrow (10 - 4) = i(2)$$

$$\Rightarrow \boxed{i = 3\text{ A}}$$

Solⁿ 7:

All resistors are in series $R_{eq} = 6 \Omega$

$$i = \frac{V}{R_{eq}} = \frac{30}{6} = 5\text{ A}$$

$$\boxed{i = 5\text{ A}}$$

Solⁿ 8:

~~R_{eq}~~ $\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6}$ [since All resistors are in parallel]

$$\frac{1}{R_{eq}} = \frac{3+2+1}{6} \Rightarrow R_{eq} = 1$$

So current passing through battery = $\frac{V}{R_{eq}} = \frac{30}{1} = 30\text{ A}$

potential diff across 2 Ω resistor = 30V

hence current through 2 Ω resistor = $\frac{30}{2} = 15\text{ A}$

—— " —— " 3 Ω resistor = $\frac{30}{3} = 10\text{ A}$

—— " —— " 6 Ω resistor = $\frac{30}{6} = 5\text{ A}$

Solⁿ 9: $R_{eq} = 1 + 1 = 2 \Omega$


hence $i = \frac{30}{2} = 15 A$

$i = 15 A$

Solⁿ 10:

$2 \Omega, 1 \Omega$ in series $= 3 \Omega$

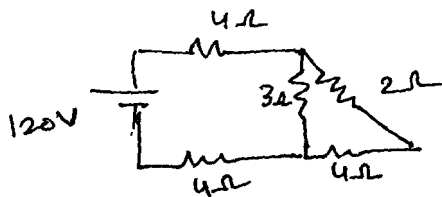
this $3 \Omega, 6 \Omega$ are in parallel $\Rightarrow \frac{3 \times 6}{3 + 6} = 2 \Omega$



Now $2 \Omega, 4 \Omega$ in series $= 6 \Omega$

6Ω in parallel with 3Ω


$= 2 \Omega$

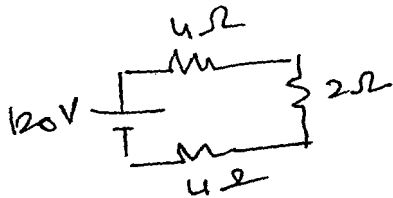

$\Rightarrow R_{eq} = 4 + 2 + 4 = 10 \Omega$

$i = \frac{120}{10} = 12 A$

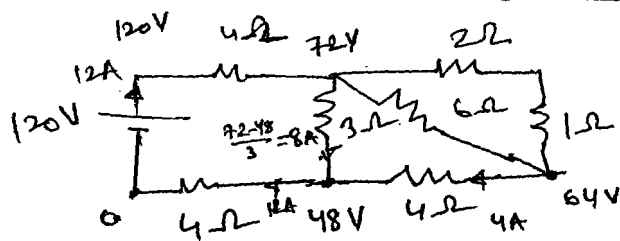~~Correct~~ Assign potential to diff. points & use Kirchhoff's law



hence current through 6Ω

$= \frac{72 - 64}{6}$
 $= \frac{8}{6} = \frac{4}{3}$

so remaining current will pass through 2Ω hence current in 2Ω

$= 12 - (8 + \frac{4}{3})$

$= 4 - \frac{4}{3} = \frac{8}{3} A$ Ans.

Current in $2 \Omega = \frac{8}{3} A$

Solⁿ 11:

(i) $\frac{V^2}{R} = 100 \Rightarrow R = \frac{(220)^2}{100} = 484 \Omega$

$R = 484$

Since Resistance depends only on material hence It is const. for bulb.

(ii) $I = \frac{V}{R} = \frac{220}{484} = \frac{5}{11} \text{ Amp.}$


$i = \frac{5}{11} \text{ Amp}$

(iii) Power consumed at 110 volt

$= \frac{(110)^2}{484} = 25 W$

$P = 25 W$

Solⁿ 12:

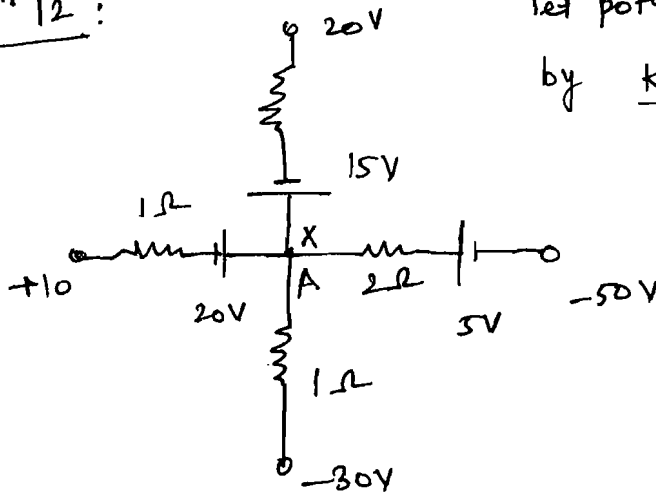

let potential at A = x
by KCL at junction A


$$\frac{x - 20 - 10}{1} + \frac{x - 15 - 20}{2} + \frac{x + 45}{2} + \frac{x + 30}{1} = 0$$

$$\Rightarrow 6x + 10 = 0$$

$$\Rightarrow x = -5/3$$

Potential at A = $-\frac{5}{3}V$

Solⁿ 13:

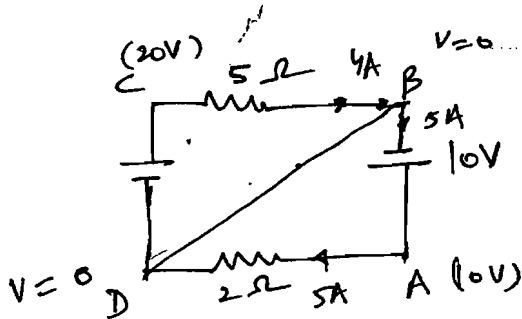

let at D potential = 0

hence current in CB
= $\frac{20 - 0}{5} = 4A$

current in AD [same as BA]
= $\frac{10 - 0}{2} = 5A$

hence at junction B by KCL

current in BD = 1A from D to B.

Solⁿ 14:


$$R_1 = \frac{(200)^2}{50} \quad R_2 = \frac{(200)^2}{100} \quad R_3 = \frac{(200)^2}{25}$$

hence $i = \frac{200}{R_1 + R_2 + R_3} = \frac{100}{200 \times 7} = \frac{1}{14} A$

Since higher resistance, will glow more
(∵ I same)


B₃ will glow more.

Solⁿ 15:

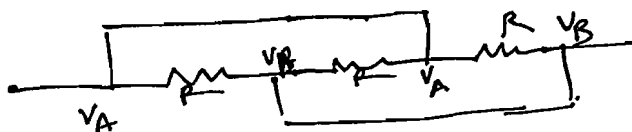


So $R_{eq} = \frac{R}{3}$

so we can have modified circuit as

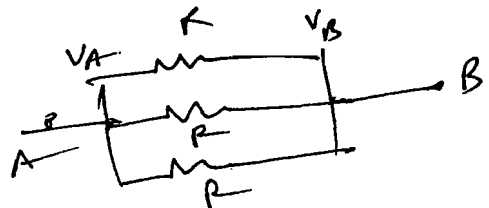

EX-II Questions based on concepts learned so far

1.


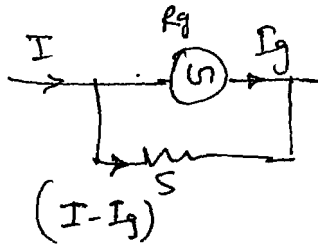


$$R_g I_g = (I - I_g) S$$

$$\Rightarrow 99 \times \frac{I}{10} = (I - \frac{I}{10}) S$$

$$\Rightarrow \boxed{S = 11 \Omega}$$

2.

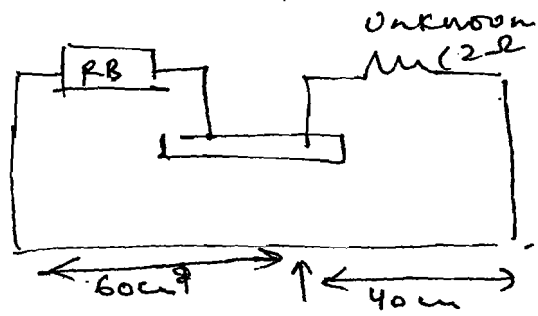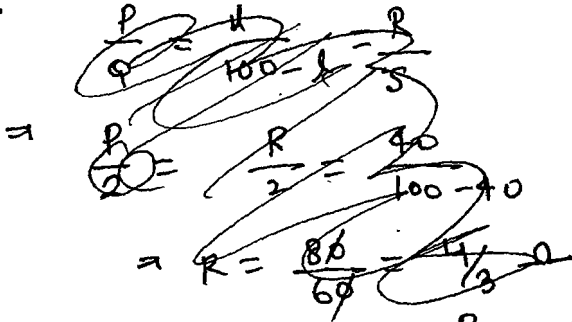

$$\Rightarrow R = \frac{80}{60} = \frac{4}{3} \Omega$$

$$\frac{R}{60} = \frac{2}{40} \Rightarrow \boxed{R = 3 \Omega}$$

3.

$$i_g R_g = (i - i_g) S$$

$$\Rightarrow S = \frac{i_g R_g}{i - i_g} = \frac{1 \times 10^{-3} \times 20}{49 \times 10^{-3}} = \frac{20}{49} \Omega$$

4. (B)


5. (A)

6. All elements are in series same current

$$E_{eq} = 25V \quad R_{eq} = 4 + 3 + 2 + 1 = 10$$

$$i = \frac{25}{10} = 2.5A$$

7.

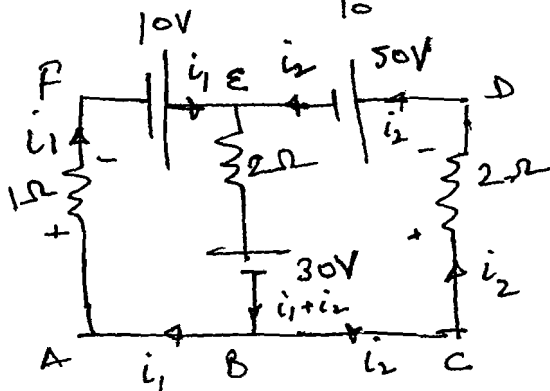

KVL in ABEFA

$$i_1 + 2(i_1 + i_2) + 30 = 0$$

$$\boxed{3i_1 + 2i_2 + 20 = 0} \quad \text{--- (1)}$$

KVL in BEDCB

$$30 + 2i_2 + 50 + 2(i_1 + i_2) = 0$$

$$\Rightarrow 4i_2 + 2i_1 + 80 = 0$$

$$\Rightarrow \boxed{2i_2 + i_1 + 40 = 0} \quad \text{--- (2)}$$

Solving (1) and (2)


$$i_1 = 10A, \quad i_2 = -25A$$

current in wire AF = 10A from A to F

— " — EB = 15A from B to E

— " — DE = 25A from E to D

Solⁿ 8

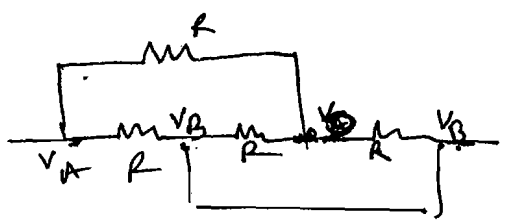

$$R_{eq} = \frac{(R + R/2) \times R}{\frac{3R}{2} + R} = \frac{3R}{5}$$

$$i = \frac{\mathcal{E}(5)}{3R} = \frac{5\mathcal{E}}{3R}$$

current in CD

(inverse ratio of resistance)

$$i = \frac{R}{(3R/2) + R}$$

$$= \frac{5\mathcal{E}}{3} \times \frac{2}{3R}$$

$$= \frac{2\mathcal{E}}{3R}$$

ANS!


Solⁿ 9

$$\mathcal{E}_{eq} = 35V$$


$$R_{eq} = 4 + 8 + 1 + 1 + 2 + 2 + 1 = 15 \Omega$$

$$i = \frac{35}{15} = \frac{7}{3} A$$

ANS!

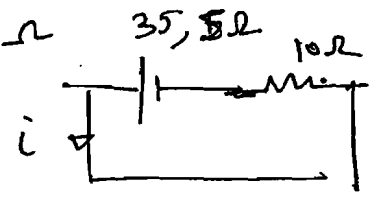

Solⁿ 10

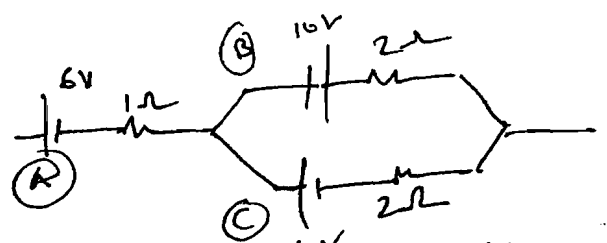


(B) & (C) are in parallel with opposite polarity. So

$$\mathcal{E}_{eq} = \frac{\mathcal{E}_2 r_1 - \mathcal{E}_1 r_2}{r_2 + r_1} = \frac{10 - 4}{2} = 3V$$

$$r_{eq} = \frac{2 \times 2}{4} = 1 \Omega$$

hence

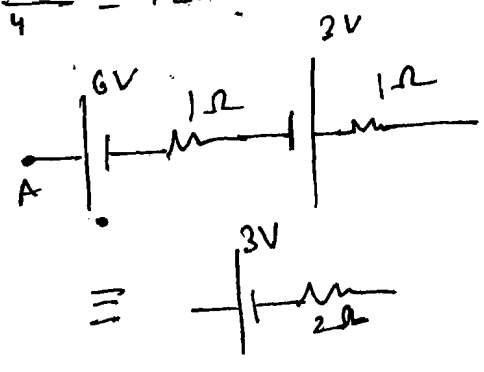

$$\mathcal{E}_{eq} = 3V$$

$$r_{eq} = 2 \Omega$$


Solⁿ 11

full scale current = $i_g = V/G$

to change its range

$$V_1 = (G + R_s) I_g \Rightarrow 2V = (G + R_s) V/G$$

12

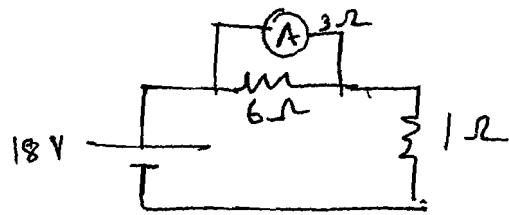

$$R_{eq} = \left(\frac{3 \times 6}{3+6} \right) + 1 = 3\Omega$$


$$\text{Current from battery} = \frac{18}{3} = 6A$$

$$\therefore \text{Current from Ammeter} = 6 \times \frac{6}{9} = 4A$$

No, It's not the current through the 6Ω resistor.

[\because Ammeter is not in series with 6Ω]



13

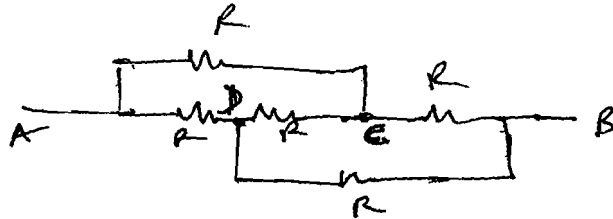

this can be modified

this is balanced
Wheatstone bridge

hence

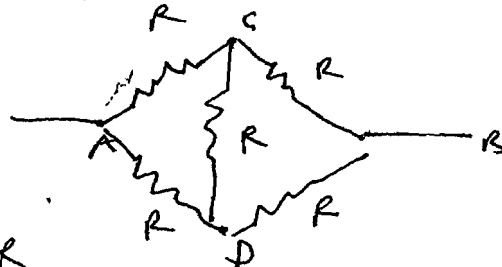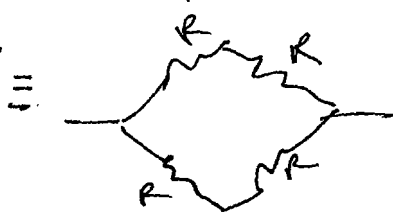

$$R_{eq} = R$$

14

balanced wheatstone bridge hence can remove 20Ω resistor.

$$R_{eq} = \frac{16 \times 8}{16+8} = \frac{16}{3} \Omega$$

15

by symmetry C, O and D will have same potential hence ~~CO & OD~~ CO & OD will have zero current.
so we can remove and can find R_{eq} easily.

$$R_{eq} = \frac{3R}{3} = R$$



1

In series current will remain same

$$\text{hence } n_1 e A v_{d1} = n_2 e A v_{d2} \quad (\because \text{Area same})$$

$$\Rightarrow \frac{v_{d1}}{v_{d2}} = \frac{n_2}{n_1} \quad \text{hence Ans (c) } 4:1$$

2

$$I = neAv_d \quad (1)$$

$$I' = neA'v_d' \quad (2) \quad [\because \text{same material hence } n \text{ will remain same}]$$

$$\Rightarrow I' = \left(\frac{A'}{A}\right) \left(\frac{v_d'}{v_d}\right) I \quad \text{by (1) and (2)}$$

$$= \left(\frac{\pi(r/2)^2}{\pi r^2}\right) \left(\frac{2V}{V}\right) I = I/2 \quad \text{Ans: (c) } I/2$$

3

By convention current moves in the direction of positive charge flow. due to potential difference positive ions and negative ions will move in opposite direction. Hence both will add up to give net current.

$$\text{Due to +ive ion flow } I_1 = n(2e)A(V/4)$$

$$\text{Due to -ive ion flow } I_2 = neAV$$

$$I = I_1 + I_2 = neAV/2 + neAV = \frac{3neAV}{2}$$

4

$$\sigma = \frac{1}{\rho} \quad (\text{Relation b/w resistivity and conductivity})$$

$$\text{Ratio } (Z) \text{ of resistivity to conductivity} = \frac{\rho}{\sigma}$$

$$\Rightarrow Z = \rho^2 \quad \text{as } T \uparrow, \rho \uparrow \quad \text{hence } Z \uparrow$$

5

n & I both same

$$ne \left(\frac{\pi d^2}{4}\right) v = ne \left(\frac{\pi (d/4)^2}{4}\right) v'$$

$$\Rightarrow v' = \frac{16}{4} v = 4v \Rightarrow \boxed{v' = 4v} \quad \text{Ans:}$$


6

Current is same through conductor. n is same also.

$$\text{hence } I = neAv_d$$

$$\text{as } A \downarrow \quad v \uparrow$$

$$\therefore v_p > v_q$$

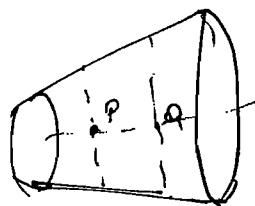

Cross-section
[Area at P < cross section area at Q]

7

$$n = p(\text{given}), A = S, e = v$$

$$I = neAv$$

$$I = pqSv$$

$$v_d = \frac{i}{pqs}$$

8

free electrons move with a very high speed in comparison with metal ions (only vibrates)

hence $K_1 > K_2$. [K.E. of conduction electrons is more]

9

$$I_{av} = \frac{\Delta Q}{\Delta t}$$

$$\Rightarrow I = \frac{Q}{(2\pi/\omega)} \Rightarrow \boxed{I = \frac{Q\omega}{2\pi}}$$

10

As temp. increases, the thermal vibrations in the lattice increase causing more electron scattering therefore more collisions will take place, slowing down the electron flow. As temp. \uparrow , No additional charge carriers can generate since free electrons in a metal is const. Scattering is the cause for increase in resistance. (collisions ~~doe~~ with metal ions will ~~more~~ slow down electron flow \downarrow more relatively).

11

Resistance \downarrow hence $i = V/R$, current increases

12

$$R_a = \frac{\rho_a l_a}{A_a} \quad R_b = \frac{\rho_b l_b}{A_b}$$

hence we can't deduce a relation b/w ρ_a and ρ_b without any information abt l_a, A_a, l_b and A_b .

13

Product (Z) of resistivity and conductivity
 $= \rho\sigma$

$$\because \sigma = \frac{1}{\rho} \Rightarrow Z = \rho \cdot \frac{1}{\rho} = 1$$

$$\Rightarrow \boxed{Z=1} \text{ (const.)}$$


hence as $T \uparrow$ Z is const.

[No effect of temperature on the product]

14 | During charging of a battery, positive charge enters the battery at the positive terminal, moves inside the battery to the negative terminal.

15 | $\Sigma E = E_1 + E_2$ $r_{eq} = r_1 + r_2$
 (hence 1 is correct but 2 is wrong)

16 | $P = \frac{V^2}{R}$ since V is same
 as $R \downarrow$ $P \uparrow$

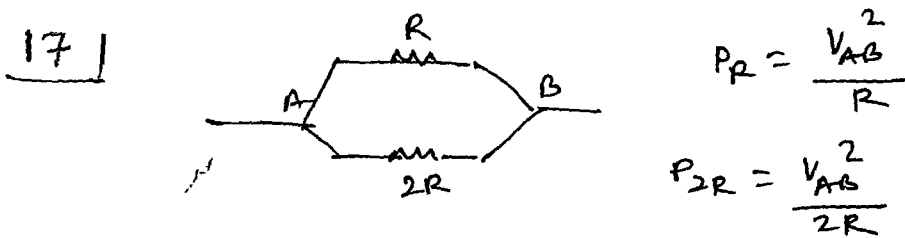

$P_R : P_{2R} = 1 : \frac{1}{2}$

$P_R : P_{2R} = 2 : 1$

18 | By Max^m Power Transfer Theorem
 $R = r$

19 | $\Sigma E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$ $r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$ (1) (2)

by eqⁿ (1) ΣE_{eq} will be greater than smaller of the two emfs

by eqⁿ (2) $\Sigma E_{eq} = E$ If $E_1 = E_2 = E$
 $r_{eq} < r_1$

Also $r_{eq} < r_2$

hence Given statement (a) is correct but 1 is wrong.

20 | If polarity of n cells is reversed in N cells in series combination

$\Sigma E_{eq} = E_0 = (N - 2n)E$


$r_0 = r + r + r \dots - N$
 $= Nr$

Ans:

21

for 1 case

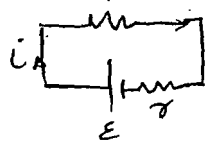Potential difference
between the terminals
 $= 1.6V$



$$i = \frac{E}{R+r}$$

hence $E - \left(\frac{E}{4+r}\right)r = 1.6$ — (1)

Similarly $E - \left(\frac{E}{9+r}\right)r = 1.8$ — (2)

Since Potential diff.
across terminal
 $= E - ir$

by (1) and (2)

$$4+r = 4E/1.6$$
$$9+r = 9E/1.8$$

$$\Rightarrow 1.6\left(\frac{4+r}{4}\right) = 1.8\left(\frac{9+r}{9}\right)$$

$$\Rightarrow 1.6 + 0.4r = 1.8 + 0.2r$$

$$\Rightarrow 0.2r = 0.2$$

$$\Rightarrow \boxed{r=1} \Omega$$


by eqn (1)

$$4+1 = \frac{4E}{1.6}$$

$$\Rightarrow 4E = 8$$

$$\Rightarrow \boxed{E = 2 \text{ Volt}}$$

22

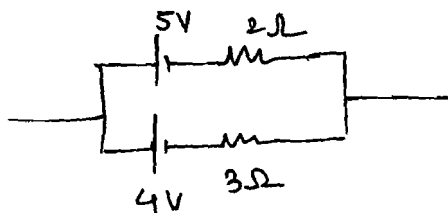

$$E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$
$$= \frac{5(3) + 4(2)}{5}$$
$$= \frac{23}{5} = 4.6 \text{ Volt}$$


23

since battery is charging

$$E + ir = 12.5$$


$$E + (1)(0.5) = 12.5$$
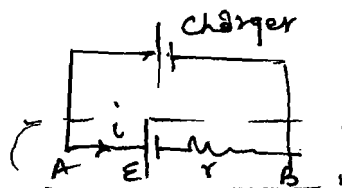
$$\Rightarrow \boxed{E = 12 \text{ Volt}}$$



$$V_A - E - ir = V_B$$
$$\Rightarrow V_A - V_B = E + ir$$


24

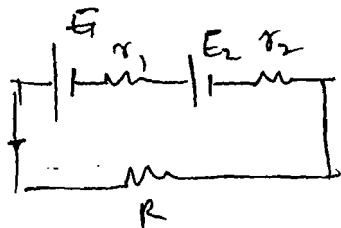

Initially current through R

$$\Rightarrow I_1 = \frac{E_1 + E_2}{R + r_1 + r_2}$$

After short circuiting the battery

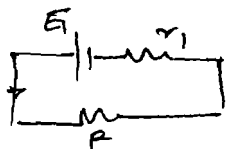

$$I_2 = \frac{E_1}{R + r_1}$$

Condition such that

$$I_2 > I_1$$

$$\Rightarrow \frac{E_1}{R+r_1} > \frac{E_1+E_2}{R+r_1+r_2}$$

$$\Rightarrow E_1 R + E_1 r_1 + E_1 r_2 > E_1 R + E_2 R + E_1 r_1 + E_2 r_1$$

$$\Rightarrow E_1 r_2 > E_2 R + E_2 r_1$$

$$\Rightarrow E_1 r_2 > E_2 (R+r_1)$$

Ans:

25

n identical cells in series connection & terminals of battery containing cells is short circuited.

hence $\Sigma_{eq} = nE$
 $r_{eq} = n\gamma$

hence $i = \frac{nE}{n\gamma}$

$i = E/\gamma = \text{const.}$ [does not depend on ' n ']

hence graph of $\frac{E}{A}$ vs ' n ' will show the same nature (A 's const.)

26

for the above example. If cells are in parallel

$$\Sigma_{eq} = E$$

$$r_{eq} = \gamma/n$$

$$\Rightarrow i = \frac{nE}{\gamma}$$

hence current changes linearly with ' n '.

27

Out of ' n ' cells two cells having reversed polarity.

$$\Sigma_{eq} = (n-2)E - 2E$$

$$\Rightarrow \Sigma_{eq} = (n-4)E$$

$$r_{eq} = n\gamma$$

$$i = \frac{(n-4)E}{n\gamma}$$

Potential drop across A
 $= V_p - V_q$


$$= nE + i\gamma$$

$$= E + \left(\frac{n-4}{n}\right)E$$

$$= \frac{2nE - 4E}{n}$$

$$= 2E - \frac{4E}{n}$$

$$= 2E \left(1 - \frac{2}{n}\right)$$

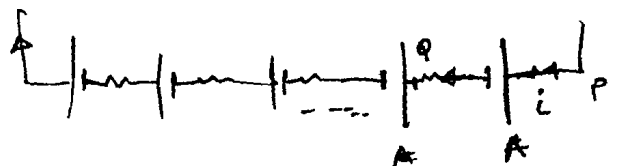


$$V_p - E - i\gamma = V_q$$

$$\Rightarrow V_p - V_q = E + i\gamma$$

$$\mathcal{E}_{eq} = 6 - 2 = 4V$$

$$R_{eq} = 4\Omega$$

$$i = \frac{4}{4} = 1 \text{ Amp}$$

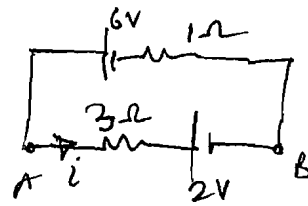

$$V_A - 3 - 2 = V_B$$

$$\boxed{V_A - V_B = 5V}$$

29)

Terminal voltage = $\mathcal{E} - ir$

or can be $\mathcal{E} + ir$


or can be zero if $\mathcal{E} - ir = 0$

hence can be $> \mathcal{E}$

can be $< \mathcal{E}$

can be zero


30)

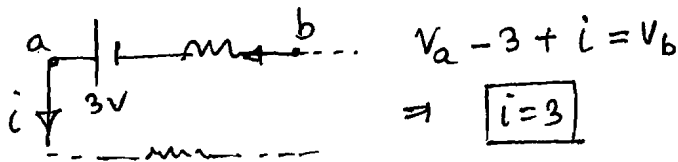

$$\Rightarrow \boxed{i = 3}$$

$$\therefore V_a = V_b$$

Now The whole circuit can be shown as

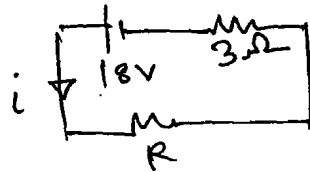

$$i = \frac{18}{R+3}$$

$$\Rightarrow 3 = \frac{18}{R+3}$$

$$\Rightarrow R+3 = 6$$

$$\Rightarrow \boxed{R = 3\Omega}$$

[since batteries are in series]

31)

$$R_T = R_1 + R_2 \quad \text{--- (1)}$$

If thermal expansion is neglected

$$\Delta R_1 = \frac{\Delta \rho_1 L_1}{A_1}$$

$$\Delta R_2 = \frac{\Delta \rho_2 L_2}{A_2}$$

$$R_1 = \frac{\rho_1 L_1}{A_1}$$

$$R_2 = \frac{\rho_2 L_2}{A_2}$$

$$\Delta \rho_1 = \rho_1 \alpha_1 \Delta T$$

$$\Delta \rho_2 = \rho_2 \alpha_2 \Delta T$$

by eqⁿ (1) $\Delta R_T = \Delta R_1 + \Delta R_2$

$$\Rightarrow 0 = \frac{(\rho_1 \alpha_1 \Delta T) L_1}{A_1} + \frac{(\rho_2 \alpha_2 \Delta T) L_2}{A_2}$$


(Given)

$$\therefore A_1 = A_2$$

$$\Rightarrow \boxed{\rho_1 \alpha_1 L_1 + \rho_2 \alpha_2 L_2 = 0}$$

Total Resistance is independent of temperature
 $\therefore \Delta R_T = 0$

32]

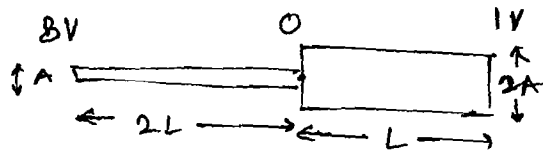

Resistance of longer wire = $\frac{\rho(2L)}{A}$

∴ shorter wire = $\frac{\rho(L)}{2A}$

$R_{eq} = \frac{\rho L}{A} (2 + \frac{1}{2}) = \frac{5\rho L}{2A}$

∴ $i = \frac{8-1}{R_{eq}} = \frac{14A}{\frac{5\rho L}{2A}} = \frac{14A}{5\rho L}$

let junction be 0

by Ohm's law

$\frac{8-V_0}{[\frac{\rho(2L)}{A}]} = i \Rightarrow 8-V_0 = \frac{14}{5} \left(\frac{A}{\rho L}\right) \left(\frac{2\rho L}{A}\right)$

~~$\Rightarrow 8-V_0 = \frac{14 \rho L}{5 A}$~~

$\Rightarrow 8-V_0 = 28/5$

$\Rightarrow V_0 = \frac{40-28}{5}$

$\Rightarrow V_0 = \frac{12}{5} = 2.4 \text{ volt}$

33]

$Q = 2t - 8t^2$

$i = \frac{dq}{dt} = 2 - 16t$

total heat = $\int_0^{1/8} i^2 R dt = \int_0^{1/8} (2-16t)^2 R dt$

= $-\frac{R}{16} \left[\frac{(2-16t)^3}{3} \right]_0^{1/8}$

= $\frac{R}{16} \cdot \left(\frac{2^3}{3}\right) = \frac{R}{6} \text{ J}$ Ans:

34]

Initially $H = \frac{V^2}{R}$

Now R_{eq} becomes = $\frac{(R/n)}{n} = R/n^2$

∴ $H' = \frac{V^2}{R_{eq}} = n^2 \frac{V^2}{R} = n^2 H$

[Making n equal parts
hence resistance of
each part becomes R/n]

Ans:

35]

$P = \frac{V^2}{R}$ as $R \downarrow$ Power \uparrow

% Change = $\frac{\frac{V^2}{R_2} - \frac{V^2}{R_1}}{\frac{V^2}{R_1}} \times 100 = \frac{\frac{1}{R_2} - \frac{1}{R_1}}{\frac{1}{R_1}} \times 100$

= $\frac{R_1 - R_2}{R_2} \times 100 = \frac{R_1 - 0.9R_1}{0.9R_1} \times 100$ [∵ $R_2 = 0.9R_1$]

= $\frac{0.1}{0.9} \times 100 = \frac{100}{9} \approx 11\%$

36

$$R_1 = \frac{(200)^2}{300} = \frac{400}{3} \Omega$$

$$R_2 = \frac{(200)^2}{600} = \frac{400}{6} \Omega$$

$$R_{eq} = R_1 + R_2$$

$$\text{Heat output} = \frac{V^2}{R_{eq}} = \frac{(200)^2}{\left(\frac{400}{3} + \frac{400}{6}\right)}$$

$$= \frac{200}{\left(\frac{2}{3} + \frac{2}{6}\right)} = \frac{200 \times 6}{(4+2)}$$

$$= 200 \text{ Watt} \quad \underline{\text{Ans:}}$$

37

$$R_1 = \frac{(200)^2}{60}$$

$$R_2 = \frac{(200)^2}{100}$$

$$\text{Power} = \frac{(200)^2}{\left[\frac{(200)^2}{60} + \frac{(200)^2}{100}\right]} = \frac{600}{10+6} = \frac{600}{16}$$

$$= \frac{150}{4} = \frac{75}{2} = 37.5 \text{ W} \quad \underline{\text{Ans:}}$$

38

$$\text{Resistance of each bulb} = \frac{(120)^2}{60} = 240 \Omega$$

$$R_{eq} \text{ for series} = 240 + 240 + 240 = 720 \Omega$$

$$\text{hence current through each resistor} = \frac{120}{720} = \frac{1}{6} \text{ Amp}$$

$$\text{so Power dissipated by each bulb} = I^2 R$$

$$= \left(\frac{1}{6}\right)^2 \times 240$$

$$= \frac{40}{6} = \frac{20}{3} = 6.7 \text{ W}$$

39

a ~~Let total current be I~~

Let total current be I (I is passing through 3R)

$$\text{Current through } R = \frac{I \times 2R}{3R} = \frac{2I}{3}$$

$$\frac{P_R}{P_{3R}} = \frac{\left(\frac{2I}{3}\right)^2 R}{I^2 (3R)} = \frac{4}{27}$$

Ans:40

for short hand assume R as part of internal resistance

Now by Max^m power transfer theorem

$$y = R + 2$$

$$\Rightarrow R = y - 2 = 5 - 2 = 3$$

$$\Rightarrow \boxed{R = 3 \Omega}$$

Ans:

41

Same potential diff across R_2, R_3 and R_4
hence by $P = \frac{V^2}{R}$ less R , more P

So R_4 will dissipate more power.

Now we can compare R_1 & R_4 by current.

$P = I^2 R$ i is greater in R_1 as well as $R_1 > R_4$

hence
Ans is R_1 .

42

Given $\frac{d^2V}{dI^2} > 0$ [convex]; as $I \uparrow V \uparrow$

$P = VI$ hence as $I \uparrow V \uparrow$

So as $I \uparrow P$ should increase at a greater rate than $V-I$ curve.

Also nature of the Graph should be convex.

43

$$I = 2.5 \pm 0.05$$

$$V = 10 \pm 0.1$$

$$V = IR \Rightarrow R = \frac{10}{2.5} = 4 \Omega$$

$$\Rightarrow \ln V = \ln I + \ln R$$

$$\Rightarrow \frac{\Delta V}{V} = \frac{\Delta I}{I} + \frac{\Delta R}{R}$$

Since we are dealing with indeterminate errors

$$\Rightarrow \frac{\Delta R}{R} = \frac{\Delta V}{V} + \frac{\Delta I}{I} \quad (\text{for max error})$$

$$\Rightarrow \Delta R = R \left[\frac{0.1}{10} + \frac{0.05}{2.5} \right]$$


$$= \frac{0.4}{10} + \frac{0.2}{2.5} = \frac{12}{100} = 0.12$$

hence Resistance $R = 4 \pm 0.12 \Omega$

44

Metallic conductor obeys Ohm's law [$V = IR$]
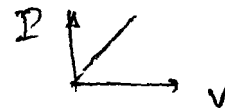
$$\text{slope of Graph} = \frac{I}{V} = \frac{1}{R}$$



So more slope, less R

\Rightarrow less R , less temperature in conductor

$\therefore T_1 < T_2$ (\because more slope, less resistance)

45

After closing switch Req decreases hence $i \uparrow$ but potential difference is maintained by battery.

as $i \uparrow$ Power by $X \uparrow$ ($\because P = i^2 R$)
dissipation

hence brightness of X increases.


Now $i \uparrow$ so more potential drop across X hence less potential drop across Y .

so by $P = \frac{V^2}{R_y}$ $V \downarrow$ hence power dissipation by Y decreases

so brightness of Y decreases.

46

The equivalent circuit can be given as

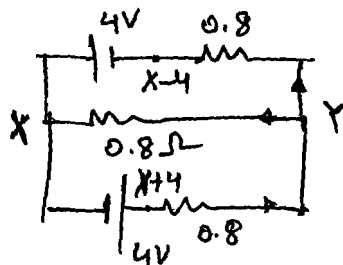

by Kirchoff's law of junction


$$\frac{X+4-Y}{0.8} = \frac{Y-X}{0.8} + \frac{Y-(X-4)}{0.8}$$

$$\Rightarrow \boxed{X=Y}$$

hence no current through 0.8Ω resistor. So the circuit becomes simpler.

$$i = \frac{8V}{1.6} = 5 \text{ Amp}$$

for a cell

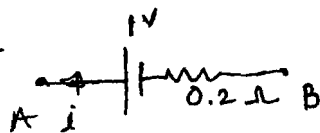


$$V_B - i(0.2) + 1 = V_A$$

$$V_A - V_B = -5(0.2) + 1$$

$$= 0$$

Ans:

47

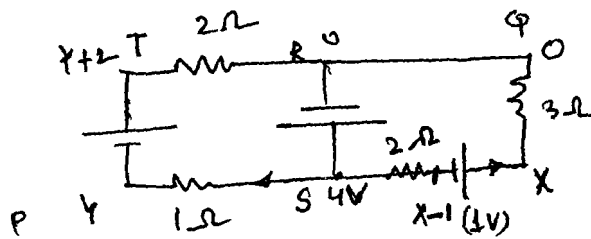

assign 'Q' as zero volt

for loop PTRS

using \oint

$$\frac{4-Y}{1} = \frac{Y+2}{2}$$

$$\Rightarrow 8 - 2Y = Y + 2$$


$$\Rightarrow 3Y = 6 \Rightarrow \boxed{Y=2}$$

hence

$$V_{PQ} = Y - 0 = Y = 2V$$

Ans:

48

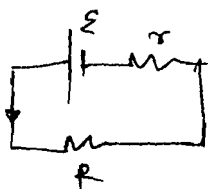


potential difference V across R

$$= iR$$


$$V = \left(\frac{E}{R+r} \right) R = \left(\frac{E}{1+r/R} \right)$$

$$\text{as } R \rightarrow \infty \quad V \rightarrow E$$

49

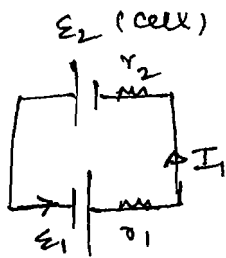
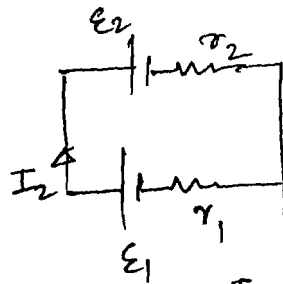
$$I_1 = \frac{\epsilon_1 + \epsilon_2}{r_1 + r_2} \quad \text{--- (1)}$$



$$I_2 = \frac{\epsilon_1 - \epsilon_2}{r_1 + r_2} \quad \text{--- (2)}$$

by (1) and (2)

$$\frac{\epsilon_1 + \epsilon_2}{I_1} = \frac{\epsilon_1 - \epsilon_2}{I_2}$$

$$\Rightarrow \frac{\epsilon_1 + \epsilon_2}{\epsilon_1 - \epsilon_2} = \frac{I_1}{I_2}$$


Now by componendo and dividendo

$$\Rightarrow \frac{2\epsilon_1}{2\epsilon_2} = \frac{I_1 + I_2}{I_1 - I_2}$$

$$\Rightarrow \epsilon_1 = \left(\frac{I_1 + I_2}{I_1 - I_2} \right) \epsilon_2$$

Ans:


50

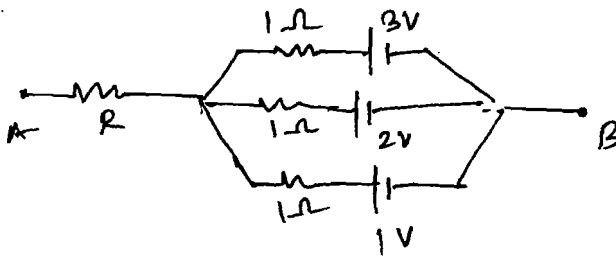

Equivalent of 3V and 1V battery


$$\epsilon_{eq} = \frac{3+1}{2} = 2V, \quad r_{eq} = 1/2$$

hence

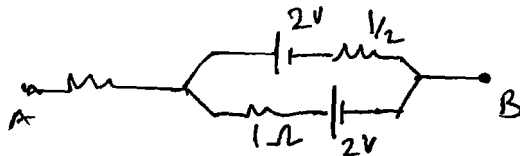

Again equivalent $\epsilon_{eq} = \frac{1+2}{1+1/2} = \frac{3}{3/2} = 2 \text{ Volt}$.

51

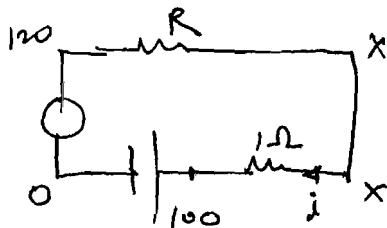

$$V = iR$$

$$\frac{X-100}{1} = 10$$

$$\Rightarrow \boxed{X = 110}$$

Now Also

$$\frac{(120 - X)}{I} = R$$

$$\Rightarrow R = \frac{10}{10} = 1 \Omega$$

Ans:

52

$R_{25} > R_{100}$ \therefore Resistance of 25W bulb will be more \therefore less power

In series current is same.

more resistance means more potential drop.

hence $V_{25} > V_{100}$ (Potential drop across resistor)

hence for 440 V line

$V_{25} > 220V$ \therefore So 25W is likely to fuse.

$$R = V^2/p$$

53

Rate of dissipation per unit volume

$$= \frac{i^2 R}{\text{Volume}}$$

$$= \frac{i^2 \frac{\rho L}{A}}{A L}$$

$$= \left(\frac{i}{A}\right) \left(\frac{i}{A}\right) \rho$$

$$= j \cdot j \rho$$

$$= jE$$

$$\therefore j = \sigma E$$

$$j = \frac{E}{\rho}$$

$$\Rightarrow j \rho = E$$

Ans:

54

n = no. of e^- per unit volume

Specific charge = $\frac{e}{m} = S$

let volume be Al . Total no. of e^- s = (nAl)

hence momentum per unit length = $\frac{(nAl) m v_d}{l}$

$$= nA \left(\frac{e}{S}\right) v_d$$

$$= \frac{neAv_d}{S}$$

$$= I/S \quad \text{Ans:}$$

55

Total current = $\int j ds$

$$= \int_0^{R/2} J_0 \left(\frac{x}{R}\right) 2\pi x dx + \int_{R/2}^R J_0 \frac{x}{R} 2\pi x dx$$

$$= 2\pi \left[\frac{J_0 x^3}{3R} - \frac{J_0 2\pi x^2}{2} \right]_0^{R/2} + \frac{J_0}{R} 2\pi \left[\frac{x^3}{3} \right]_{R/2}^R$$

$$= 2\pi \left[\frac{J_0 R^3}{24R} - \frac{J_0 2\pi R^2}{8} \right] + \frac{J_0 2\pi}{R} \left[\frac{R^3}{3} - \frac{R^3}{24} \right]$$

56

let resistance of wire is R

$$\frac{(3E)^2}{R} \text{ is heat generated}$$

$$ms \Delta T = \frac{(3E)^2}{R} t \quad \text{--- (1)}$$

Now for the other wire mass = $2m$
 $R' = 2R$


$$2ms \Delta T = \frac{(NE)^2}{2R} t \quad \text{--- (2)}$$

$$\left(\frac{3}{N}\right)^2 = \frac{1}{4} \quad \text{by (1) and (2)}$$

$$\Rightarrow N^2 = 36 \Rightarrow \boxed{N=6} \quad \text{Ans!}$$

57

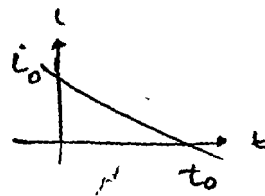let at $t=0$ current is i_0
 and $\Delta t = t_0$



Area under the graph = $\int i dt$
 = charge

$$\Rightarrow \frac{1}{2} i_0 t_0 = q \quad \Rightarrow i_0 = \frac{2q}{t_0}$$

by graph we have

$$i = -\frac{2q}{t_0^2} t + i_0$$

$$i = -\frac{2q}{t_0^2} t + \frac{2q}{t_0}$$

$$\text{Heat Generated} = \int_0^{t_0} \left(-\frac{2q}{t_0^2} t + \frac{2q}{t_0}\right)^2 R dt$$

$$\because H = \int i^2 R dt$$

$$= \frac{t_0^2}{2q} \left[\frac{\left(-\frac{2q}{t_0^2} t + \frac{2q}{t_0}\right)^3}{3} \right]_0^{t_0} R$$

$$= \left(\frac{8q^3 R}{3t_0^3}\right) \left(\frac{t_0^2}{2q}\right) = \frac{4}{3} \frac{q^2 R}{t_0}$$

$$\because t_0 = \Delta t$$

$$H = \frac{4}{3} \frac{q^2 R}{\Delta t}$$

Ans!

58

by effective grouping of cells
 for max^m current

$mn =$ total no. of ~~cells~~ ~~res~~


$$\therefore I = \frac{m n E}{n r + m R}$$

$$\therefore R = 0$$

for I_{max} , m should be max^m

m no. of rows
 n no. of cells in each row

59 |

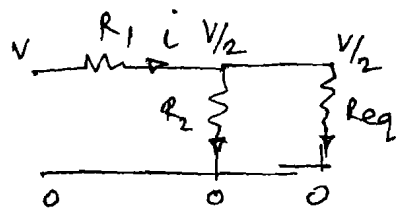

Total current $i = V/R_{eq}$

\therefore current in $R_{eq} = \frac{V/2}{R_{eq}} = i/2$

hence current in R_2 is also $i/2$


We can write

$(V - V/2) = iR_1$ — (1)

$V/2 = (i/2)R_2$ — (2)

$\Rightarrow \frac{R_2}{2} = R_1 \Rightarrow \boxed{\frac{R_1}{R_2} = \frac{1}{2}}$

60 |

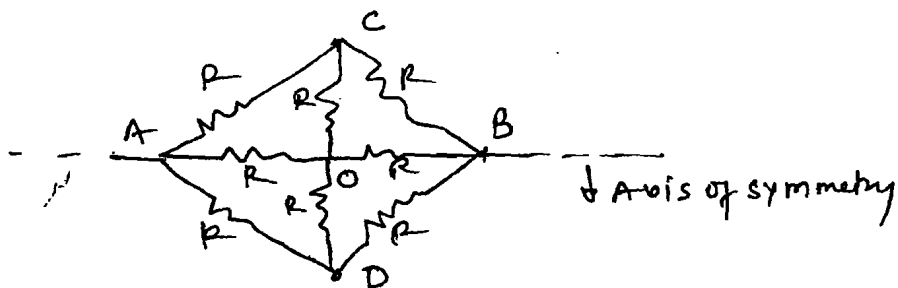


by symmetry \perp branches CO and OD will have no current.

hence simplified circuit is






$R_{eq} = \frac{2R \times 2R}{2R + 2R} = 2R/3$ Ans.

61 |

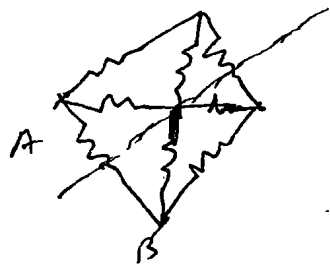


by symmetry

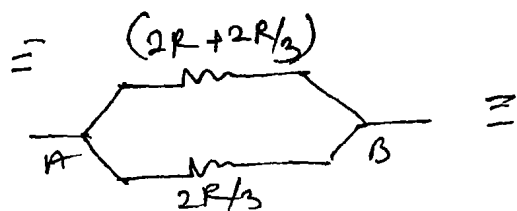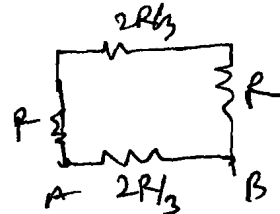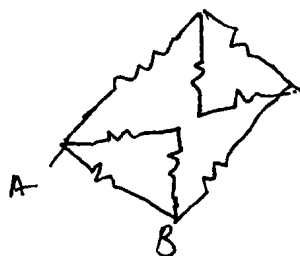


$= \frac{(8R/3) \times (2R/3)}{8R/3 + 2R/3} = \frac{16R^2}{3(10R)} = \frac{16R}{30} = \frac{8R}{15}$

Ans.


62

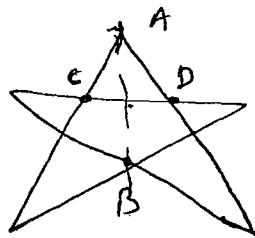

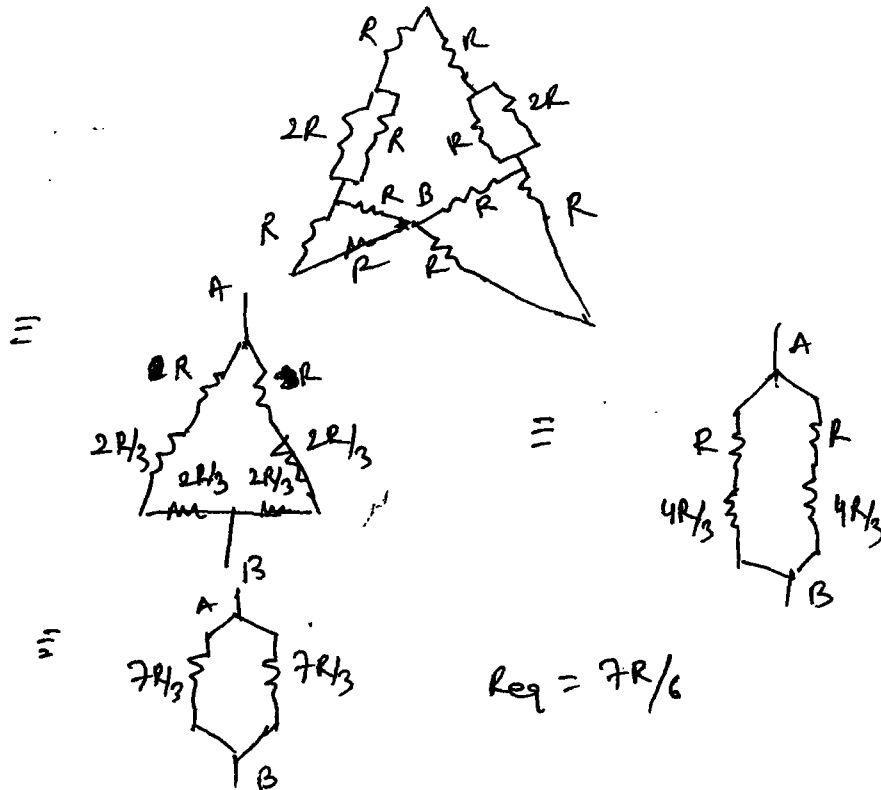by symmetry 1 branch will have no current hence we can remove ~~resistor~~ resistor CD.
circuit becomes



53

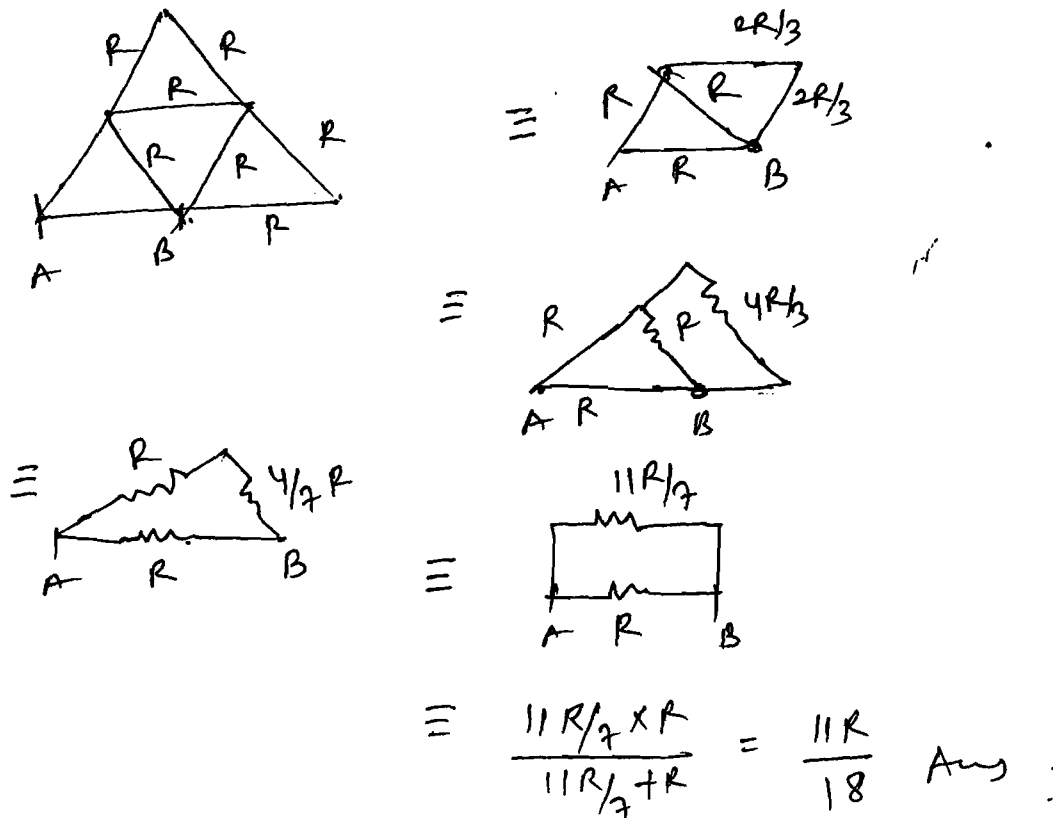

64


When they are in series current is same. When current is

1 Amp both will have same potential drop of 10 volt. [see graphs]

hence for total potential drop of 20 volt the current in circuit is 1 Amp. After 1 Amp, Q has no resistance for current while P can't ~~permit~~ ^{permit} more than 1 Amp. Hence max current will pass through the circuit is 1 Amp. Elements P and Q are in

Series. So below 10 V, current through Q is less. Hence when both put in series, current characteristic will be same as shown by Q because in series current has to be same. This characteristics will be shown up to 20V. After that P will decide the current.

65

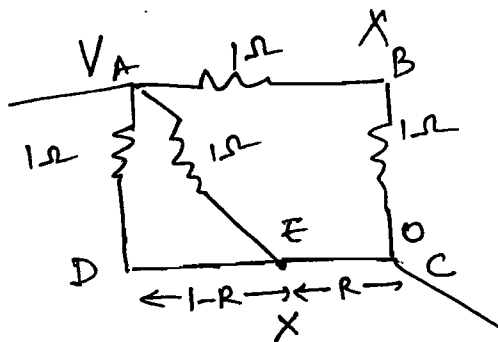

Assign voltage

$$\text{at } A = V$$

$$\text{at } C = 0$$

$$\text{at } E = X = \text{at } B \text{ (Given)}$$

$$\text{let resistance of } EO = R_2$$

$$\text{then resistance of } DX = (1-R)R$$

function, Rule at B

$$\frac{V-X}{1} = \frac{X}{1} \Rightarrow \boxed{V=2X} \quad \text{--- (1)}$$

at E'

$$\frac{V-X}{2-R} + \frac{V-X}{1} = \frac{X-0}{R} \quad \text{--- (2)}$$

$$\Rightarrow \text{by eqn (1)} \Rightarrow \frac{X}{2-R} + X = \frac{X}{R}$$

$$\Rightarrow \frac{1}{2-R} + 1 = \frac{1}{R}$$

$$\Rightarrow (1+2-R)R = 2-R$$

$$\Rightarrow 3R - R^2 = 2 - R \Rightarrow R^2 - 4R + 2 = 0$$

$$R = \frac{4 \pm \sqrt{16-8}}{2} = \frac{4-2\sqrt{2}}{2} \quad [\because R < 1]$$

$$\boxed{R = 2 - \sqrt{2}}$$

hence

$$\frac{CE}{ED} = \frac{R}{1-R} = \frac{2-\sqrt{2}}{\sqrt{2}-1} = \frac{\sqrt{2}(\sqrt{2}-1)}{\sqrt{2}-1} = \sqrt{2}$$

Ans.

66

Total length = l , Total Resistance = R

Fraction x of length = lx , Remaining length = $l(1-x)$

Resistance of this length = Rx

Remaining Resistance = $R - Rx = R(1-x)$

Final length l_2

$$l_2 + l(1-x) = \frac{3}{2}l$$

$$\Rightarrow \boxed{l_2 = \frac{l}{2} + lx}$$

but $\frac{R_1}{R_2} = \frac{l^2}{l_2^2}$ (\because Volume const.)

$$\Rightarrow R_2 = \frac{l^2 (\frac{l}{2} + lx)^2}{x^2 l^2} \cdot Rx = \frac{(1+2x)^2 R}{4x}$$

but It's given $R_2 + R(1-x) = 4$ (original Resistance)

$$\Rightarrow R_2 + R(1-x) = 4R$$

$$\Rightarrow \frac{(1+2x)^2 R}{4x} + R(1-x) = 4R$$

$$\Rightarrow (1+2x)^2 + 4x(1-x) = 16x$$


$$\Rightarrow 1 + 4x^2 + 4x + 4x - 4x^2 = 16x$$

$$\Rightarrow 8x + 1 = 16x$$

$$\Rightarrow 8x = 1 \Rightarrow \boxed{x = \frac{1}{8}} \text{ Ans.}$$

67

Equivalent circuit can be represented by

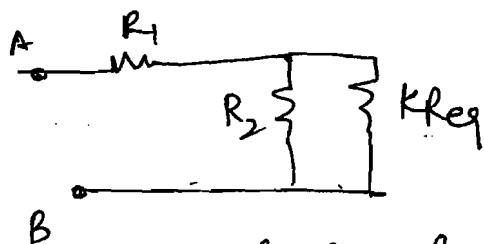

$$R_{eq} = R_1 + \frac{R_2 K_{eq}}{R_2 + K_{eq}}$$

($\because K = \frac{1}{2}$ given)

$$\Rightarrow R_{eq} R_2 + \frac{R_{eq}^2}{2} = R_1 R_2 + \frac{R_1 R_{eq}}{2} + \frac{R_2 R_{eq}}{2}$$

Let $R_{eq} = x$

$$\Rightarrow \frac{x^2}{2} + \frac{x}{2}(R_2 - R_1) - R_1 R_2 = 0$$

$$\Rightarrow x^2 + x(R_2 - R_1) - 2R_1 R_2 = 0$$

$$\Rightarrow x = \frac{(R_1 - R_2) \pm \sqrt{(R_2 - R_1)^2 + 8R_1 R_2}}{2}$$

$$\Rightarrow x = R_{eq} = \frac{(R_1 - R_2) + \sqrt{R_1^2 + R_2^2 + 6R_1 R_2}}{2}$$

68 Resistivity of Semiconductor decreases with increase in temperature. Effect of heating a semiconductor frees additional electrons (and holes); at high temp. more charge carriers.

69 Copper is conductor and Germanium is semiconductor.

70 Potential difference across $20\Omega = 20 \times 0.3 = 6$ Volt

$$\text{Current in } 15\Omega = \frac{6}{15} = 0.4 \text{ Amp}$$

$$\text{Hence current in } R_1 = 0.8 - (0.4 + 0.3) \\ = 0.1 \text{ Amp.}$$

by Ohm's law
 $(0.1)R_1 = 6$ (parallel combination)

$$\Rightarrow \boxed{R_1 = 60\Omega} \quad \text{Ans:}$$

71

$$R_{eq} = 60 + \frac{120 \times 60}{120 + 60}$$

$$= 60 + 40 = 100\Omega$$

$$\text{Hence } i = \frac{120}{100} = 1.2 \text{ Amp}$$

$$\text{Potential drop across } R_1 = iR_1 = 1.2 \times 60 = 72 \text{ V}$$

Hence potential drop across voltmeter

$$= 120 - 72 = 48 \text{ V}$$

72

When S_2 is closed, R_{eq} is ~~less~~ ^{more} than when S_1 is closed. ~~so more current~~. So less current. Hence potential drop across 'R' is less than case I. So when potential drop across R is less, across $6R$ is more.

$$\text{So } V_2 > V_1.$$

When both S_1 and S_2 are closed. R_{eq} is least among three cases. So current through circuit is greater than case I and case II. So potential drop across resistor 'R' is greater hence remaining potential difference (potential difference across $3R$ & $6R$) is less.

$$\text{So } V_2 > V_1 > V_3$$

[V_3 reading is least]

73

current is same. In parallel, two resistances are given.


∴ Rg = 20 Ω

74

deflection θ reduced to one fifth

current I in Galvanometer, becomes I/5


'I × θ'

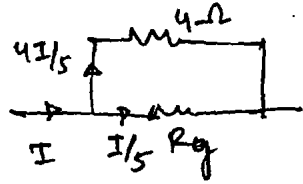


$I/5 R_g = \frac{4\Omega}{5} \times 4$

$R_g = 16 \Omega$

Now

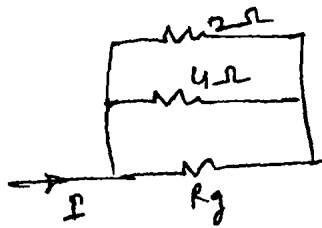

=

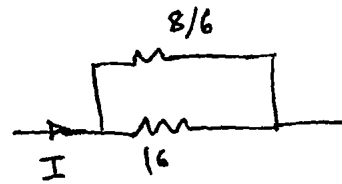

current in Galvanometer = $\frac{8/6 I}{8/6 + 16} = \frac{8 I}{8 + 96} = \frac{I}{13}$

deflection θ becomes θ/13.

reduction in deflection w.r.t. 'when shunted with 4Ω only'

$Z = \frac{\theta}{5} - \frac{\theta}{13} = \frac{8\theta}{65}$


deflection when shunted with 4Ω = θ/5

hence $Z = \frac{8}{13} \left(\frac{\theta}{5} \right)$

= 8/13 of the deflection when shunted with

4Ω only.

75

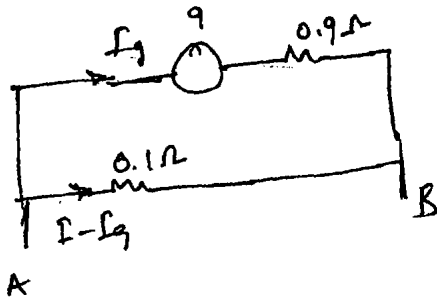

$(I - I_g) 0.1 = (9.9) I_g$ [parallel combination]

$\Rightarrow 10 I_g = I/10$

$\Rightarrow I = 100 I_g$

$= 100 \times 10 \times 10^{-3}$

$I = 1 \text{ Amp}$

76

$$\text{Total resistance} = 90 + 910 = 1000 \Omega$$

$$I = 10 \text{ mA}$$

$$\begin{aligned} \text{So potential diff} &= 1000 \times 10 \times 10^{-3} \\ &= 10 \text{ Volts} \end{aligned}$$

$$\text{least count} = 0.1 \text{ V}$$

$$n(\text{L.C.}) = 10$$

$$n = \frac{10}{0.1} = 100 \quad \text{Ans.}$$

77

$$(R + 20)(0.10) = 12$$

$$\Rightarrow R + 20 = \frac{1200}{10}$$

$$\Rightarrow R = 100 \Omega$$

(current in resistor and ammeter is same)

78 | Nearly ideal voltmeter has very high resistance so very low current. Hence no current so emf is the voltmeter reading. $i \approx 0$

79

by putting a voltmeter of finite resistance. $R_{eq} \downarrow$
hence $I \uparrow$, so more drop across ammeter so voltmeter will measure less

$$I > I_0, \quad V < V_0$$

80

when $i = 0$, voltmeter will measure only emf

by graph $V = y = \text{EMF}(E)$ — (1)

when $V = 0$ that means $E - ir = 0$

but by graph $V = 0$ when $i = x \Rightarrow E - x r = 0$

$$\Rightarrow y = x r \quad (\because y = E) \quad \text{by eqn (1)}$$

$$\Rightarrow \boxed{r = y/x} \quad \text{Ans.}$$


81

small resistance will not change R_{eq} . Hence in series current is almost same.

82 |

High resistance in parallel will not change req. hence potential difference to be measured does not appreciably change.

83 |

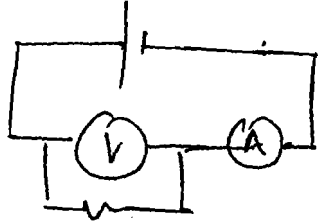

Req of circuit decreases, $I \uparrow$
Potential difference across ammeter increases. Hence potential diff. across voltmeter decreases.

Ammeter reading \uparrow
Voltmeter reading \downarrow

84 |

$$\frac{12}{x+y+r} = 1 \quad \text{--- (1)}$$

$$\frac{1}{x} = \frac{12}{x+y+r} \quad \text{--- (2)}$$

$$\frac{10}{x} = \frac{12}{x+r} \quad \text{(since } y \text{ is shorted) --- (3)}$$


by (1) and (2) $x = 1$

by (3) $10 = \frac{12}{1+r}$

$$1+r = 1.2$$

$$\Rightarrow \boxed{r = 0.2 \Omega} \quad \text{Ans.}$$

85 |

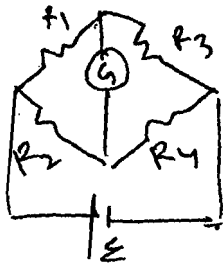

$$\text{If } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

then current through Galvanometer remains zero.

$$\frac{SR_1}{SR_2} = \frac{SR_3}{SR_4}$$

hence again current through Galvanometer is zero.

→ ~~It~~ doesn't depend on EMF

→ Can exchange position of battery and Galvanometer.

86 |

$$\frac{P}{S} = \frac{Q}{625} \quad \text{--- (1)}$$

$$\frac{Q}{S} = \frac{P}{676} \quad \text{--- (2)}$$

$$\frac{625}{S} = \frac{S}{676} \quad \text{by (1) and (2)}$$

$$\Rightarrow S^2 = 676 \times 625$$

$$\Rightarrow \boxed{S = 650 \Omega} \quad \text{Ans}$$

87

$$\frac{R_1}{40} = \frac{R_2}{60} \quad \text{--- (1)}$$

$$\frac{R_1}{50} = \frac{10R_2}{10+R_2} \quad \text{--- (2)}$$

by (1) $R_1 = \frac{2}{3}R_2$

\Rightarrow by (2) $\frac{2}{150}R_2 = \frac{R_2}{5(10+R_2)}$

$\Rightarrow 20+2R_2=30 \Rightarrow \boxed{R_2=5\Omega} \Rightarrow \boxed{R_1=10/3\Omega}$

88

potential gradient = $\frac{6}{1}$

hence for zero deflection

$(6)(AC) = 4$

$AC = 4/6 = 2/3 \text{ m}$ Ans

89

Initially $\frac{12}{x} = \frac{18}{100-x}$

$\Rightarrow 1200 = 30x$

$\Rightarrow x = 40 \text{ cm}$

Now $\frac{12}{y} = \frac{8}{100-y}$

$\Rightarrow 1200 = 20y$

$\Rightarrow y = 60 \text{ cm}$

J have to be moved by $60 - 40 = 20 \text{ cm}$.

90

$i = \frac{11}{10+1} = 1 \text{ amp}$

Potential gradient = $\frac{\text{potential drop across wire}}{\text{length}} = \frac{IR}{10}$

$= \frac{1 \times 10}{10} = 1 \text{ V/m}$

91

x (potential gradient) = $\frac{\text{potential drop across wire}}{\text{length}}$

$(\frac{1}{3})x = \epsilon \Rightarrow x = 3\epsilon/l$

potential diff across wire = 3ϵ

now length becomes $3l/2$

x' (New gradient) = $\frac{3\epsilon}{(3l/2)} = 2\epsilon/l$

$(\frac{2\epsilon}{l}) \times (y) = \epsilon \Rightarrow y = l/2$ Ans:

$l/2$ is distance of balance point.

92

$$i = \frac{\mathcal{E}}{10r}$$

Potential diff across potentiometer = $i(9r)$

$$= \frac{9\mathcal{E}}{10}$$

$$\text{potential Gradient} = \frac{9\mathcal{E}}{10L}$$

$$\left(\frac{9\mathcal{E}}{10L}\right) \times AJ = \mathcal{E}/2$$

$$\Rightarrow AJ = \frac{5L}{9} \quad \underline{\text{Ans}}$$

93

Can't find a balance point, because along wire from A to B potential decreases but from connecting battery a point with higher potential is needed. So it's not possible.

94

$$\mathcal{E}_{\text{eq of cells}} = \frac{2(6) - 4(2)}{8} = \frac{1}{2} \text{ Volt}$$

$$\text{Resistance of potentiometer wire} = 4 \times 4 = 16 \Omega$$

$$i = \frac{12}{16+8} = \frac{1}{2} \text{ Amp}$$

$$\text{potential Gradient} = \frac{(\frac{1}{2}) \times 16}{4} = 2 \text{ V/m}$$

$$\underline{\text{Hence}} \cdot 2(y) = \frac{1}{2} \quad [\text{At balance point}]$$

$$\Rightarrow \boxed{y = \frac{1}{4}} \Rightarrow y = 25 \text{ cm}$$

95

Initially given balance point is $l = L/2$

$$\text{(Potential Gradient)} \frac{L}{2} = 6 \quad \text{--- (1)}$$

$$\Rightarrow \left(\frac{\mathcal{E}}{L}\right) \left(\frac{L}{2}\right) = 6 \Rightarrow \boxed{\mathcal{E} = 12 \text{ V}}$$

Now If S_2 is closed



terminal voltage of cell

$$= 6 - ir$$

$$\Rightarrow 6 - \left(\frac{6}{10+r}\right)r = \left(\frac{12}{L}\right) \times \frac{5L}{12}$$

$$\Rightarrow \frac{60}{10+r} = 5$$
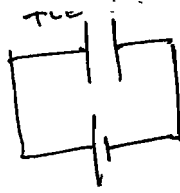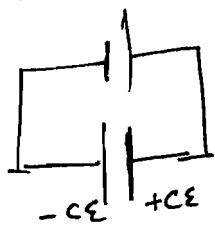
$$\Rightarrow 50 + 5r = 60 \Rightarrow \boxed{r = 2 \Omega}$$



Charge flown through
battery = $2CE$

$$\text{Work done by battery} = E(2CE) = 2CE^2$$

$$\text{Energy stored now} = \frac{Q^2}{2C} = \frac{1}{2}CE^2$$

$$\text{Energy stored before} = \frac{1}{2}CE^2$$


Hence produced
= Work done by
battery

$$\text{Heat produced} = 2CE^2 = 4(\text{Energy stored in capacitor})$$

Solutions

Ex-II

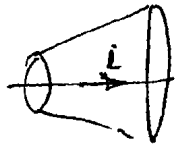Since there is no accumulation of charge, Hence current is same.



$I = n e A v_d$


$\therefore A \uparrow \text{ so } v_d \downarrow$

[carrier density is const for a metallic conductor]

2

Ammeter must be in series but voltmeter must be in parallel with resistor.

3

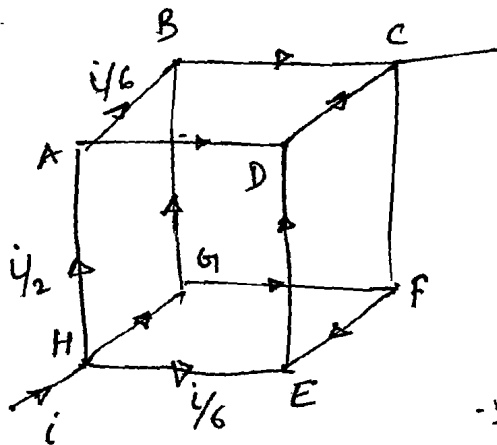

$i_{AB} = i/6, i_{DC} = 2i/3,$

$i_{HA} = i/2, i_{GF} = i/6, i_{HE} = i/6$

by KCL we can find currents as shown

$i_{HG} = i - (i/2 + i/6) = i/3$

$\therefore i_{AB} = i/6$

$i_{AD} = i - (i/2 + i/6) = i/3$

$\therefore i_{DC} = 2i/3, i_{ED} = 2i/3 - i/3 = i/3$

$i_{FE} = i/3 - i/6 = i/6$ (KCL at junction E)

$\therefore i_{GF} = i/6 \therefore i_{GB} = i_{HG} - i_{GF} = i/3 - i/6 = i/6$

$\therefore i_{BC} = i/6 + i/6 = i/3$

$\therefore \text{current in } CF = 0$

4

i is same in series hence more R, more power, more brightness

$R = \frac{V^2}{P}$

$\therefore P$ is same.


If marked voltage is high, R is high

$\therefore \text{brightness} \propto R \propto V^2$


Ans.

5

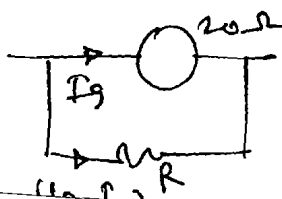To convert into ammeter, resistor should be connected across it.



$(10 - I_g)R = I_g(20)$

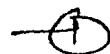

Given for 0.2 V galvanometer - shows full deflection (I_g)

$$I_g(20) = 0.2$$

$$\Rightarrow I_g = \frac{1}{100} \text{ Amp}$$

by eqⁿ ①

$$(10 - I_g)R = \frac{20}{100}$$

$$R = \frac{20}{100 \times (10 - I_g)} \approx \frac{20}{100 \times 10} = 0.02 \Omega$$

Aus:

6

$$H = \frac{V^2}{R} t$$

Heat developed in time 't' is doubled if Resistance becomes half of the initial.

$$R' = \frac{\rho L'}{A'}$$

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi R^2}$$

$$\therefore R' = R/2 \quad \text{If}$$

both the length and the radius of wire are doubled.

$$R' = \frac{\rho(2L)}{\pi(2R)^2} = \frac{1}{2} \left(\frac{\rho L}{\pi R^2} \right) = R/2$$

Aus:


7

this is charging of battery

Potential diff across points A and B = $\mathcal{E} + ir$
current flows from positive to -ve terminal

$$V_A - V_B = \mathcal{E} + ir \Rightarrow V_A > V_B$$

8

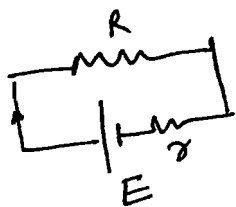

When current is zero, potential difference across resistor is \mathcal{E}

by graph we can find $\mathcal{E} = 10 \text{ Volt}$

$$\text{When } V = 0 \Rightarrow \mathcal{E} - ir = 0$$

$$\Rightarrow \mathcal{E} = ir$$

$$\Rightarrow 10 = (2)r$$

$$\Rightarrow \boxed{r = 5 \Omega}$$

[$i = 2$ when $V = 0$ by graph]

Aus:

Max^m current which

$$\text{can be taken} = \frac{10}{5} = 2 \text{ A}$$

9

parallel combination decreases R_{eq}

$$\therefore R_1 < R$$

series combination increases R_{eq}


$$\therefore R_2 > R$$

10

Max^m current can go is 10A. [otherwise fuse will melt]


If they are in series
current same the combination
acts as fuse of rating 10A

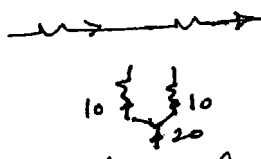If they are in parallel 20A current can go through both
since they are identical. In parallel, the combination
acts as fuse of rating 20A.



11

Equivalent circuit for both situation

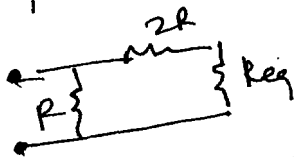

$$\therefore R_{eq} = x$$

$$R_{eq} = \frac{(2R + R_{eq})R}{3R + R_{eq}}$$

$$\Rightarrow x = \frac{(2R + x)R}{3R + x}$$


$$\Rightarrow 2R^2 + xR = 3Rx + x^2$$

$$\Rightarrow x^2 = 2R^2 - 2Rx$$

$$\Rightarrow x^2 + 2Rx - 2R^2 = 0$$

$$\Rightarrow x = (\sqrt{3} - 1)R$$

$$\therefore xy = 2R^2$$

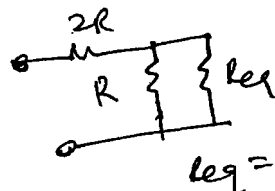

$$R_{eq} = y$$

$$R_{eq} = 2R + \frac{R R_{eq}}{R + R_{eq}}$$


$$\Rightarrow 2Ry + 2R^2 + \frac{yR}{R + y} = y^2 + yR$$

$$\Rightarrow y^2 - 2Ry - 2R^2 = 0$$

$$\Rightarrow y = \frac{2R \pm \sqrt{4R^2 + 8R^2}}{2}$$

$$\Rightarrow y = (\sqrt{3} + 1)R$$

12

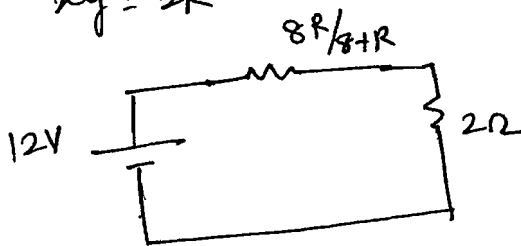

power through $2R$ is max
when i is max^m


when $\frac{8R}{8+R}$ is min^m

min value is zero when $R=0$

hence at $R=0$ power in $2R$ is max^m.
at $R=0$, current will not go through $8R$. ($R=0$ will
behave like zero resistance) $i = \frac{12}{2} = 6$

13]

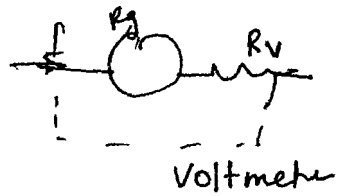The resistance will be largest for series combination
hence In voltmeter resistance of device will be more




I is same hence more R_v , more range of voltmeter.
so more is the range more is the resistance of device

$$I(R_g + R_v) = \text{Range of voltmeter} \quad (R_g + R_v)$$

14]

An ammeter should have small resistance otherwise current in circuit will change.
Similarly large resistance of voltmeter does not change potential to ~~be~~ be measured appreciably.

15]

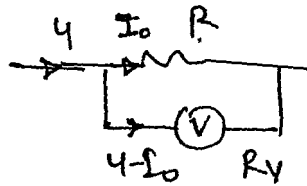

$$I_0 R = (4 - I_0) R_v = 20$$

$$\Rightarrow 4 - I_0 = \frac{20}{R_v}$$

$$I_0 = 4 - \frac{20}{R_v}$$

$$\Rightarrow I_0 R = 20$$


$$\Rightarrow R = \frac{20}{4 - \frac{20}{R_v}}$$

hence R is greater than 5Ω

as $R_v \rightarrow \infty$ $R \rightarrow 5\Omega$ (min^m possible R)

16]

for Voltmeter

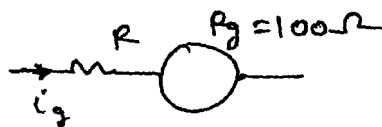

$$(100 + R) (5 \times 10^{-6}) = 10V$$

$$\Rightarrow (100 + R) 5 = 10^6$$

$$\Rightarrow 500 + 5R = 10^6$$

$$\approx 5R = 10^6 \Rightarrow R = \frac{(10^3)(10^3)}{5} = 200k\Omega$$

Similarly for 50V range voltmeter


$$(100 + R) \times (5 \times 10^{-5}) = 50V$$

Hence $R > 200k\Omega$

$$R = (10^6 - 100)\Omega$$

for Ammeter

Resistance should be in parallel.

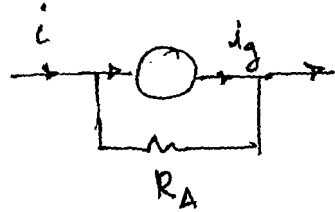

$$i_g R_g = R_A (i - i_g)$$

$$\Rightarrow 100 \times 50 \times 10^{-6} \approx i R_A$$

$$\Rightarrow R_A = \frac{5 \times 10^{-3}}{i}$$

$$\text{If } i = 5 \text{ mA}$$

$$R_A = 1 \Omega$$

Ans:

17

~~Measured~~

Potential drop across potentiometer wire should be greater than emf to be measured. For balance to be obtained positive terminals of both E_1 and E_2 or -ive terminals must be joined to one end of potentiometer wire.

18

Potential drop across potentiometer wire when $R = 120 \Omega$

$$= \left(\frac{20}{5 + 120 + 75} \right) \times 75 = 7.5 \text{ V}$$

hence potential difference can be measured

5V, 6V and 7V.

19


r does not play any role at balance point.

If $R \gg R_0$ in this case less potential drop across potentiometer wire.

20

number of free electrons remain same in a conductor.

21

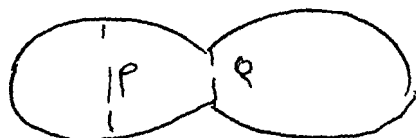

(a) current through conductor is same throughout.

$$(b) \quad j = -E \Rightarrow E = \frac{j}{A_0}$$

Same No. of free electrons are crossing at Q and at P. (Current same)
 ∴ Number of electrons crossing (per unit time) same
 per unit area of cross-section at P is less than that at Q

Rate of Heat Generated per unit time at Q


$$i^2 R_Q$$

$$\therefore R_Q = \frac{\rho dx}{A_Q} \quad R_P = \frac{\rho dx}{A_P}$$

$$\therefore R_Q > R_P \quad [A_Q < A_P]$$

∴ Heat Generated per unit time at Q > Heat generated per unit time at P.

22

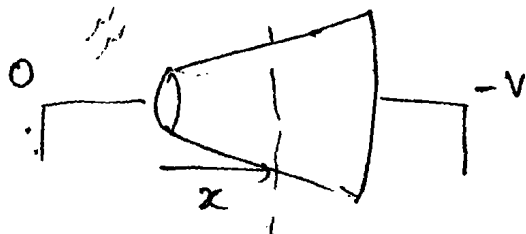

at a distance potential is -ive.

$$E = \frac{I}{A\sigma} \quad (\because j = \sigma E)$$


at a distance x

$$H = (dV) i$$

$$E = \left| \frac{dV}{dx} \right|$$

Rate of Generation of Heat per unit length

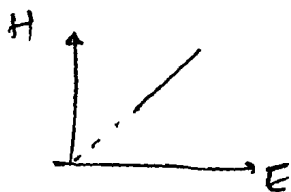
$$= \left(\frac{dV}{dx} \right) i = E i$$



Area at x of x

$$R = x \tan \theta + r_1$$

[θ and r_1 const.]

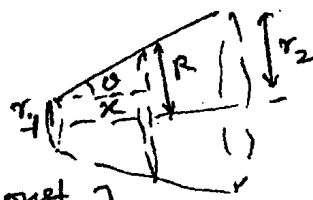


$$E = \frac{I}{\pi (x \tan \theta + r_1)^2 \sigma}$$

(E vs x is not linear)

similarly
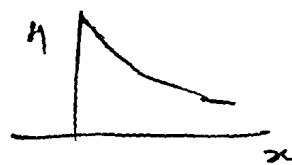
$$H = \frac{I^2}{\pi \sigma (x \tan \theta + r_1)^2}$$




23

Req ↑ current through battery ↓.


Potential diff remains same. Current through R remains same as $i = V/R$, hence the power by R.

24

~~Equivalent~~ Equivalent circuit can be represented by

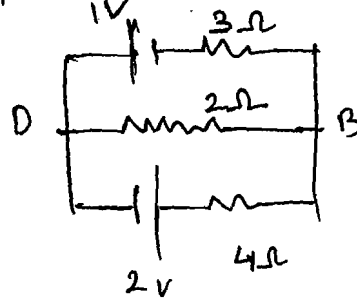

(Figure 1)

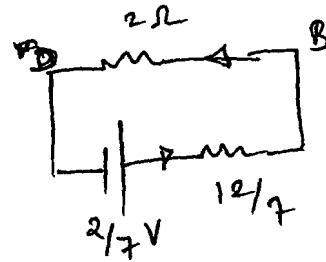

$$R_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} \quad r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$$


hence $i = \frac{2/7}{2 + 12/7} = \frac{2}{26} = \frac{1}{13}$

potential diff across $2\Omega = 2 \times \frac{1}{13} = \frac{2}{13}$

$\Rightarrow V_B - V_D = \frac{2}{13}$

$\Rightarrow V_D - V_B = -\frac{2}{13}$

Again by figure (2)

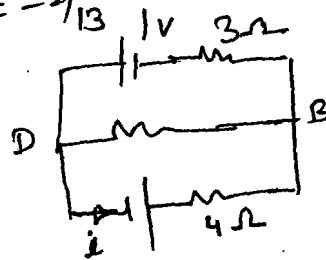


$V_D + 2 - 4i = V_B$

$\Rightarrow 2 - 4i = \frac{2}{13}$

$\Rightarrow i = \frac{6}{13}$

hence current through battery G and H is $\frac{6}{13}$ amp


for battery G

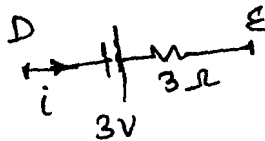

$V_D + 3 - 3i = V_E$

$\Rightarrow V_E - V_D = 3 - 3\left(\frac{6}{13}\right) = \frac{21}{13}$ Volt

for battery H

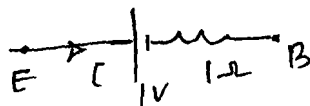

$V_E - 1 - 1(i) = V_B$


$V_E - V_B = 1 + \frac{6}{13} = \frac{19}{13}$

Ans


25

$$R_{eq} = 14 \Omega$$

$$j = \frac{28}{14} = 2 \text{ A}$$

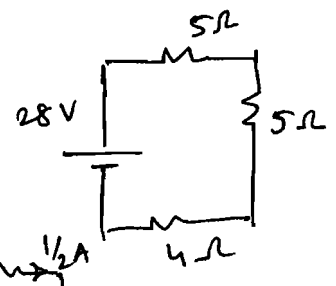

Now Again

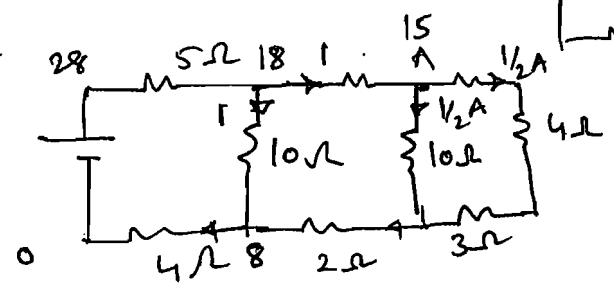

$$V_A - V_B = 15 - 8 = 7 \text{ Volt}$$

26

current is same, so charge crossing in a given time is same. free electron density for a conductor is const.

27

Average velocity of all electrons at an instant is zero. [since momentum is zero]

for a long time average velocity of a free electron is zero [since displacement becomes zero]

28

$$P = \left(\frac{E}{R+5} \right)^2 R \quad R \text{ increases from } 1 \Omega \text{ to } 5 \Omega$$

$$P = E^2 \frac{R}{(R+5)^2} = E^2 \left(\frac{R}{R+5} \right) \left(\frac{1}{R+5} \right)$$

Hence as
$$P = E^2 \left(\frac{1}{R+5} - \frac{5}{(R+5)^2} \right)$$

as $R \uparrow$ first term decreases as a less rate than second terms

hence as $R \uparrow$ $P \uparrow$

29

It will melt if current exceeds 8A.

30

In short circuited battery, hence potential diff. is also zero.

charging potential diff. = $E + iR$

discharging potential diff = $E - iR$

terminal potential diff = E

Ex-III
Comprehension-I

$$P = 1000 \text{ W}$$

$$V = 220 \text{ Volt}$$

1. $i = \frac{P}{V} = 4.545 \approx 4.55 \text{ A}$

2. $R = \frac{V^2}{P} = \frac{(220)^2}{1000} = 48.4 \Omega$

3. Power given = 1 kW = 1000 W

4. Heat produced in cal/sec

$$= \frac{1000}{4.18} \approx 239.2 \text{ Cal/sec}$$

Ans: $\approx 240 \text{ cal/sec}$

5.

$$Q = mL$$

$$\Rightarrow (240) \times 60 = m(540) \quad (\because t = 60 \text{ sec})$$

$$\Rightarrow m = \frac{240}{9} = \frac{80}{3} \text{ gms} \quad \underline{\text{Ans}}$$

Comprehension-II

6.

$$\alpha = -\frac{n}{T} \quad \alpha = \frac{dP}{PdT}$$

$$\therefore \int -\frac{n dT}{T} = \int \frac{dP}{P}$$

$$\Rightarrow -n \ln T = \ln P + \ln k$$

$$\Rightarrow T^{-n} = Pk \quad \uparrow \text{(const. of integration)}$$

$$\Rightarrow P = \frac{1}{k} T^{-n} \quad \text{where } a = \frac{1}{k}$$

$$\Rightarrow \boxed{P = a T^{-n}} \quad (a)$$

Ans.

7.

$$n = -\alpha T = 5 \times 10^{-4} \times 294 = 0.147$$

$$\therefore a = (3.5 \times 10^{-5}) T^n$$

$$= (3.5 \times 10^{-5}) (294)^n = 8.07 \times 10^{-5}$$

Ans.

8. calculation of 'n' has been done in last question

$$n = 0.147$$

9. $T_1 = -196 + 273 = 77 \text{ K}$

$$T_2 = 573 \text{ K}$$

$$\therefore a = 8 \times 10^{-5}, \quad n = 0.147$$

$$\rho = a T^{-n}$$


$$\rho_1 = (8 \times 10^{-5}) (77)^{-0.147}$$

$$= 4.23 \times 10^{-5}$$

$$\rho_2 = (8 \times 10^{-5}) (573)^{-0.147}$$

$$= 3.15 \times 10^{-5} \quad \underline{\text{Ans}}$$

Comprehension - III

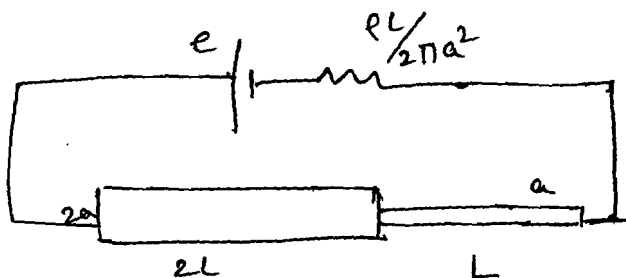

let say

$$\frac{RL}{2\pi a^2} = R$$

10. Resistance of potentiometer wire

$$R_1 + R_2 = \frac{\rho(2L)}{\pi(2a)^2} + \frac{\rho(L)}{\pi a^2} = \frac{3}{2} \frac{RL}{\pi a^2} = 3R$$

$$\begin{aligned} \text{Req of potentiometer wire + internal resistance} \\ = \frac{2\rho L}{\pi a^2} = 4R \end{aligned}$$

$$i = \frac{e}{4R}$$

Potential drop across potentiometer

$$= i(3R) = \frac{e}{4R} \times 3R = \frac{3}{4} e$$

= Max^m Voltage which can be balanced on the potentiometer wire

11. Max^m drop across first wire

$$= i(R_1) = \frac{e}{4R} \times R = e/4$$

So balance point will occur on second wire (for emf $e/2$)

So remaining ~~emf~~ drop ($e/2 - e/4$) must be on second wire so length required is x (say)


$$\left(\frac{e}{2} - \frac{e}{4}\right) = i \left(\frac{\rho x}{\pi a^2}\right)$$

$$\Rightarrow \frac{e}{4} = \frac{e}{4R} \cdot \frac{\rho x}{\pi a^2}$$

$$\Rightarrow x = \frac{\pi a^2 R}{\rho} = \frac{\pi a^2}{\rho} \times \frac{\rho L}{2\pi a^2} = L/2$$

hence balancing length = $2l + l/2 = 5l/2$ Ans

12.

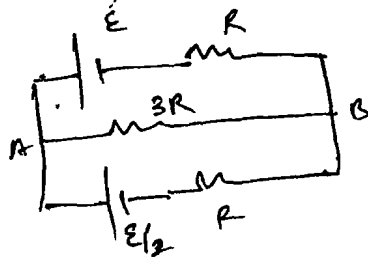


$$E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} = \frac{ER + \frac{E}{2}R}{2R} = \frac{3E}{4}$$

$$r_{eq} = R/2$$

hence current in potentiometer
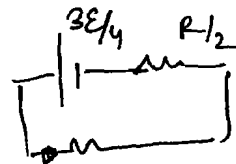
$$= \frac{(3E/4)}{(3R + R/2)} = \frac{3E}{14R}$$



$$V_A - V_B = \left(\frac{3E}{14R}\right) \times 3R = \frac{9E}{14}$$

Current through this cell


$$V_A - \frac{E}{2} - iR = V_B$$

$$\Rightarrow iR = \frac{9E}{14} - \frac{E}{2}$$

$$= \frac{9E - 7E}{14} = \frac{2E}{14}$$


$$\boxed{i = \frac{E}{7R}}$$

where $R = \frac{\rho L}{2\pi a^2}$ Ans

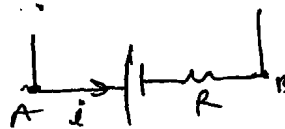

Comprehension - IV

13.

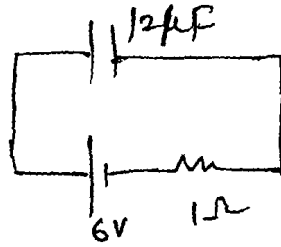

$$C = 12 \times 10^{-6}$$

$$RC = 12 \times 10^{-6}$$

$$\frac{t}{RC} = 1$$

$$i = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$= \frac{6}{1} e^{-1} = 2.207 = 2.21 \text{ A}$$

14.

$$P = Vi = 2.207 \times 6 = 13.24 \text{ W}$$

Ans

15. Heat = $i^2 R = 4.8708 \text{ W}$ $\left\{ \begin{array}{l} i = 2.207 \\ R = 1\Omega \end{array} \right.$

16. Rate at which energy stored in the capacitor is increasing

$$E = \frac{Q^2}{2C}$$

$$Q = CE(1 - e^{-t/RC})$$


$$\frac{dE}{dt} = \frac{2Q}{2C} \frac{dQ}{dt} = \frac{Q}{C} i$$

$$= \frac{CE(1 - e^{-1}) \cdot i}{C} = E(1 - e^{-1})(2.207)$$


$$= 6 \times (1 - 1/e) (2.207) = 8.3705 \text{ W}$$

Ans.

Comprehension - V

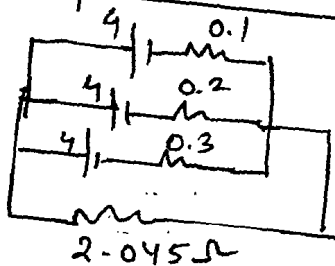

Equivalent circuit can be represented by

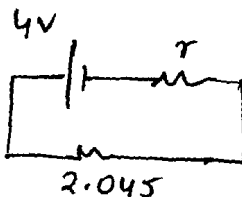

$$R = \frac{0.3 \times \left(\frac{0.1 \times 0.2}{0.1 + 0.2} \right)}{0.3 + \left(\frac{0.1 \times 0.2}{0.1 + 0.2} \right)} = \frac{3}{55} = 0.0545$$

17. Equivalent resistance for calculation of

$$\text{current} = 2.045 + 0.0545$$


~~$$= 2.099$$~~

$$= 2.1 \Omega$$

18. ϵ_{eq} voltage as shown = 4V $\therefore \epsilon_1 = \epsilon_2 = \epsilon_3 = 4V$

19. $\text{current} = \frac{4}{2.1} = 1.904 \text{ Amp}$

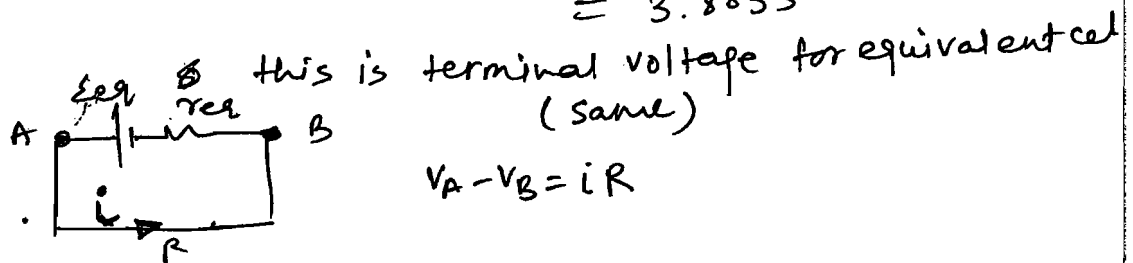20. potential drop across resistor = $(1.90) \times (2.045)$
 $= 3.8855$




21. for each cell terminal voltage is same as

$$V_A - V_B = 3.8855$$

Aus

Comprehension - VI

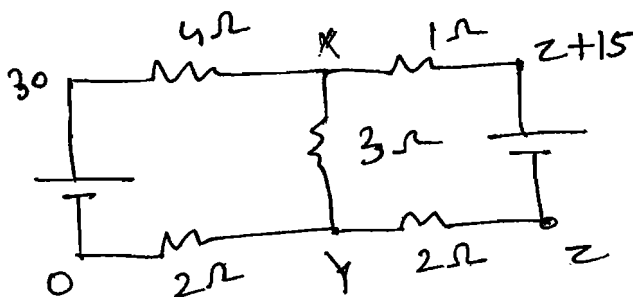

$$\frac{30-x}{4} = \frac{x-y}{3} + \frac{x-z-15}{1} \quad \text{--- (1)}$$

$$19x - 4y - 12z = 270$$

$$\frac{y-0}{2} + \frac{y-x}{3} = \frac{z-y}{2} \quad \text{--- (2)}$$

$$3z + 2x - 8y = 0$$

$$\frac{y-z}{2} = \frac{z+15-x}{1} \quad \text{--- (3)}$$

$$2x + y - 3z = 0$$

hence $x=8, y=6, z=4$ volt

22. current through 30V = $\frac{30-x}{4} = \frac{12}{4} = 3A$

23. current through 15V = $\frac{(2+15)-x}{1} = \frac{19-18}{1} = 1A$


24. from each battery current is leaving
hence No one is getting charged.

25. Total electrical power consumed

$$V_1 i_1 + V_2 i_2$$

$$= (30 \times 3) + (15 \times 1) = 90 + 15 = 105W$$

Comprehension - VIII

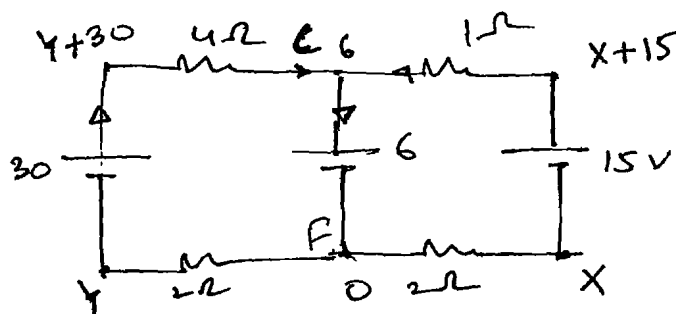

$$\frac{-Y}{2} = \frac{Y+2Y}{4}$$

$$\Rightarrow Y = -8$$

$$\frac{-x}{2} = \frac{x+9}{1}$$

$$\Rightarrow x = -6$$

current in BC = 4 Amp = $\left(\frac{22-6}{4}\right)$

in CD = $\frac{9-6}{1} = 3 \text{ Amp}$

current in ~~BC~~ CF branch = 4 + 3 = 7A

26. (A) $V_C - V_F = 6V$

current in CF flows from C to F.

27. both loop are independent.


Incorrect statement is (C)

28. only 6V is getting charged

29. current in branch CF = 4 + 3 = 7A

$6(7) = 42 = 115 \times 10 = 1150W$

Match the column

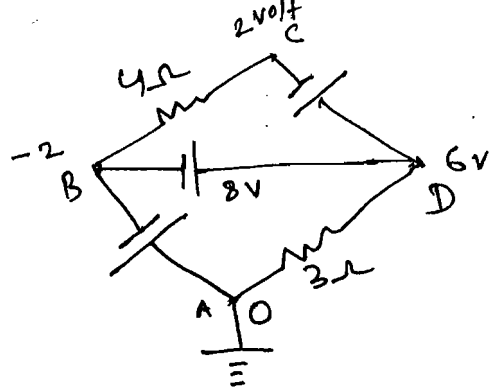

(a) least potential is of
B = -2 Volt

(b) The current through 3Ω resistor = $\frac{6-0}{3} = 2A$ from D to A.

(c) current through 4Ω resistor = $\frac{2-(-2)}{4} = 1A$ from C to B.

2. $RC = 3$, $E = 4V$ $t = 1sec$

$$(a) \frac{dq}{dt} = i = \frac{E}{R} e^{-t/RC} = \frac{4}{3 \times 10^6} e^{-1/3}$$

$$= 0.955 \times 10^{-6}$$

$$= 9.6 \times 10^{-7}$$

(b) Rate at which energy stored in capacitor = Power by cell - joule heat

$$= (3.8 - 2.7) \times 10^{-6}$$

$$= 1.1 \times 10^{-6}$$

(c) joule heat = $i^2 R$

$$= (9.6)^2 \times 10^{-14} \times 3 \times 10^{-6}$$

$$= 2.76 \times 10^{-6}$$

(d) Rate at which energy delivered by cell = Ei

$$= 3.84 \times 10^{-6}$$

Ans.

3.

When capacitor is fully charged

$$\begin{aligned} \text{Energy stored} &= \frac{1}{2} C (60)^2 \\ &= \frac{1}{2} \times \frac{0.1 \times 3600}{10^6} = 180 \text{ J} \end{aligned}$$

At any instant

current in 4Ω is I then current in 6Ω will be $I/3$ and in 3Ω be $2I/3$.Hence Ratio of Rate of heat dissipation. $4\Omega : 6\Omega : 3\Omega$

$$I^2 \cdot 4 : \frac{I^2}{9} \cdot 6 : \frac{4I^2}{9} \cdot 3$$

$$\Rightarrow 12 : 2 : 4$$


$$\Rightarrow 6 : 1 : 2$$

If total Heat produced = H then Heat produced by $4\Omega = 6H/9$ by $6\Omega = H/9$ by $3\Omega = 2H/9$

[but Heat = Energy of capacitor = 180 J]

 \therefore (a) Heat generated across $4\Omega = 120 \text{ J}$ (b) across $6\Omega = 20 \text{ J}$ (c) across $3\Omega = 40 \text{ J}$ (d) across $4\Omega + 6\Omega = 140 \text{ J}$

(4)

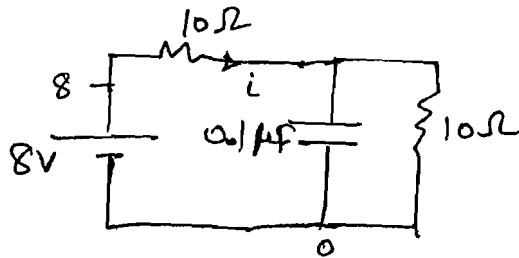

Remaining circuit is replaced by a 10Ω resistor.

In steady state NO current through capacitor.


$$I = \frac{8}{20} = 0.4 \text{ A}$$

$$\text{potential drop across capacitor} = 8 - (0.4)10 = 4 \text{ V}$$

hence

$$(A) \text{ charge on capacitor} = 0.4 \mu\text{C} \quad (q = CV)$$

(B) for current in AC branch

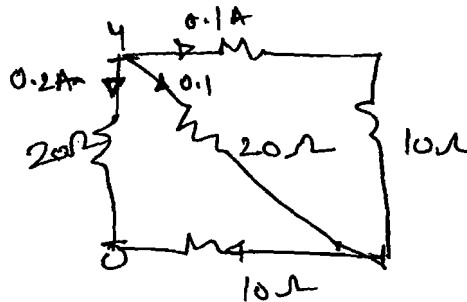

$$= 0.1 \text{ A}$$

(∵ equal parallel resistance)


(C) current in AB Branch

$$= \frac{4}{20} = 0.2 \text{ A}$$

(d) current in resistance between

$$E \text{ and } F = \frac{8-4}{10} = 0.4 \text{ A}$$

5

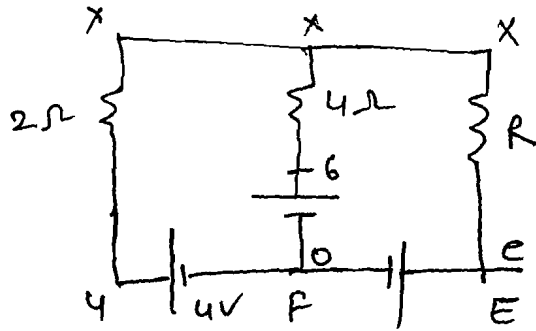

$$\frac{4-X}{2} = \frac{X-6}{4} + \frac{X-E}{R} \quad \text{--- (1)}$$

(A) current through 4Ω is zero $\Rightarrow X=6$
 hence by (1)

$$\Rightarrow -1 = \frac{6-E}{R}$$

$$\Rightarrow -R = 6-E$$

$$\Rightarrow e = 6 + R \quad \underline{e > 6 \text{ volt}}$$

(B) from F to c direction $X < 6$ volt
 by (1)

$$2R(4-X) = R(X-6) + 4X - 4E$$

$$\Rightarrow 8R - 2RX = RX - 6R + 4X - 4E$$

$$\Rightarrow 14R + 4E = (4+3R)X$$

$$\Rightarrow X = \frac{14R + 4E}{4 + 3R} < 6$$

$$\Rightarrow 14R + 4E < 24 + 18R$$

$$\Rightarrow 4E < 24 + 4R$$

$$\Rightarrow e < 6 + R$$

for $R=0$ $e < 6$

for diff R

hence

$$e = 6V$$

(a), (b), (c)

$$\text{or } e > 6V$$

but since R is finite

$e < \text{some finite value}$.

(C)

for c to f direction

$$e > R + 6$$

$$\min R = 0 \Rightarrow e$$

$$\text{hence } e > 6 \Omega$$

(D) current in 2Ω will be from B to A

$$\text{Pf } X > 4$$

$$\Rightarrow \frac{14R + 4e}{4 + 3R} > 4$$

$$\Rightarrow 14R + 4e > 16 + 12R$$


$$\Rightarrow 4e > 16 - 2R$$

$$\Rightarrow e > 4 - R/2$$

$$\min R = 0 \therefore e > 4$$



So for depending upon the value of R e can take any value from 0 to infinity.

Ex-IV Solutions

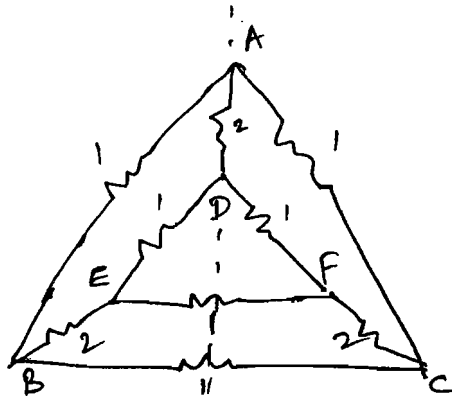


by symmetry, No current in resistor EF and BC

Equivalent circuit can be represented by

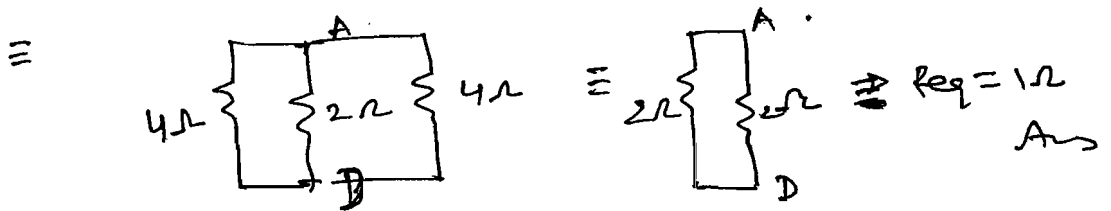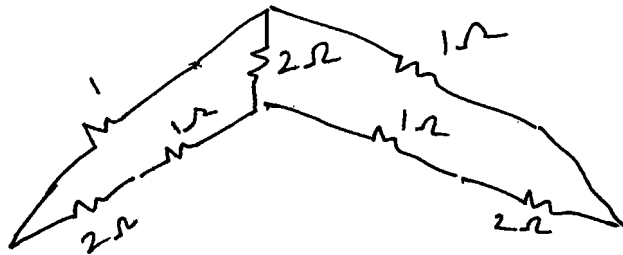

21

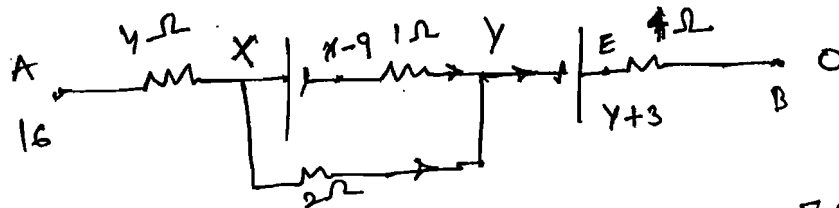

we have $\frac{16-x}{4} = \frac{(y+3)-0}{4}$ (1)

[Same current in branch AX and EB]

similarly $\frac{x-9-y}{1} + \frac{x-y}{2} = \frac{(y+3)-0}{4}$ (2) [at junction X]


by (1) $x+y=13$, by (2) $6x-7y-39=0$

$\therefore x=10, y=3$

Current through $2\Omega = \frac{10-3}{2} = \frac{7}{2} = 3.5A$ Ans.


3

Equivalent circuit for current

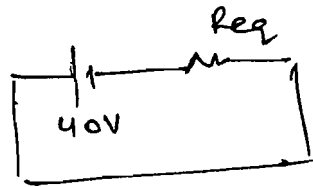

$$i = \frac{40}{16} = \frac{5}{2} = 2.5 \text{ Amp}$$

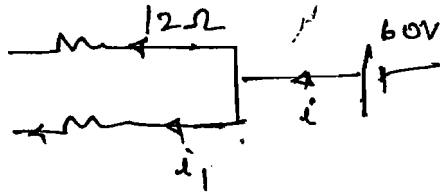
Now for voltmeter reading
current through 7Ω resistor



$$i_1 = \left(\frac{12}{48+12}\right)i = \frac{i}{5}$$


$$\therefore V = \left(\frac{i}{5}\right)7 = \frac{5}{2} \times \frac{1}{5} \times 7 = 3.5 \text{ Volt} \quad \underline{\text{Ans}}$$

for Req


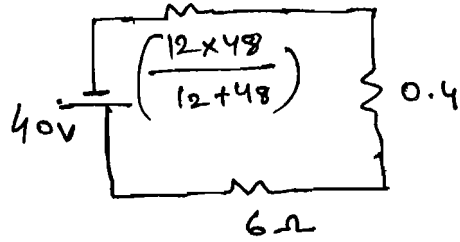



$$R_{eq} = 6 + \frac{48}{5} + \frac{4}{10} = 16\Omega$$

4


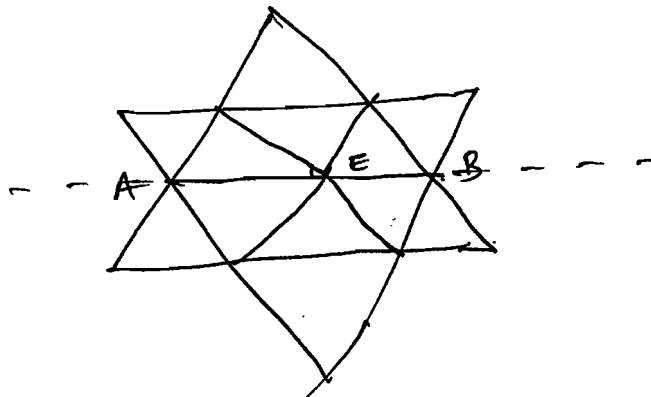


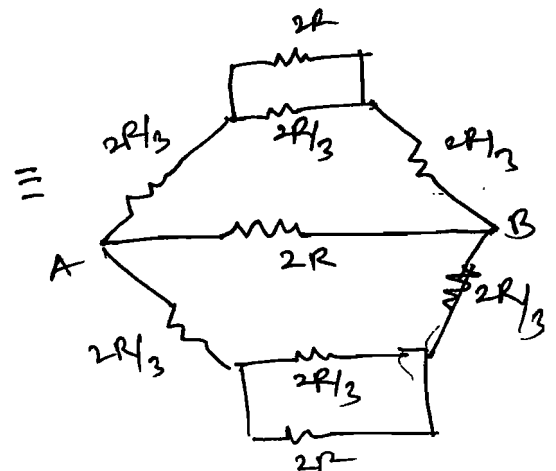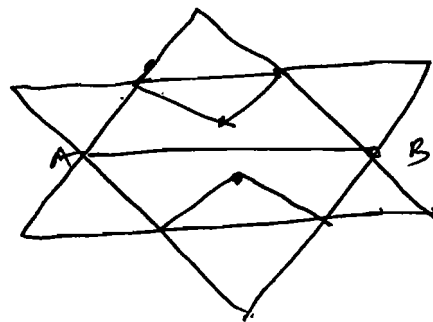by symmetry
we can disconnect
the junction E
as shown



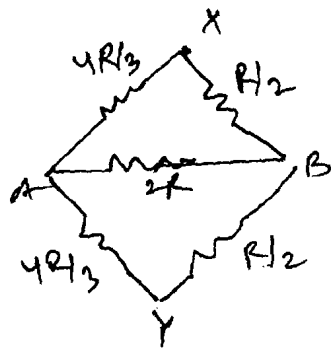

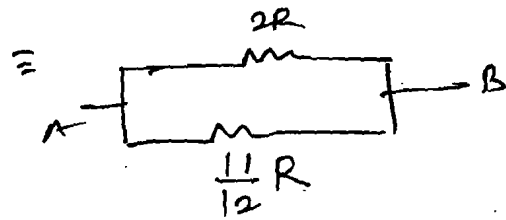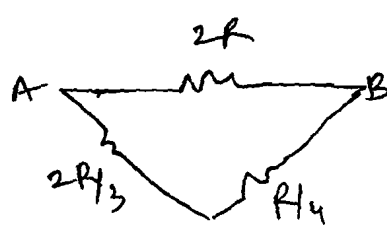
by symmetry again point X and Y are at same potential hence by folding.



$\therefore R = 1 \Omega$

$R_{eq} = \frac{2 \times \frac{11}{12}}{2 + \frac{11}{12}} = \frac{22}{35} \Omega$ Ans.

5

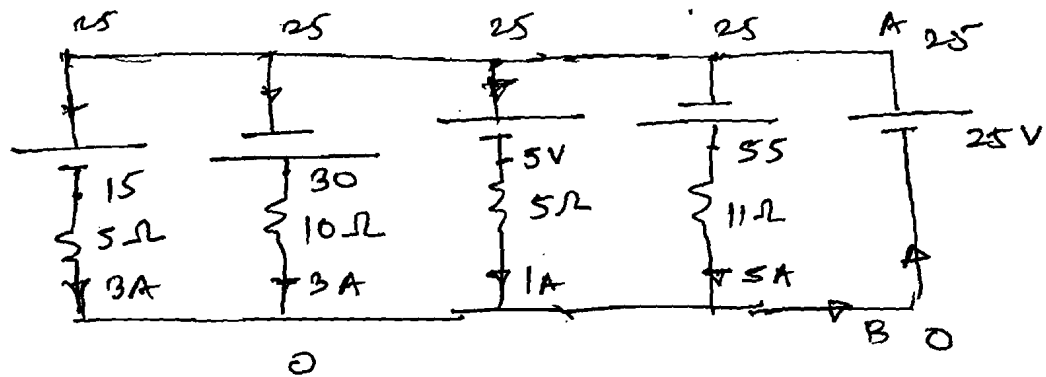

~~Assign~~ Assign potential A + B = 0 Volt hence at A potential = 25V similarly other points potentials are known.

Now current can be calculated by $V = IR$ in various branches as shown

Hence current through 25V = $3 + 3 + 1 + 5 = 12$ Amp.

Power supplied by 20V cell = $-(20)1 = -20$ W
(Since current is entering into battery)

6

by given condition

$$\left(\frac{E}{R_1 + r}\right)^2 R_1 \neq \left(\frac{E}{R_2 + r}\right)^2 R_2 \neq$$

$$\Rightarrow \frac{R_1}{(R_1 + r)^2} = \frac{R_2}{(R_2 + r)^2}$$

$$\Rightarrow \frac{R_2 + r}{R_1 + r} = \frac{\sqrt{R_2}}{\sqrt{R_1}}$$

\Rightarrow by componendo & dividendo

$$\Rightarrow \frac{R_1 + R_2 + 2r}{R_2 - R_1} = \frac{\sqrt{R_2} + \sqrt{R_1}}{\sqrt{R_2} - \sqrt{R_1}}$$


$$\Rightarrow (R_1 + R_2) + 2r = (\sqrt{R_2} + \sqrt{R_1})^2$$

$$\Rightarrow 2r = 2\sqrt{R_1 R_2}$$




$$\Rightarrow r = \sqrt{R_1 R_2}$$

Ans

7

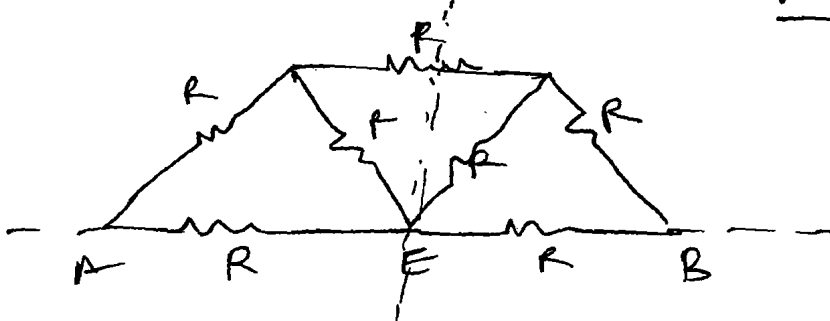


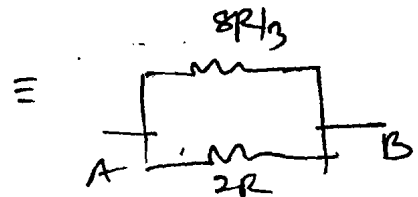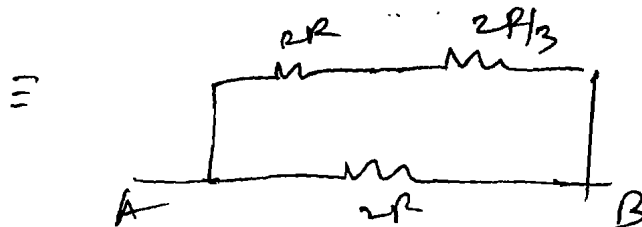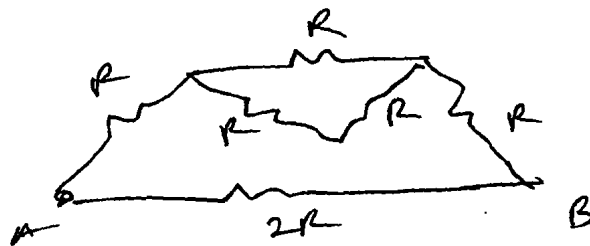by symmetry we can disconnect junction as shown



$$R_{eq} = \frac{(8R/3) \times 2R}{8R/3 + 2R} = \frac{16/3 R}{16/3} = \frac{8}{3} R$$

8

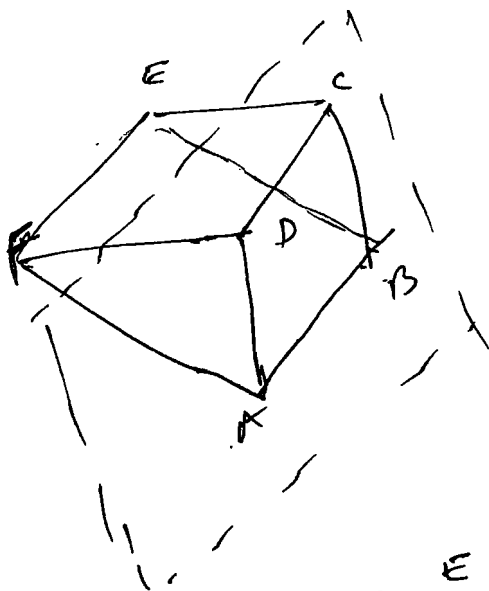

by plane of symmetry

We can say


current through

EC and FD is zero


hence ~~can~~ remove
can

EC and DF resistors.


Equivalent
Circuit can be
shown as

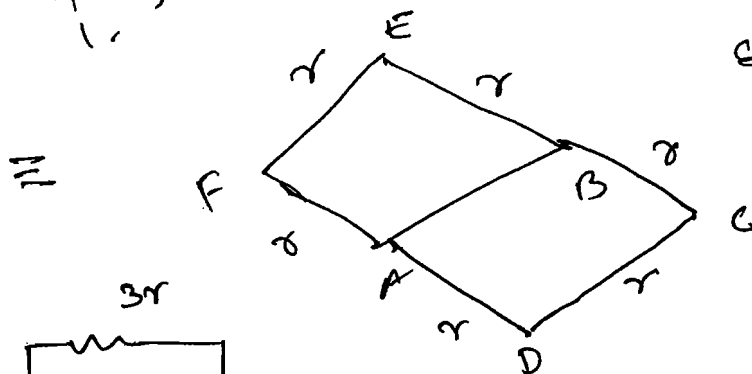

|||

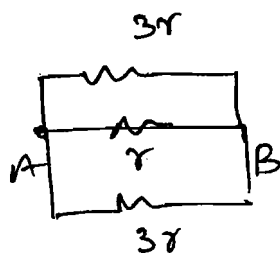


|||

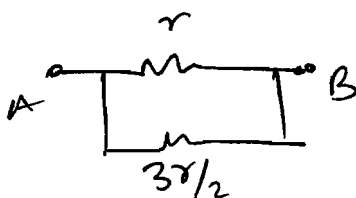

$$R_{eq} = \frac{\left(\frac{3r}{2}\right)r}{\frac{3r}{2} + r} = \frac{3r}{5} \quad \underline{\underline{Ans}}$$

9

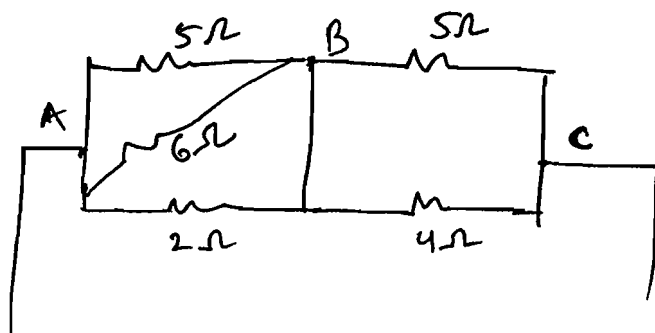

across BC
potential drop is
same


hence $P = \frac{V^2}{R}$

4Ω will produce
more power.

Similarly across AB 2Ω will produce more heat.
Now b/w 2Ω & 4Ω we have to compare which
one is producing more heat.

Let total current be I

Equivalent circuit can be represented by

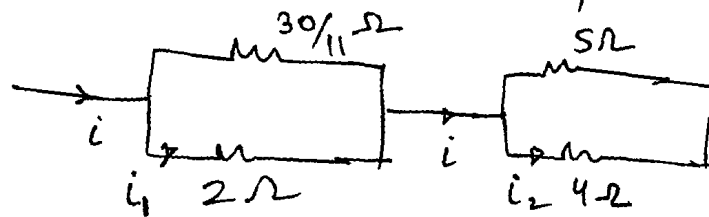

$$i_1 = \left(\frac{\frac{30}{11}}{\frac{30}{11} + 2} \right) i \quad i_2 = \left(\frac{5}{5+4} \right) i$$

$$= \frac{30}{52} i = \frac{15}{26} i \quad i_2 = \frac{15}{27} i$$

$H_1 =$ Heat in 2Ω produced $= \left(\frac{15i}{26} \right)^2 \times 2t = 0.665 i^2 t$


Heat produced in 4Ω (H_2) $= \left(\frac{15i}{27} \right)^2 \times 4t = 1.23 i^2 t$

$\therefore H_2 > H_1$

Heat produced in 4Ω is greater than heat produced in 2Ω .

\therefore since current through 4Ω is zero.

10

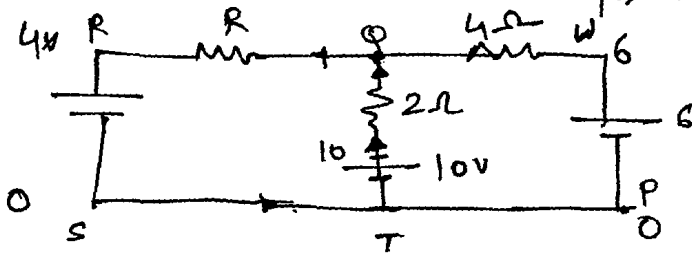

Assign voltage at point $P = 0$

Voltage at $W = 6V$

$V_Q = 6V$ also
(\because No current in 4Ω)

$V_S = V_T = 0$

\therefore Current in TQ branch $= \frac{10 - V_Q}{2}$

$$= \frac{10 - 6}{2} = 2 \text{ Amp} \quad \text{--- (1)}$$

Current in RQ branch $= \frac{V_Q - V_R}{R} = 2 \text{ Amp}$

$\Rightarrow \frac{6 - 4}{R} = 2 \text{ Amp}$

$\Rightarrow \underline{R = 1\Omega} \quad \text{Ans.}$

by eqn (1)

11

Initially - when both switches are open

$$i_1 = \frac{\epsilon}{450}$$

When both are closed

$$i_2 = \frac{\epsilon}{300 + \frac{100R}{100+R}}$$

[No current through 50Ω ∴ It is short-circuited]

∴ Reading of Ammeter is same

$$\therefore \frac{\epsilon}{450} = \left(\frac{\epsilon}{300 + \frac{100R}{100+R}} \right) \times \frac{R}{R+100}$$


$$\Rightarrow \frac{1}{450} = \frac{R}{300(R+100) + 100R}$$

$$\Rightarrow 400R + 30000 = 450R$$

$$\Rightarrow 50R = 30000 \Rightarrow R = \underline{600\Omega}$$

12

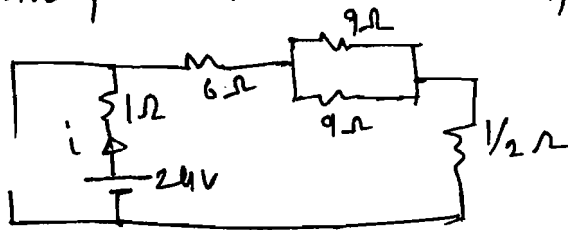S_1 must be open otherwise current will not go through resistors. Similarly S_2 & S_3 are open. Ans.



because for less current through battery, more should be the resistance.

$$\text{Current } i = \frac{24}{R_{eq}} \quad \left| \quad R_{eq} = 6 + \frac{9}{2} + \frac{1}{2} + 1\Omega \right.$$

$$i = \frac{24}{12} = 2 \text{ Amp} \quad \left| \quad \begin{aligned} &= 11 + 1 \\ &= 12\Omega \end{aligned} \right.$$

for potential diff. calculation
current in AB branch = 1 Amp.


$$\therefore V_{AB} = LR$$

$$= (1)(1\Omega) = 1 \text{ Volt}$$

[current 2A will be divided equally in two resistors ∴ both resistors are same]

.Ans

131




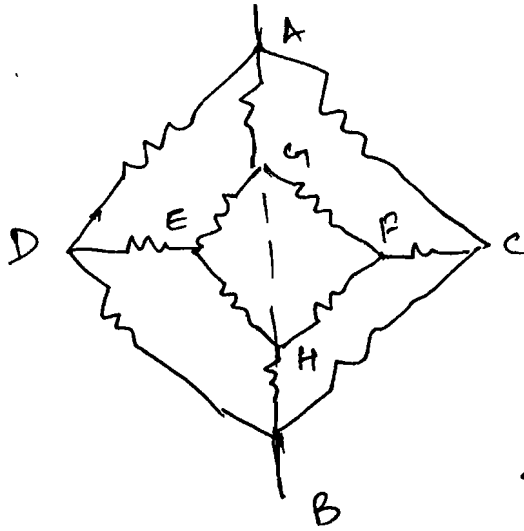


by symmetry

branches DE and CF will have no current.

hence can remove these resistance.

Equivalent circuit is given below

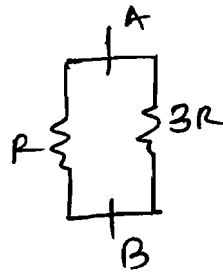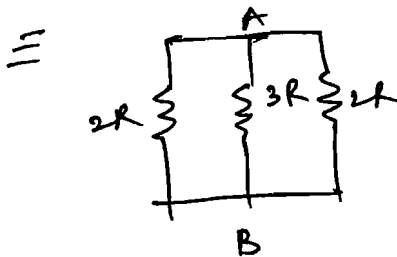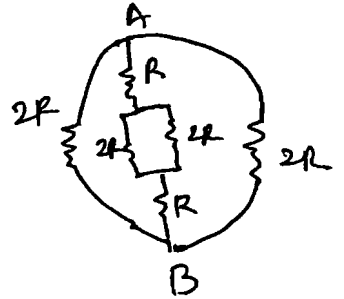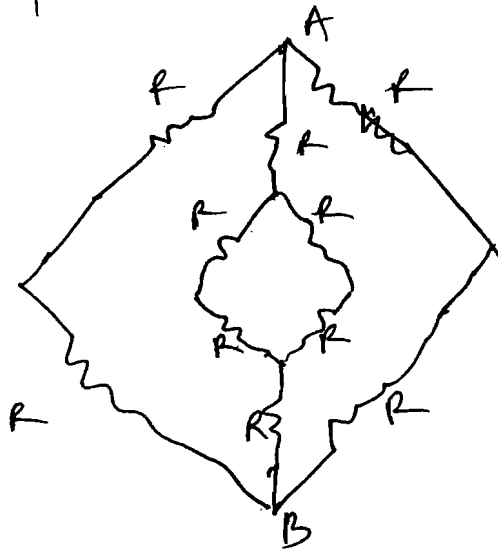

$$R_{eq} = \frac{3R^2}{3R + R}$$
$$= \frac{3}{4} R$$

$$\therefore R = 12 \Omega$$

$$R_{eq} = \frac{3}{4} \times 12 = 9 \Omega$$

Ans:

$$\text{potential gradient} = \left(\frac{\left(\frac{10}{20}\right) \times 10}{L} \right) = 5/L = \frac{5}{1} \text{ Volt/meter}$$

$$E_{eq}(\text{cell}) = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} \quad r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$$

$$= \frac{10 + 4}{6}$$

Wren during balance

$$\frac{14}{6} = (5) x$$

$$\Rightarrow x = \frac{14}{30} \text{ m} = \frac{1400}{30} \text{ cm}$$

$$= 46.666 \text{ cm}$$

$$= 46.67 \text{ cm} \text{ Ans}$$

15

$$\text{potential gradient} = \frac{\frac{10}{10} \times 10}{1} = 10 \text{ V/m}$$

potential drop across AC


$$= 10 \times 0.4 = 4 \text{ Volt}$$

by cell
potential drop = $E - ir$

$$5 - \left(\frac{5}{R+1} \right) 1 = 4$$


$$\Rightarrow 1 = \frac{5}{R+1}$$

$$\Rightarrow \underline{R = 4 \Omega}$$

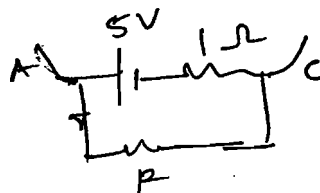

Ans

16

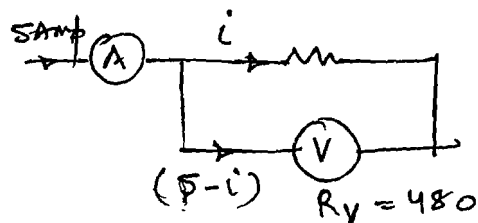

$$(5-i)(480) = i(R) = 96$$

$$\Rightarrow 5 \times 480 = (480 + R)i$$

$$\Rightarrow i = \frac{480 \times 5}{480 + R}$$

but $iR = 96$


$$\Rightarrow R = \frac{96 \left(\frac{480 + R}{480 \times 5} \right)}{480 \times R} \quad \left(\frac{480 \times 5}{480 + R} \right) R = 96$$

$$\Rightarrow 25R = 480 + R$$

$$\Rightarrow 24R = 480$$

$$\Rightarrow R = 20 \Omega \quad \underline{\text{Ans}}$$

17

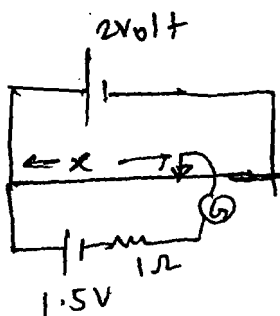

Potential Gradient
 $= \frac{2}{10} \text{ V/m}$

for zero deflection $\left(\frac{2}{10} \right) z = 1.5$

$$\Rightarrow z = \frac{15}{2} = 7.5 \text{ m}$$


(a) When 5 ohm is placed in series $i = \frac{2}{35} \text{ Amp}$

Potential Gradient = $\left(\frac{\frac{2}{35} \times 30}{10} \right) \text{ V/m}$

$$\left(\frac{6}{35} \right) z = 1.5$$

$$\Rightarrow z = 8.75 \text{ m}$$


(b)

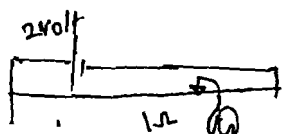

$$\left(\frac{2}{10} \right) z = \varepsilon - iR$$

$$= 3 - \left(\frac{3}{2} \right) 1$$

181

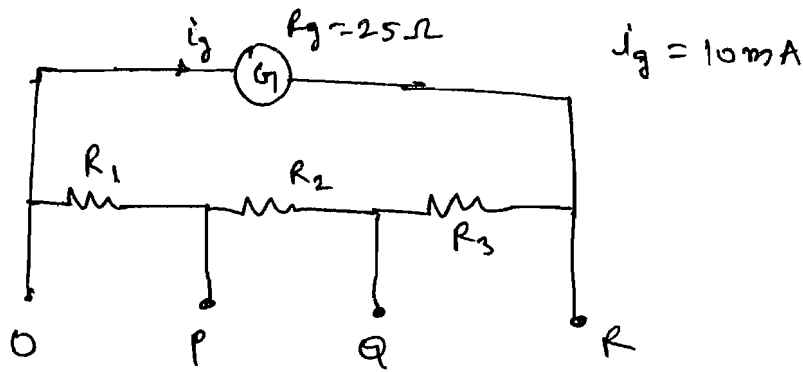

We can have following eqⁿs (taking current in mA)

$$10(25 + R_2 + R_3) = (10^4 - 10)R_1 \quad \left[\begin{array}{l} \text{When terminals} \\ \text{O and P are taken} \end{array} \right]$$

$$\Rightarrow 25 + R_2 + R_3 = (10^3 - 1)R_1 \quad \text{--- (1)}$$

$$25 + R_3 = (10^2 - 1)(R_1 + R_2) \quad \left[\begin{array}{l} \text{O and Q are taken} \end{array} \right]$$

$$\text{--- (2)}$$

$$25 = (10 - 1)(R_1 + R_2 + R_3) \quad \text{--- (3)}$$

by eqⁿ (2)

$$99(R_1 + R_2) = 25 + R_3 \quad \text{--- (4)}$$

$R_1 + R_2$ by eqⁿ (3)
put in eqⁿ (4)

$$R_1 + R_2 = \frac{25}{9} - R_3$$

$$99\left(\frac{25}{9} - R_3\right) = 25 + R_3$$

$$\Rightarrow 25 \times 11 - 99R_3 = 25 + R_3$$

$$\Rightarrow 100R_3 = 25(11 - 1)$$

$$\Rightarrow \boxed{R_3 = 2.5 \Omega} \quad \text{Ans}$$

$$\therefore R_1 + R_2 = \frac{25}{9} - \frac{5}{2} = \frac{5}{18}$$

Now by eqⁿ (1)

$$\Rightarrow 25 + R_2 + \frac{5}{2} = 999\left(\frac{5}{18} - R_2\right)$$

$$\Rightarrow 1000R_2 = \frac{555}{2} - \frac{55}{2} = \frac{500}{2}$$

$$\Rightarrow \boxed{R_2 = \frac{1}{4} = 0.25 \Omega} \quad \text{Ans}$$

$$R_1 = \frac{25}{9} - \left(\frac{1}{4} + \frac{5}{2}\right)$$


$$= \frac{25}{9} - \frac{11}{4}$$

$$= \frac{100 - 99}{36} = \frac{1}{36}$$

$$= 0.0278 \Omega$$

Ans


19/

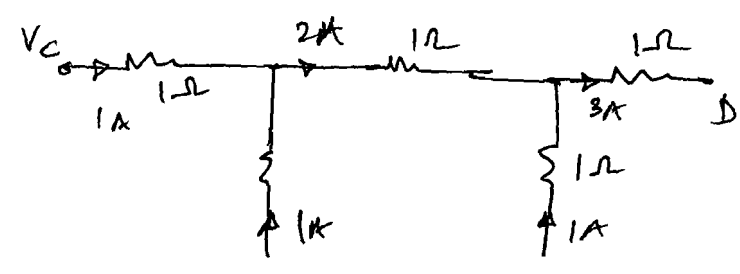

$$V_c - (1) - (2) - (3) = V_D$$

$$V_c - V_D = 6 \text{ Volt} \quad \underline{\text{Ans.}}$$

20/

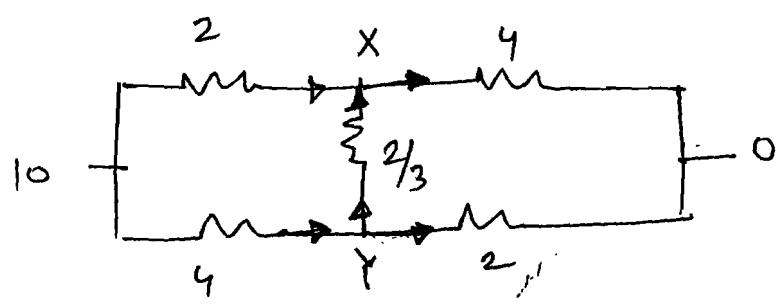

by Kirchoff's junction Rule

$$\frac{10-x}{2} + \frac{(y-x)3}{2} = \frac{x}{4} \quad \text{--- (1)}$$

$$\frac{10-y}{4} = \frac{(y-x)3}{2} + \frac{y}{2} \quad \text{--- (2)}$$

by (1) $9x - 6y = 20$ by (2) $-6x + 9y = 10$

hence $x = 16/3, y = 14/3$


$\therefore x - y = 2/3$

$\therefore \text{current} = \frac{2/3}{2/3} = 1 \text{ Amp} \quad \underline{\text{Ans}}$

21/


$R_1 = 5R$

In latter case

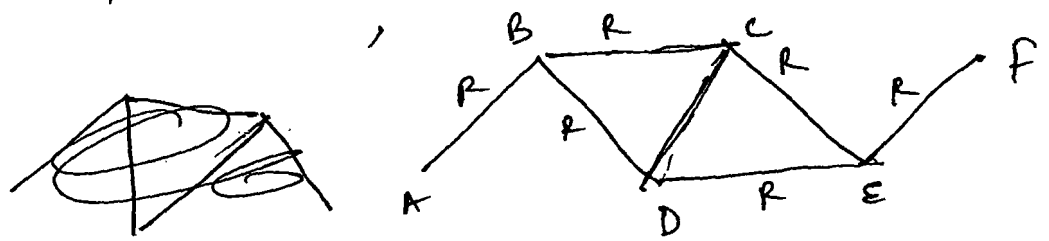


by wheatstone bridge No current in 'D' hence can remove. Hence

$0 \dots 0 + R + R = 3R$

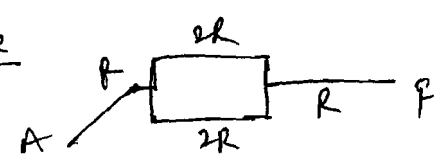

22

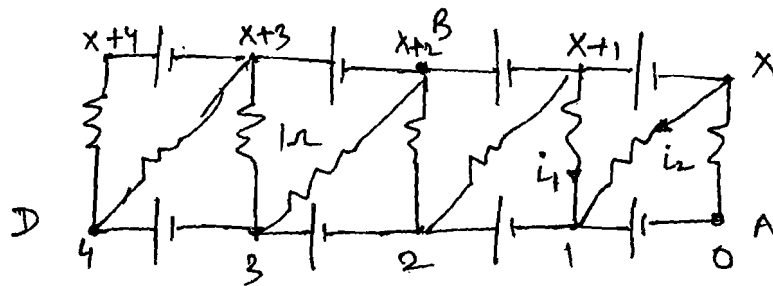

$$i_1 = \frac{x}{1} \quad i_2 = \frac{x-1}{1}$$

junction law at 'D'

$$3 \left[\left(\frac{x-1}{1} \right) + \frac{x}{1} \right] + \frac{x-0}{1} = \frac{-x}{1} + \frac{1-x}{1}$$

$$\Rightarrow 3x - 3 + 3x + x = -2x + 1$$

$$\Rightarrow 9x = 4 \quad \Rightarrow x = 4/9 \text{ Volt}$$

Hence

$$V_A - V_B = 0 - (x+2)$$

$$= 0 - \left(\frac{4}{9} + 2 \right) = -\frac{22}{9} \text{ Volt}$$

Ans

23

When S is open

$$i_1 = \frac{36}{9} = 4 \text{ A}$$

$$i_2 = \frac{36}{9} = 4 \text{ Amp}$$

potential drop
across 6Ω in
left branch

$$= 6 \times 4 = 24$$


hence

$$V_A = 36 - 24 = 12 \text{ Volt}$$

similarity $V_B = 36 - 12 = 24 \text{ Volt}$


(i)

$$V_A - V_B = -12 \text{ Volt}$$

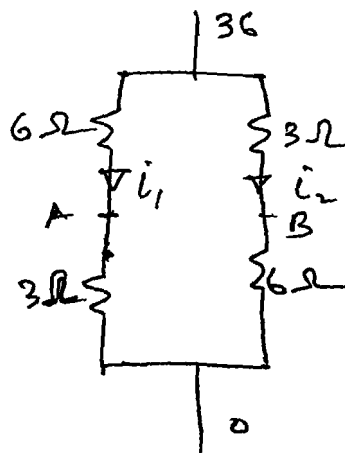

23


(ii)

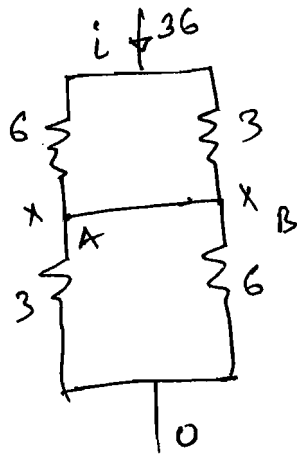

Req = 4Ω

$$i = \frac{36}{4} = 9 \text{ Amp}$$

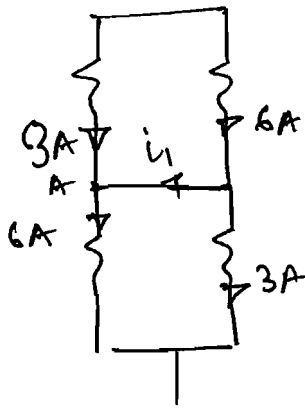current through 6Ω will be 3A and current through 3Ω will be 6A.



by junction A


$$i_1 + 3 = 6$$

$$i_1 = 3 \text{ Amp}$$

[3 Amp from B to A]
current through S.

Ans.




24

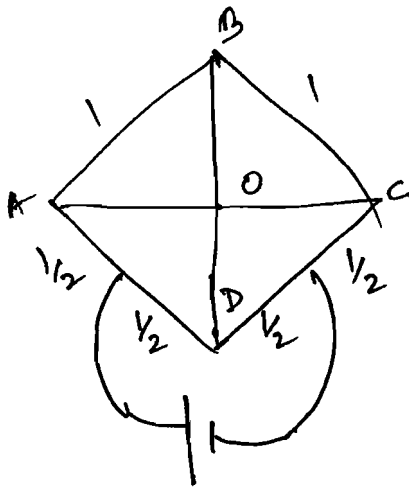

By symmetry

BO and OD will have no current.

hence

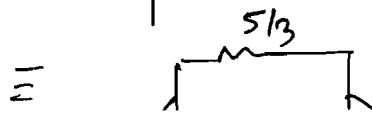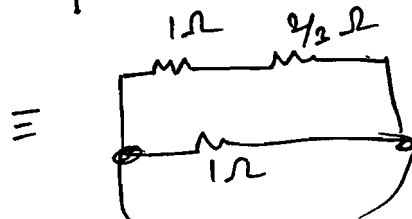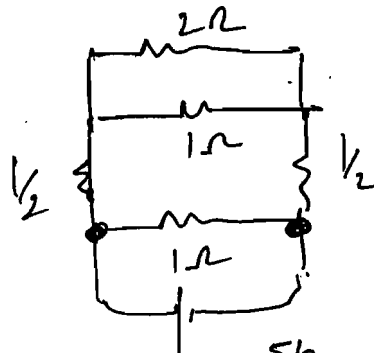


$$R_{eq} = \frac{5/3}{(1+1)} = 5/8 \Omega$$


35

25

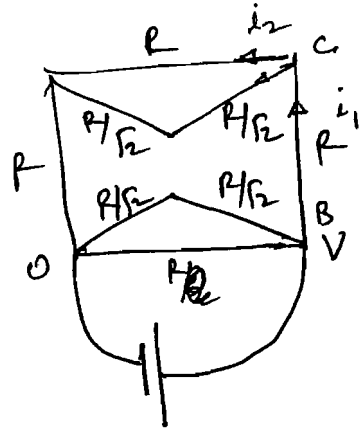By symmetry we can make equivalent circuit as given below



for
Req
calculation:

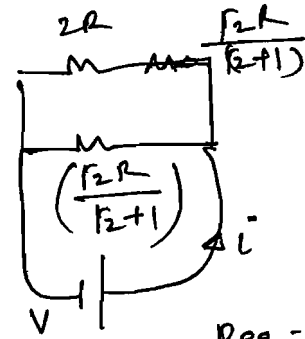

$$R_{eq} = \frac{\left(2R + \frac{R}{2+1}\right) \times \frac{R}{2+1}}{2R + \frac{2R}{2+1}}$$

$$R_{eq} = \frac{(3R+2)R}{2(2+1)(2+1)}$$

$$i = \frac{V}{R_{eq}}$$

let current in the circuit is i
current in branch

$$BC, i_1 = \frac{\left(\frac{R}{2+1}\right) \cdot i}{2R + \frac{2R}{2+1}}$$

$$= \frac{R}{2(2R+1)} i$$

current in CD

i_2 can be calculated as

$$= \frac{R}{(2+1)R} i_1$$

$$= \frac{R}{(2+1)} \times \frac{R}{2(2R+1)} i$$

$$= \frac{i}{(2+1)(2R+1)}$$

$$\therefore \text{Power in CD} = i_2^2 R = \frac{i^2 R}{(2+1)^2 (2R+1)^2} = \frac{V^2 R}{R_{eq}^2 (2+1)^2 (2R+1)^2}$$

$$\text{Power in AB} = \frac{V^2}{R}$$

$$\text{Ratio of Heat liberated} = \frac{P_{AB}}{P_{CD}}$$

$$\frac{P_{AB}}{P_{CD}} = \frac{V^2/R \cdot \text{req}^2 (\sqrt{2}+1)^2 (2\sqrt{2}+1)^2}{V^2 R}$$

$$= \frac{1}{R^2} \cdot \frac{(3\sqrt{2}+2)^2 \cdot R^2 (\cancel{\sqrt{2}+1}^2) (\cancel{2\sqrt{2}+1}^2)}{2 (\cancel{\sqrt{2}+1}^2) (\cancel{2\sqrt{2}+1}^2)}$$

$$= \frac{18 + 4 + 12\sqrt{2}}{2}$$

$$= \frac{22 + 12\sqrt{2}}{2}$$

$$= 11 + 6\sqrt{2}$$

Aus

Only One Option Correct

1. (C)

(c) In case of balanced meter bridge

$$\frac{R}{l} = \frac{X}{100-l} \quad \text{Given: } X = 90 \Omega, l = 40.0 \text{ cm}$$

$$\therefore R = \frac{Xl}{100-l} = \frac{90 \times 40}{60} = 60 \Omega$$

$$\therefore \frac{\Delta R}{R} = \frac{\Delta l}{l} + \frac{\Delta(100-l)}{100-l} \Rightarrow \frac{\Delta R}{60} = \frac{0.1}{40} + \frac{0.1}{60}$$

$$\therefore \Delta R = 0.25 \Omega$$

Therefore, $R = (60 \pm 0.25) \Omega$

2. (B)

(b) As resistance of wire, $R = \int \rho \frac{l}{A}$

$$R_{Fe} = \frac{\rho_{Fe} \times l_{Fe}}{A_{Fe}} = \frac{10^{-7} \times 50 \times 10^{-3}}{4 \times 10^{-6}} = \frac{25}{2} \times 10^{-4}$$

$$R_{Al} = \frac{\rho_{Al} \times l_{Al}}{A_{Al}} = \frac{2.7 \times 10^{-8} \times 50 \times 10^{-3}}{(49-4) \times 10^{-6}} = \frac{2.7 \times 50}{45} \times 10^{-5}$$

$$= 0.3 \times 10^{-4}$$

As potential difference across both resistors is same, so they are in parallel combination.

$$\therefore R_{PQ} = \frac{R_{Fe} \times R_{Al}}{R_{Fe} + R_{Al}} = \frac{12.5 \times 10^{-4} \times 0.3 \times 10^{-4}}{12.8 \times 10^{-4}} = \frac{1875}{64} \mu\Omega$$

3. (C)

(e) Electric field at a distance r from line charge

$$E = \frac{\lambda}{2\pi\epsilon r} = \frac{dV}{dr} \quad (\lambda = \text{linear charge density of wire})$$

$$dV = -\frac{\lambda}{2\pi\epsilon r} dr$$

Current through the elemental shell

$$I = \frac{|dV|}{dr} = \frac{\frac{\lambda}{2\pi\epsilon r} dr}{\frac{1}{\sigma} \times \frac{dr}{2\pi r l}} = \frac{\lambda \sigma l}{\epsilon}$$

$$(\because R = \rho \frac{l}{A} \therefore dR = \rho \frac{dr}{2\pi r l} = \frac{1}{\sigma} \frac{dr}{2\pi r l})$$

This current is radially outwards,

$$\therefore \frac{d}{dt}(\lambda l) = \frac{-\lambda \sigma l}{\epsilon} \Rightarrow \int_{\lambda_0}^{\lambda} \frac{d\lambda}{\lambda} = -\left(\frac{\sigma}{\epsilon}\right) \int_0^t dt$$

$$\Rightarrow \lambda = \lambda_0 e^{-(\sigma/\epsilon)t}$$

$$\therefore J = \frac{I}{2\pi r l} = \frac{\lambda \sigma l}{2\pi \epsilon r l} = \frac{\lambda \sigma}{2\pi \epsilon r}$$

$$\text{or, } J = \left(\frac{\lambda_0 \sigma}{2\pi \epsilon r}\right) e^{-(\sigma/\epsilon)t} \Rightarrow J = J_0 e^{-(\sigma/\epsilon)t}$$

One or More than One Option Correct

1. (A, B, D)

(a, b, d) No current is flowing through resistance R_2 .

Applying KVL in loop

$$V_1 - iR_1 + V_2 - iR_3 = 0$$

$$\therefore i = \frac{V_1 + V_2}{R_1 + R_3} \quad \dots (i)$$

Applying KVL in loop BCDEB

$$V_1 - iR_1 = 0 \quad \therefore i = \frac{V_1}{R_1} \quad \dots (ii)$$

$$\text{From eq. (i) \& (ii) } \frac{V_1}{R_1} = \frac{V_1 + V_2}{R_1 + R_3}$$

$$\therefore V_1 R_1 + V_1 R_3 = V_1 R_1 + V_2 R_1$$


$$\Rightarrow V_1 R_3 = V_2 R_1$$

If $V_1 = V_2$ then $R_1 = R_3 = R_2$

If $V_1 = V_2$ then $R_1 = R_3 = 2R_2$

If $V_1 = 2V_2$ then $2R_3 = R_1$

If $2V_1 = V_2$ then $R_3 = 2R_1 = R_2$

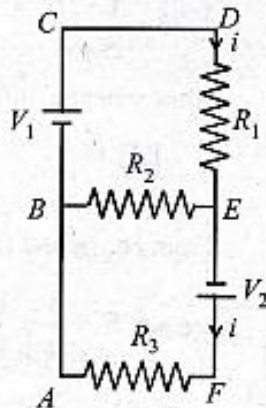

2. (B, D)

$$(b, d) \text{ Heat produced, } H = \left(\frac{V^2}{R} \right) t = \frac{V^2}{R} \times 4 \dots (i)$$

$$\text{where } R = \rho \frac{l}{A} = \frac{4\rho l}{\pi d^2}$$

When resistances are connected in series

$$\text{Total resistance} = R_1 + R_2 = 2 \left[\frac{4\rho l}{4\pi d^2} \right] = 2 \times \frac{R}{4} = \frac{R}{2}$$

$$\therefore H = \frac{V^2}{R/2} \times t_2 \dots (ii)$$

From eq. (i) and (ii) $t_2 = 2 \text{ min.}$

When resistance are connected in parallel

$$\text{Total resistance} = \frac{R_1 R_2}{R_1 + R_2} = \frac{R_1^2}{2R_1} = \frac{R/4}{2} = \frac{R}{8}$$

$$\therefore H = \frac{V^2}{R/8} \times t_2 \dots (iii)$$

From eq. (i) and (iii) $t_2 = 0.5 \text{ min}$


3. (A, B, C, D)

(a, b, c, d) At $t = 0$, i.e., As soon as the key is pressed, Capacitors act as short circuit and voltmeter display reading, $-5V$

At $t = \infty$, i.e., after a long time of key press, Capacitor acts as open circuit and no current flows through voltmeter (\because very high resistance of voltmeter) so it display $+5V$.

$$q_1 = 2CV(1 - e^{-t/2CR}), \quad i_1 = \frac{V}{R} e^{-\frac{t}{2CR}}$$
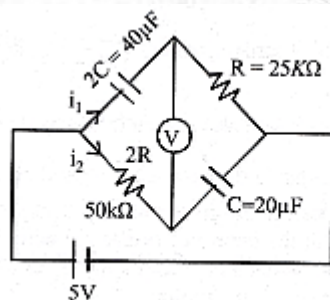
$$q_2 = CV(1 - e^{-t/2CR}), \quad i_2 = \frac{V}{2R} e^{-\frac{t}{2CR}}$$



$$\therefore \Delta V = -i_2 \times 2R + \frac{CV_1}{2C} = V \left[1 - 2e^{-t/2CR} \right] = 0$$

i.e., At time $t = \ln 2s$ voltmeter will display reading 0 V.

$$\text{At } \tau = 1 \text{ sec, } i = \frac{i_0}{e} \quad \left[\because i = i_0 e^{-t/\tau} \right]$$

i.e., After 1s current in the ammeter becomes $\frac{1}{e}$ of the initial value.

After a long time no current flows since both capacitor and voltmeter do not allow current to flow.

4. (C, D)

With the use of filament and the evaporation involved, the filament will become thinner thereby decreasing the area of cross-section and increasing the resistance. Therefore the filament will consume less power towards the end of life.

$$\text{As power, } P = \frac{V^2}{R} \text{ or, } P \propto \frac{1}{r} \quad (\because V = \text{constant})$$

As the evaporation is non-uniform, the area of cross-section will be different at different cross-section. Therefore temperature distribution will be non-uniform. The filament will break at the point where the temperature is maximum.

When the filament temperature is higher $\left(\lambda_n \propto \frac{1}{T} \right)$, it emits light of lower wavelength or higher band of frequencies.

5. (A, C, D)

(a, c, d) Resistance of elementary strips

$$\int \frac{1}{dR} = \int_{R_1}^{R_2} \frac{tdx}{\rho \pi x} \Rightarrow \frac{1}{R} = \frac{t}{\pi \rho} \ln \left(\frac{R_2}{R_1} \right)$$

$$\text{Resistance, } R = \frac{\pi \rho}{t \ln \left(\frac{R_2}{R_1} \right)} \Rightarrow I = \frac{V_0}{R} = \frac{V_0 t \ln \left(\frac{R_2}{R_1} \right)}{\pi \rho}$$

Hence option (a) is correct.

And, for circular motion of electron, ΔV develops

Inner surface at higher potential so that electric field develops radially outward.

So option (b) is correct.


$$\frac{mV_d^2}{r} = q\bar{E} \Rightarrow \bar{E} = \frac{mV_d^2}{qr}$$

$$\bar{E} = \frac{mI^2}{n^2 e^2 A^2 qr}$$

$$\left(\because \text{Drift velocity, } V_d = \frac{I}{neA} \right)$$


$$\Delta V = \int \bar{E} \cdot d\vec{r} \quad \text{or, } \Delta V \propto V_d^2 \quad \therefore \Delta V \propto I^2$$

Hence option (d) is correct.

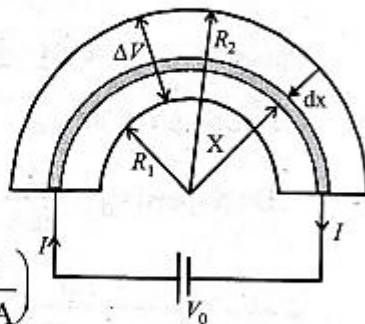

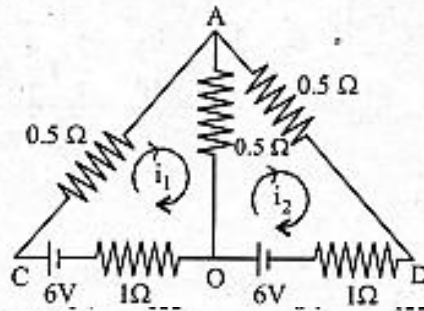6. (A, B, C, D)

(a,b,c,d) Here we have folding symmetry, so circuit can be redrawn as



By mesh analysis:

In circuit ACO

$$0.5i_1 + 0.5(i_1 - i_2) + i_1 - 6 = 0$$

$$0.5i_1 + 0.5i_1 - 0.5i_2 + i_1 - 6 = 0$$

$$2i_1 - 0.5i_2 = 6$$

$$8i_1 - 2i_2 = 24$$

....(i)

In circuit ADO

$$0.5i_2 + 1 \times i_2 - 12 + 0.5(i_2 - i_1) = 0$$

$$2i_2 - 0.5i_1 = 12$$

....(ii)

from (i) and (ii), we get

$$7.5i_1 = 36$$

$$i_1 = \frac{36}{7.5} = 4.8 \text{ A}$$

So, current through ' R_1 ' = $i_1 = 4.8 \text{ A}$

Putting $i_1 = 4.8 \text{ A}$ in (ii), we get

$$2i_2 - 2.4 = 12$$

$$2i_2 = 14.4 \Rightarrow i_2 = 7.2 \text{ A} \Rightarrow \text{Current through } R_1 = 7.2 \text{ A}$$


$$\text{So, current through } R_2 = \frac{|i_2 - i_1|}{2} = 1.2 \text{ A}$$

$$\text{Current through } R_5 = \frac{i_1}{2} = 2.4 \text{ A}$$

Stem Type Questions

1. (1.33)

When switch is connected to position P

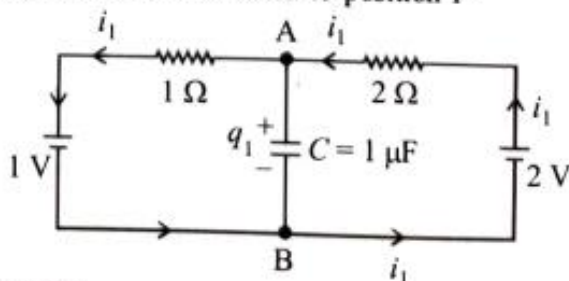

From KVL,

$$V_A - 1 \cdot i_1 - 1 + 2 - 2i_1 = V_A \Rightarrow 3i_1 = 1 \quad \therefore i_1 = \frac{1}{3} \text{ A}$$


Again $V_A - 1 \cdot i_1 - 1 = V_B$ or, $V_A - V_B = 1 + i_1 = \frac{4}{3} \text{ V}$

Potential drop across capacitor $\Delta V = \frac{4}{3} \text{ V}$

\therefore Charge on capacitor, $q_1 = C\Delta V = 1 \times \frac{4}{3} \mu\text{C}$

$$q_1 = 1.33 \mu\text{C}$$

When switch is connected to position Q

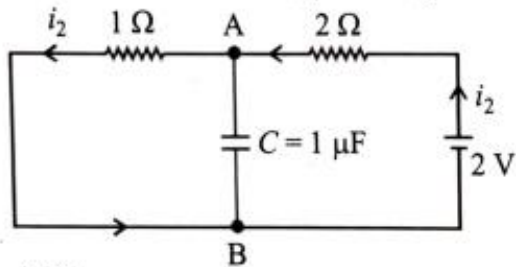

From KVL,

$$V_A - 1 \cdot i_2 + 2 - 2i_2 = V_A \Rightarrow 3i_2 = 2 \quad \therefore i_2 = \frac{2}{3} \text{ A}$$

Again, $V_A - i_2 \times 1 = V_B$


$$V_A - V_B = i_2 \times 1 = \frac{2}{3} \text{ V}$$

Potential difference across capacitor $\Delta V = \frac{2}{3} \text{ V}$

\therefore Charge on capacitor, $q_2 = C\Delta V = 1 \times \frac{2}{3} = 0.67 \mu\text{C}$

2. (0.67)

When switch is connected to position P

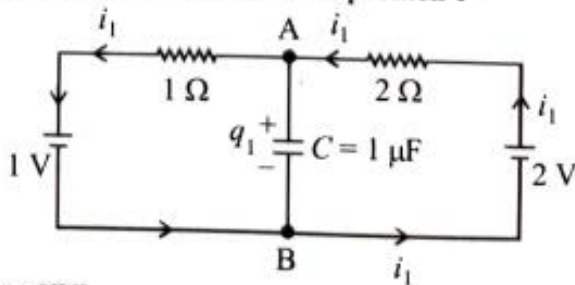

From KVL,

$$V_A - 1 \cdot i_1 - 1 + 2 - 2i_1 = V_A \Rightarrow 3i_1 = 1 \quad \therefore i_1 = \frac{1}{3} \text{ A}$$


Again $V_A - 1 \cdot i_1 - 1 = V_B$ or, $V_A - V_B = 1 + i_1 = \frac{4}{3} \text{ V}$

Potential drop across capacitor $\Delta V = \frac{4}{3} \text{ V}$

\therefore Charge on capacitor, $q_1 = C\Delta V = 1 \times \frac{4}{3} \mu\text{C}$

$$q_1 = 1.33 \mu\text{C}$$

When switch is connected to position Q

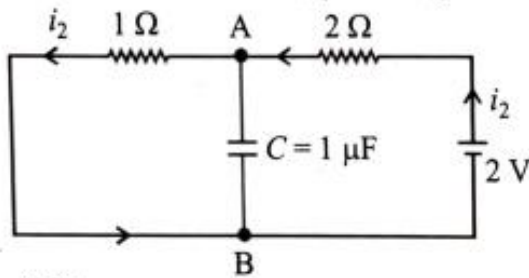

From KVL,

$$V_A - 1 \cdot i_2 + 2 - 2i_2 = V_A \Rightarrow 3i_2 = 2 \quad \therefore i_2 = \frac{2}{3} \text{ A}$$

Again, $V_A - i_2 \times 1 = V_B$

$$V_A - V_B = i_2 \times 1 = \frac{2}{3} \text{ V}$$

Potential difference across capacitor $\Delta V = \frac{2}{3} \text{ V}$

\therefore Charge on capacitor, $q_2 = C\Delta V = 1 \times \frac{2}{3} = 0.67 \mu\text{C}$

Integer / Numerical Answer Type


1. (5)

$$(5) \quad \text{From } \left(\frac{I - I_g}{I_g} \right) S = \frac{V}{I_g} - R$$

$$\frac{1.5 - 0.006}{0.006} \times \frac{2n}{249} = \frac{30}{0.006} - 4990 \quad \therefore n = \frac{2490}{498} = 5$$

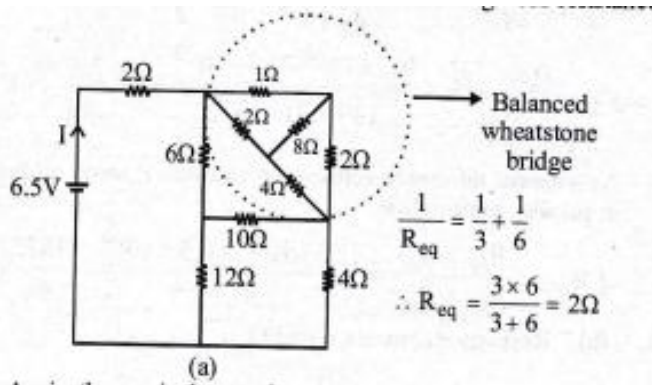
2. (1)

In the figure (a) no current flows through 8Ω resistance



Again the equivalent resistance of balanced wheatstone bridge fig (b) no current through 10Ω resistance.
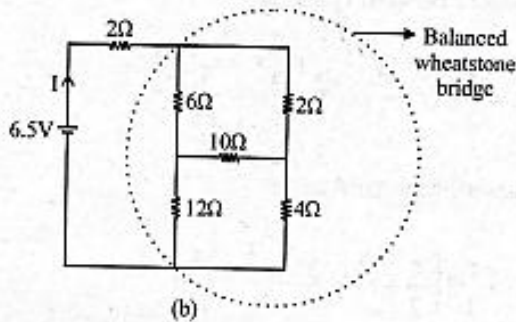
$$\therefore R_{eq} = \frac{6 \times 18}{24} = \frac{9}{2}\Omega$$



Therefore the current through the resistor $R = 2\Omega$

$$I = \frac{V}{R} = \frac{6.5}{2 + \frac{9}{2}} = \frac{6.5}{6.5} = 1A$$


3. (0.27)

(0.27) According to question, resistance R_3 has temperature coefficient, $\alpha = 0.0004^\circ\text{C}^{-1}$

And temperature is increased by 100°C i.e., $\Delta T = 100^\circ\text{C}$

$$R'_3 = R_0(1 + \alpha\Delta T) = 300(1 + \alpha\Delta T)$$

$$\therefore R'_3 = 312\Omega$$

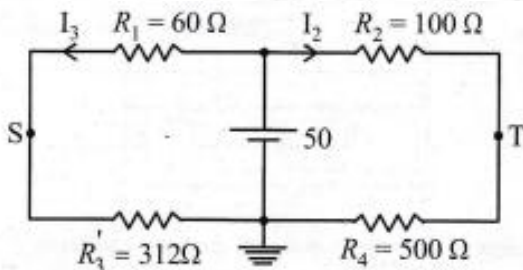

$$\text{Here, } I_1 = \frac{V}{R_1 + R_3} = \frac{50}{372} \text{ and } I_2 = \frac{V}{R_2 + R_4} = \frac{50}{600}$$

$$V_S - V_T = 312I_1 - 500I_2$$


$$= 312 \times \frac{50}{372} - 50 \times \frac{500}{600} = 41.94 - 41.67 = 0.27V$$

Hence voltage developed between S and T = 0.27 Volt

4. (3)

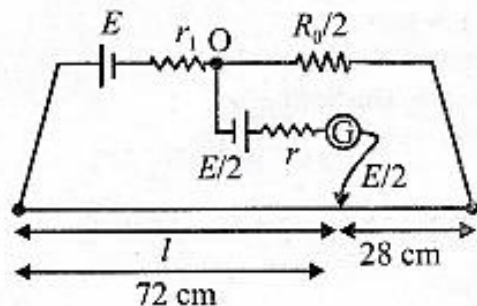(3) Here null point is at 72 cm

$$i \left(\frac{R_0}{2} + 0.28R_0 \right) = \frac{E_0}{2}$$



$$\Rightarrow i \times 0.78R_0 = \frac{E_0}{2}$$


$$i = \frac{E_0}{2 \times 0.78R_0} = \frac{E_0}{r_1 + \frac{3}{2}R_0}$$

or, $r_1 + 1.5 R_0 = 1.56 R_0$

$$\Rightarrow r_1 = 1.56 R_0 - 1.5 R_0 = 0.06 R_0$$

$$\therefore r_1 = 0.06 \times 50 = 3 \Omega$$

5. (5)

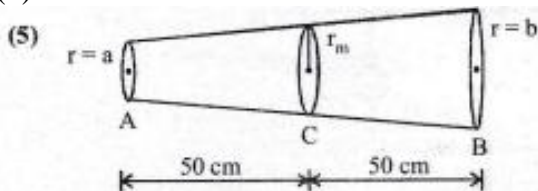

For a frustum, $R = \frac{\rho \ell}{\pi a b}$ and $r_m = \frac{a + b}{2}$

$$\text{So, } R_{AC} = \frac{\rho \ell / 2}{\pi (a r_m)}$$

$$R_{CB} = \frac{\rho \ell / 2}{\pi r_m b} \text{ . By wheatstone bridge principal}$$

$$\frac{R_1}{R_2} = \frac{R_{AC}}{R_{CB}} \Rightarrow \frac{R_1}{1} = \frac{b}{a} = \frac{1}{0.2} = 5$$

$$\text{So, } R_1 = 5 \Omega$$